

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 1


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 65Ω resistor paralel with a 0.634 pF capacitor, at 7.2 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.225 - j\cdot 0.995$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.55\text{dB}$, two matched amplifiers $G_1 = 8.9\text{dB}$ and $G_2 = 9.8\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.5dB). Assume the input power is 3.90mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

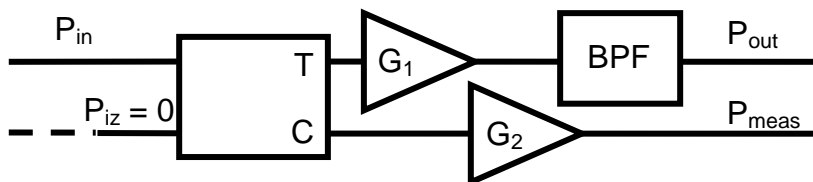

- A 50Ω source is connected to a $43.3\Omega + j\cdot 41.7\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.2dB and Noise Factor 1.28dB) and Device 2 (Gain 11.4dB and Noise Factor 1.00dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 12.8 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 147.6° | 1.720 | -20.4° | 0.090 | -31.0° | 0.550 | -148.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.2


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 39Ω resistor series with a 0.580 nH inductor, at 9.0 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.145 - j \cdot 0.955$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.05\text{dB}$, two matched amplifiers $G_1 = 7.9\text{dB}$ and $G_2 = 10.4\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.8dB). Assume the input power is 1.45mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

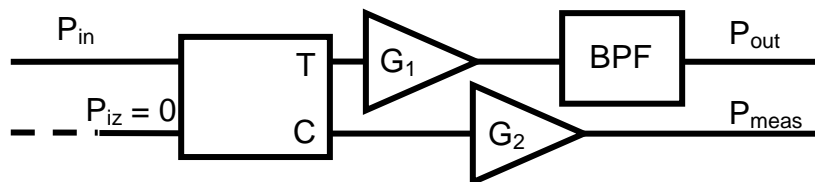

- A 50Ω source is connected to a $66.8\Omega - j \cdot 53.8\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.6dB and Noise Factor 1.25dB) and Device 2 (Gain 11.8dB and Noise Factor 1.00dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.612 | 124.8° | 1.629 | -42.8° | 0.096 | -38.8° | 0.556 | -164.4° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 3


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 60Ω resistor series with a 0.897 nH inductor, at 9.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.040 - j\cdot 0.825$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.50\text{dB}$, two matched amplifiers $G_1 = 6.9\text{dB}$ and $G_2 = 9.8\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.5dB). Assume the input power is 1.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 16.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

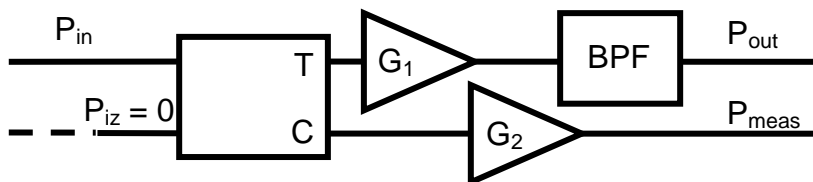

- A 50Ω source is connected to a $62.6\Omega - j\cdot 48.5\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.4dB and Noise Factor 1.23dB) and Device 2 (Gain 11.6dB and Noise Factor 0.93dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.615 | 126.0° | 1.633 | -41.5° | 0.095 | -38.0° | 0.555 | -163.5° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 4


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 35Ω resistor paralel with a 1.607 nH inductor, at 7.3 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.925 + j\cdot 0.925$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.95\text{dB}$, two matched amplifiers $G_1 = 6.9\text{dB}$ and $G_2 = 11.0\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.7dB). Assume the input power is 2.65mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 24.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

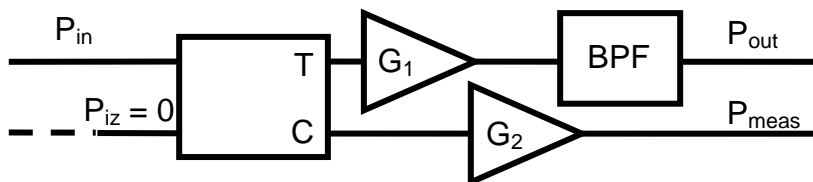

- A 50Ω source is connected to a $58.5\Omega + j\cdot 46.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.25dB) and Device 2 (Gain 10.4dB and Noise Factor 1.05dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.9 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.631 | 133.3° | 1.658 | -33.8° | 0.090 | -33.8° | 0.550 | -158.1° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 5


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 73Ω resistor paralel with a 0.433 pF capacitor, at 9.3 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.170 - j \cdot 1.105$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.10\text{dB}$, two matched amplifiers $G_1 = 8.9\text{dB}$ and $G_2 = 10.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.3dB). Assume the input power is 2.50mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 19.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

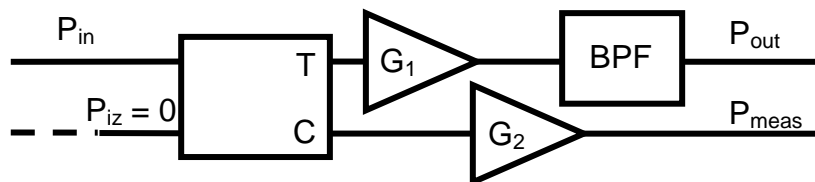

- A 50Ω source is connected to a $62.9\Omega - j \cdot 66.2\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.6dB and Noise Factor 1.24dB) and Device 2 (Gain 11.4dB and Noise Factor 0.92dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 15.0 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.600 | 120.0° | 1.614 | -48.0° | 0.100 | -42.0° | 0.560 | -168.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 6


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 38Ω resistor paralel with a 0.701 nH inductor, at 9.6 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.910 - j \cdot 1.225$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.55\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 10.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.4dB). Assume the input power is 3.50mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

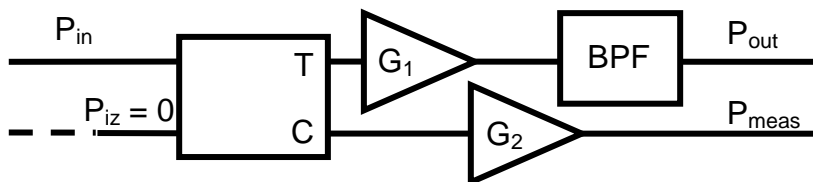

- A 50Ω source is connected to a $55.3\Omega - j \cdot 41.7\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.8dB and Noise Factor 1.27dB) and Device 2 (Gain 11.1dB and Noise Factor 1.03dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.0 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.650 | -164.0° | 2.508 | 28.0° | 0.070 | 3.0° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 7


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 31Ω resistor paralel with a 1.291 nH inductor, at 8.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.750 - j\cdot 0.725$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.05\text{dB}$, two matched amplifiers $G_1 = 8.1\text{dB}$ and $G_2 = 11.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.6dB). Assume the input power is 3.45mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 20.2dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

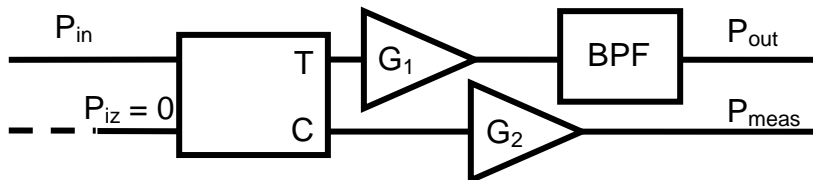

- A 50Ω source is connected to a $36.4\Omega - j\cdot 40.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.7dB and Noise Factor 1.10dB) and Device 2 (Gain 11.6dB and Noise Factor 0.95dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.2 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.638 | 142.4° | 1.698 | -25.4° | 0.090 | -32.4° | 0.550 | -151.8° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 8


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 53Ω resistor paralel with a 0.286 pF capacitor, at 9.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.165 - j\cdot 0.840$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.05\text{dB}$, two matched amplifiers $G_1 = 9.9\text{dB}$ and $G_2 = 11.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.8dB). Assume the input power is 3.30mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 24.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

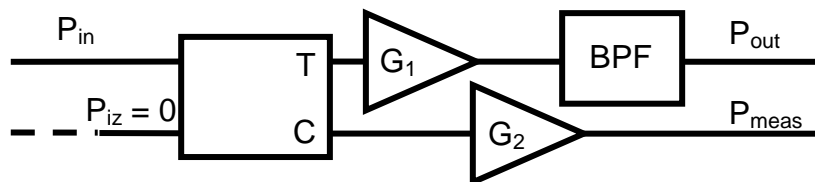

- A 50Ω source is connected to a $36.7\Omega - j\cdot 58.1\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.5dB and Noise Factor 1.12dB) and Device 2 (Gain 11.3dB and Noise Factor 0.91dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|-------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.602 | 174.0° | 2.306 | 7.2° | 0.080 | -4.0° | 0.520 | -114.4° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 9


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 72Ω resistor parallel with a 0.421 pF capacitor, at 10.0 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.730 + j\cdot 0.865$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.30\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 11.0\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.2dB). Assume the input power is 3.65mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 18.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

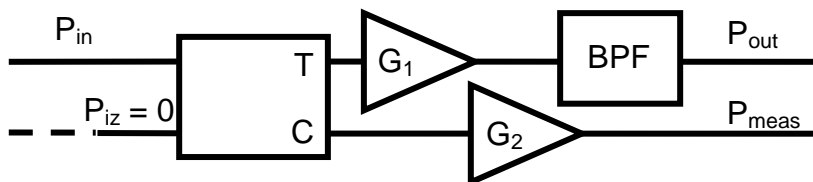

- A 50Ω source is connected to a $36.0\Omega + j\cdot 36.6\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.4dB and Noise Factor 1.22dB) and Device 2 (Gain 11.4dB and Noise Factor 0.97dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.632 | -171.8° | 2.430 | 20.2° | 0.076 | 0.6° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 10


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 44Ω resistor paralel with a 0.348 pF capacitor, at 7.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.950 + j \cdot 1.100$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.40\text{dB}$, two matched amplifiers $G_1 = 9.3\text{dB}$ and $G_2 = 10.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.0dB). Assume the input power is 1.50mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 19.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

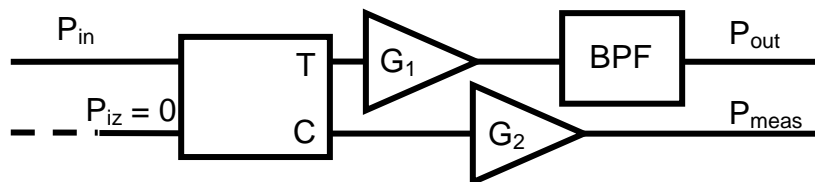

- A 50Ω source is connected to a $44.9\Omega - j \cdot 55.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.1dB and Noise Factor 1.16dB) and Device 2 (Gain 10.3dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.0 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 145.0° | 1.709 | -23.0° | 0.090 | -32.0° | 0.550 | -150.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 11


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 40Ω resistor paralel with a 0.626 nH inductor, at 9.6 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.225 + j \cdot 1.200$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.80\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 8.0\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.3dB). Assume the input power is 2.65mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

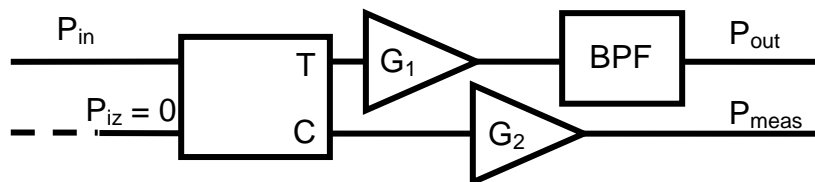

- A 50Ω source is connected to a $48.8\Omega + j \cdot 51.6\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.1dB and Noise Factor 1.29dB) and Device 2 (Gain 10.7dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.2 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.644 | -166.6° | 2.482 | 25.4° | 0.072 | 2.2° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 12


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 35Ω resistor paralel with a 0.445 pF capacitor, at 8.2 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.015 - j \cdot 0.710$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.65\text{dB}$, two matched amplifiers $G_1 = 9.6\text{dB}$ and $G_2 = 8.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.6dB). Assume the input power is 2.25mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

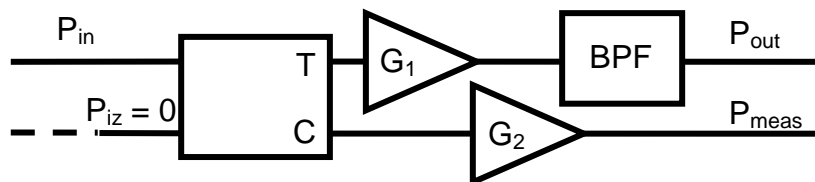

- A 50Ω source is connected to a $54.5\Omega + j \cdot 55.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.2dB and Noise Factor 1.16dB) and Device 2 (Gain 10.6dB and Noise Factor 1.07dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.4 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.638 | -169.2° | 2.456 | 22.8° | 0.074 | 1.4° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 13


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 50Ω resistor paralel with a 0.364 pF capacitor, at 8.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.910 - j\cdot 0.810$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.45\text{dB}$, two matched amplifiers $G_1 = 6.5\text{dB}$ and $G_2 = 9.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.1dB). Assume the input power is 1.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 16.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

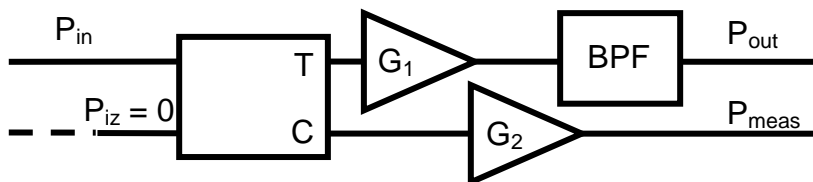

- A 50Ω source is connected to a $58.0\Omega - j\cdot 39.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.0dB and Noise Factor 1.18dB) and Device 2 (Gain 10.8dB and Noise Factor 0.98dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 12.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 150.2° | 1.732 | -17.8° | 0.090 | -30.0° | 0.550 | -146.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 14


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 52Ω resistor series with a 0.674 nH inductor, at 7.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.040 + j \cdot 1.085$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.10\text{dB}$, two matched amplifiers $G_1 = 7.9\text{dB}$ and $G_2 = 8.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.2dB). Assume the input power is 2.30mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

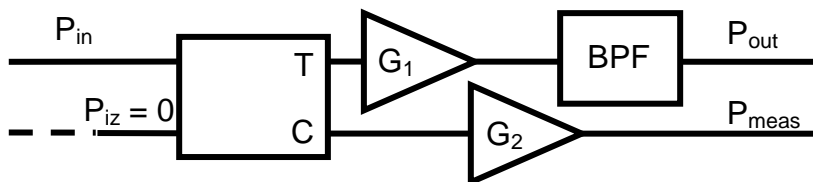

- A 50Ω source is connected to a $63.4\Omega - j \cdot 55.6\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.1dB and Noise Factor 1.18dB) and Device 2 (Gain 10.6dB and Noise Factor 1.05dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 12.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 151.5° | 1.737 | -16.5° | 0.090 | -29.5° | 0.550 | -145.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 15


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 71Ω resistor paralel with a 0.595 pF capacitor, at 6.5 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.950 + j \cdot 1.275$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.60\text{dB}$, two matched amplifiers $G_1 = 7.1\text{dB}$ and $G_2 = 10.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.1dB). Assume the input power is 2.30mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 18.5dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

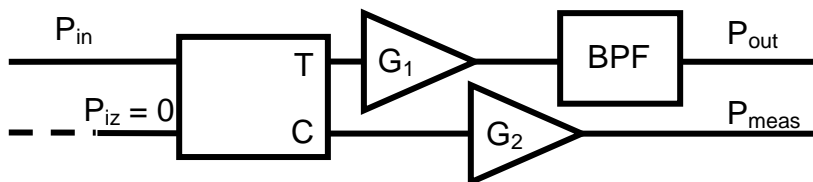

- A 50Ω source is connected to a $52.1\Omega - j \cdot 34.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.9dB and Noise Factor 1.27dB) and Device 2 (Gain 10.2dB and Noise Factor 1.08dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.0 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.620 | -177.0° | 2.378 | 15.0° | 0.080 | -1.0° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 16


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 38Ω resistor paralel with a 0.896 nH inductor, at 7.3 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.855 + j \cdot 1.275$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.90\text{dB}$, two matched amplifiers $G_1 = 8.3\text{dB}$ and $G_2 = 9.6\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.2dB). Assume the input power is 1.60mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

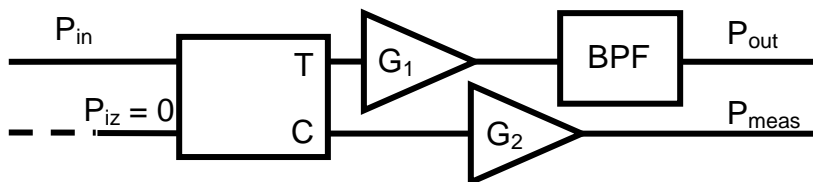

- A 50Ω source is connected to a $67.8\Omega - j \cdot 62.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.9dB and Noise Factor 1.15dB) and Device 2 (Gain 10.3dB and Noise Factor 1.07dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.609 | 123.6° | 1.625 | -44.1° | 0.097 | -39.6° | 0.557 | -165.3° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 17


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 60Ω resistor series with a 0.301 pF capacitor, at 7.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.735 + j \cdot 0.905$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.75\text{dB}$, two matched amplifiers $G_1 = 8.9\text{dB}$ and $G_2 = 10.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.7dB). Assume the input power is 1.30mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.5dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

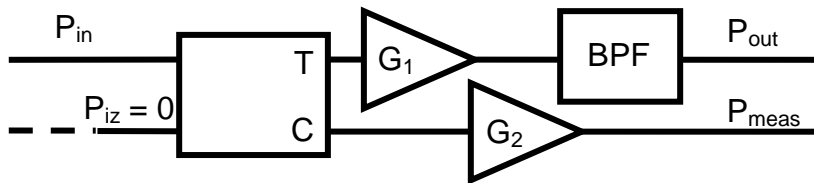

- A 50Ω source is connected to a $47.1\Omega - j \cdot 53.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.7dB and Noise Factor 1.23dB) and Device 2 (Gain 10.5dB and Noise Factor 1.08dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.634 | 137.2° | 1.675 | -30.2° | 0.090 | -33.2° | 0.550 | -155.4° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 18


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 36Ω resistor series with a 1.178 nH inductor, at 7.3 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.890 + j \cdot 1.110$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.10\text{dB}$, two matched amplifiers $G_1 = 8.7\text{dB}$ and $G_2 = 8.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.9dB). Assume the input power is 1.95mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.5dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

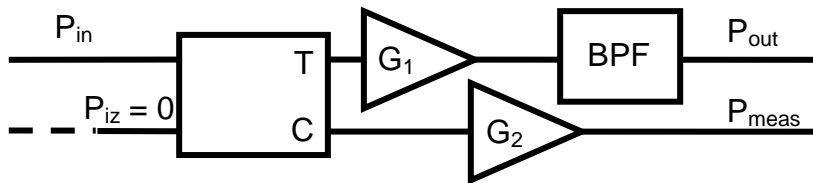

- A 50Ω source is connected to a $51.7\Omega + j \cdot 63.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.25dB) and Device 2 (Gain 10.3dB and Noise Factor 0.98dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.6 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.662 | -158.8° | 2.576 | 33.6° | 0.070 | 5.4° | 0.516 | -101.4° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 19


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

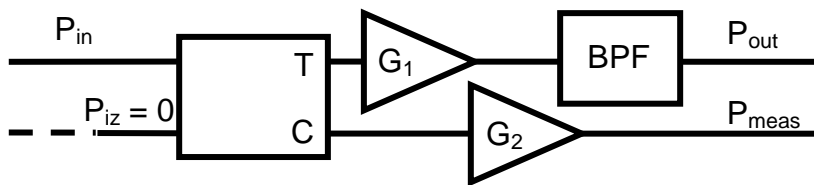1. For a load composed from a 51 Ω resistor series with a 0.649 pF capacitor, at 7.1 GHz, compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
2. For a normalized admittance equal to $0.825 + j \cdot 1.280$ compute the impedance. (**1p**)
3. A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.50\text{dB}$, two matched amplifiers $G_1 = 9.5\text{dB}$ and $G_2 = 10.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.3dB). Assume the input power is 2.00mW.
 - a) Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - b) Compute the power at the measurement port P_{meas} (**0.5p**)
 - c) Assume the same input signal is outside the filter passband at a frequency where the filter provides a 19.8dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)



4. A 50Ω source is connected to a $68.9\Omega - j \cdot 68.1\Omega$ load .
 - a) Compute the reflection coefficient seen by the source. (**0.5p**)
 - b) Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - c) **Draw** the match schematic. (**0.5p**)
5. You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.10dB) and Device 2 (Gain 10.5dB and Noise Factor 0.92dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
6. The scattering parameters of a transistor at 14.3 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.621 | 128.4° | 1.641 | -38.9° | 0.093 | -36.4° | 0.553 | -161.7° |

- a) Prove that you can design a match for maximum gain (**0.5p**)
- b) Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- c) Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.20


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 44Ω resistor series with a 0.477 pF capacitor, at 8.1 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.840 + j\cdot 0.810$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.40\text{dB}$, two matched amplifiers $G_1 = 7.7\text{dB}$ and $G_2 = 9.8\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.3dB). Assume the input power is 1.60mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.0dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

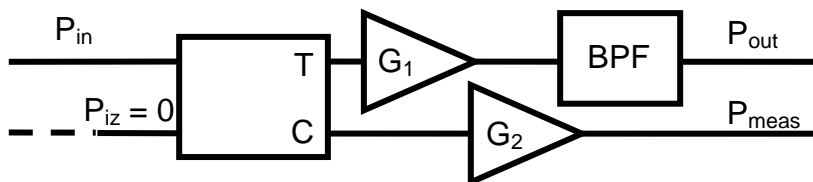

- A 50Ω source is connected to a $46.2\Omega + j\cdot 38.4\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.4dB and Noise Factor 1.19dB) and Device 2 (Gain 10.8dB and Noise Factor 0.90dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.9 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.653 | -162.7° | 2.525 | 29.4° | 0.070 | 3.6° | 0.519 | -107.1° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.21


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 38Ω resistor series with a 1.417 nH inductor, at 8.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.240 + j\cdot 0.825$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.55\text{dB}$, two matched amplifiers $G_1 = 8.4\text{dB}$ and $G_2 = 10.8\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.8dB). Assume the input power is 2.45mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 24.8dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

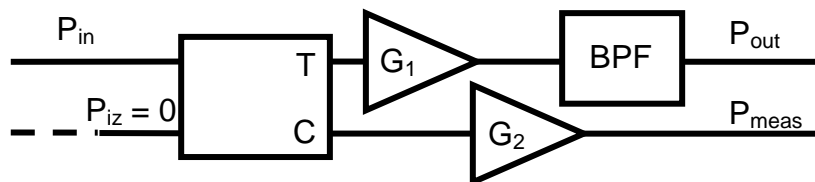

- A 50Ω source is connected to a $41.7\Omega - j\cdot 54.6\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.4dB and Noise Factor 1.15dB) and Device 2 (Gain 11.0dB and Noise Factor 1.02dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 12.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 148.9° | 1.726 | -19.1° | 0.090 | -30.5° | 0.550 | -147.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.22


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 50Ω resistor series with a 0.318 pF capacitor, at 9.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.995 - j\cdot 0.700$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.20\text{dB}$, two matched amplifiers $G_1 = 9.8\text{dB}$ and $G_2 = 8.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.6dB). Assume the input power is 3.20mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 20.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

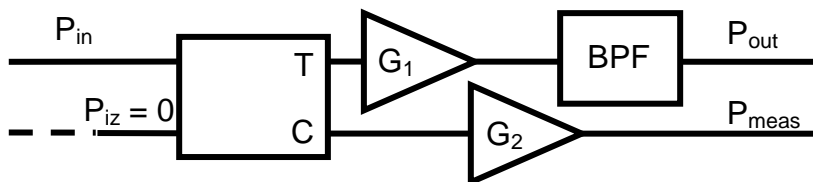

- A 50Ω source is connected to a $43.7\Omega + j\cdot 57.3\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.8dB and Noise Factor 1.12dB) and Device 2 (Gain 11.8dB and Noise Factor 1.06dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.8 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.656 | -161.4° | 2.542 | 30.8° | 0.070 | 4.2° | 0.518 | -105.2° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.23


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 48Ω resistor paralel with a 1.068 nH inductor, at 9.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.745 + j\cdot 0.855$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.95\text{dB}$, two matched amplifiers $G_1 = 6.0\text{dB}$ and $G_2 = 8.7\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.8dB). Assume the input power is 2.20mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 24.2dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

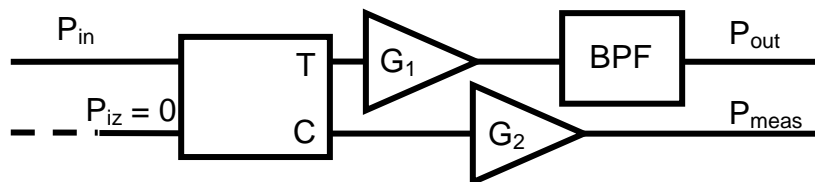

- A 50Ω source is connected to a $46.8\Omega + j\cdot 56.4\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.0dB and Noise Factor 1.27dB) and Device 2 (Gain 10.2dB and Noise Factor 1.02dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.9 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.623 | -175.7° | 2.391 | 16.3° | 0.079 | -0.6° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.24


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 51Ω resistor paralel with a 0.511 pF capacitor, at 8.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.805 + j\cdot 0.845$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.45\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 9.4\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.9dB). Assume the input power is 3.60mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

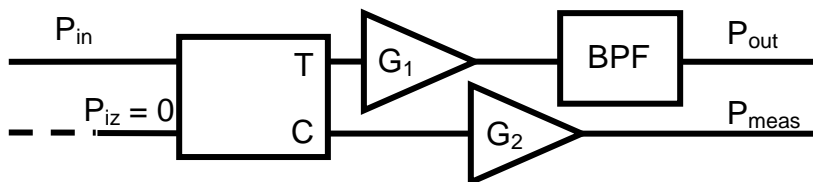

- A 50Ω source is connected to a $55.3\Omega - j\cdot 56.2\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.1dB and Noise Factor 1.29dB) and Device 2 (Gain 10.0dB and Noise Factor 0.97dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.4 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.618 | 127.2° | 1.637 | -40.2° | 0.094 | -37.2° | 0.554 | -162.6° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.25


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 59Ω resistor series with a 0.630 pF capacitor, at 8.2 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.135 - j\cdot 0.775$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.85\text{dB}$, two matched amplifiers $G_1 = 7.0\text{dB}$ and $G_2 = 10.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.0dB). Assume the input power is 2.45mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 20.5dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

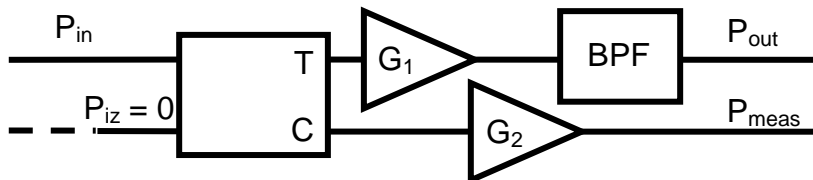

- A 50Ω source is connected to a $30.2\Omega + j\cdot 41.1\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.12dB) and Device 2 (Gain 11.5dB and Noise Factor 0.93dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.3 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.641 | -167.9° | 2.469 | 24.1° | 0.073 | 1.8° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.26


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 50Ω resistor paralel with a 0.515 pF capacitor, at 7.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.265 + j \cdot 1.155$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.80\text{dB}$, two matched amplifiers $G_1 = 6.4\text{dB}$ and $G_2 = 9.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.9dB). Assume the input power is 1.90mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 16.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

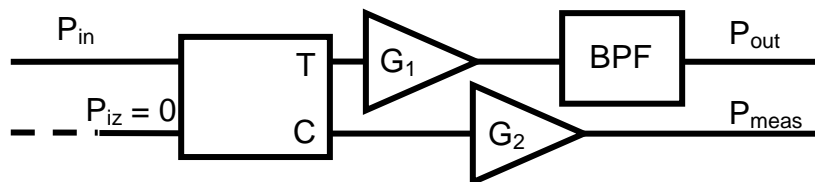

- A 50Ω source is connected to a $53.9\Omega - j \cdot 60.7\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.8dB and Noise Factor 1.25dB) and Device 2 (Gain 11.6dB and Noise Factor 0.91dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.629 | -173.1° | 2.417 | 18.9° | 0.077 | 0.2° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.27


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 74Ω resistor series with a 1.150 nH inductor, at 8.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.085 + j\cdot 0.860$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.55\text{dB}$, two matched amplifiers $G_1 = 9.5\text{dB}$ and $G_2 = 9.7\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.9dB). Assume the input power is 1.80mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.0dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

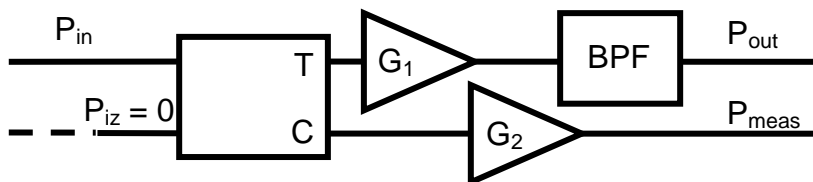

- A 50Ω source is connected to a $45.3\Omega + j\cdot 31.1\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.0dB and Noise Factor 1.26dB) and Device 2 (Gain 11.6dB and Noise Factor 1.05dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|---------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.665 | -157.5° | 2.593 | 35.0° | 0.070 | 6.0° | 0.515 | -99.5° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.28


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 50Ω resistor paralel with a 0.221 pF capacitor, at 9.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.715 - j\cdot 0.940$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.30\text{dB}$, two matched amplifiers $G_1 = 8.1\text{dB}$ and $G_2 = 8.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.0dB). Assume the input power is 2.30mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 23.9dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

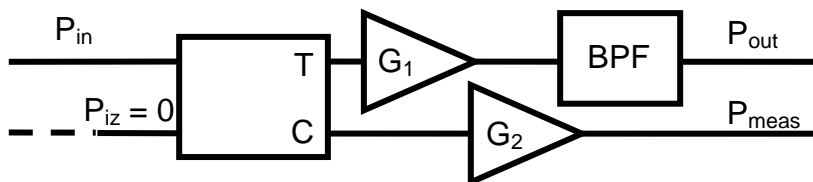

- A 50Ω source is connected to a $65.2\Omega - j\cdot 67.4\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.8dB and Noise Factor 1.24dB) and Device 2 (Gain 11.0dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.8 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.626 | -174.4° | 2.404 | 17.6° | 0.078 | -0.2° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.29


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 42Ω resistor paralel with a 1.559 nH inductor, at 6.5 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.985 - j\cdot 0.815$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.05\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 8.1\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.8dB). Assume the input power is 2.55mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 17.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

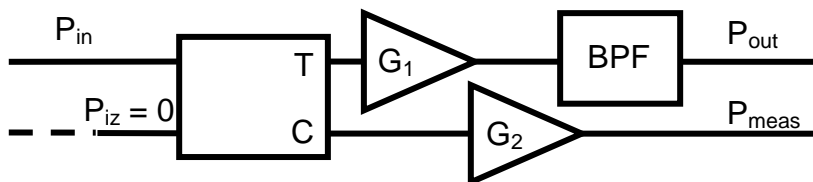

- A 50Ω source is connected to a $45.7\Omega - j\cdot 39.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.8dB and Noise Factor 1.24dB) and Device 2 (Gain 11.1dB and Noise Factor 1.08dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.1 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.617 | -178.5° | 2.366 | 13.7° | 0.080 | -1.5° | 0.520 | -109.9° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.30


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

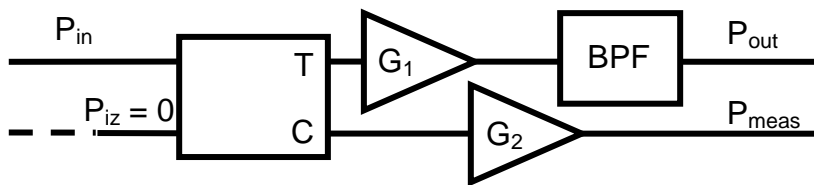1. For a load composed from a 57 Ω resistor paralel with a 0.320 pF capacitor, at 7.2 GHz, compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
2. For a normalized admittance equal to $0.900 + j \cdot 0.990$ compute the impedance. (**1p**)
3. A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.65\text{dB}$, two matched amplifiers $G_1 = 7.3\text{dB}$ and $G_2 = 10.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.6dB). Assume the input power is 2.80mW.
 - a) Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - b) Compute the power at the measurement port P_{meas} (**0.5p**)
 - c) Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)



4. A 50Ω source is connected to a $65.7\Omega - j \cdot 39.5\Omega$ load .
 - a) Compute the reflection coefficient seen by the source. (**0.5p**)
 - b) Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - c) **Draw** the match schematic. (**0.5p**)
5. You must design a LNA using two amplifiers: Device 1 (Gain 9.8dB and Noise Factor 1.11dB) and Device 2 (Gain 11.0dB and Noise Factor 0.90dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
6. The scattering parameters of a transistor at 12.9 GHz are as follows:

| S ₁₁ | | S ₁₂ | | S ₂₁ | | S ₂₂ | |
|-----------------|--------|-----------------|--------|-----------------|--------|-----------------|---------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.640 | 146.3° | 1.715 | -21.7° | 0.090 | -31.5° | 0.550 | -149.0° |

- a) Prove that you can design a match for maximum gain (**0.5p**)
- b) Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- c) Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 31


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 60Ω resistor paralel with a 1.179 nH inductor, at 9.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.870 - j\cdot 0.775$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.90\text{dB}$, two matched amplifiers $G_1 = 6.3\text{dB}$ and $G_2 = 8.6\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.5dB). Assume the input power is 3.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.9dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

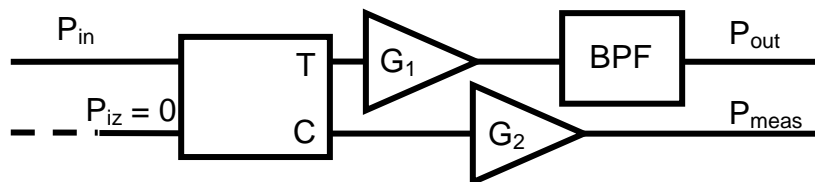

- A 50Ω source is connected to a $35.2\Omega + j\cdot 64.4\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.7dB and Noise Factor 1.22dB) and Device 2 (Gain 10.4dB and Noise Factor 0.90dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.635 | -170.5° | 2.443 | 21.5° | 0.075 | 1.0° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.32


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 40Ω resistor series with a 0.732 nH inductor, at 6.5 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.700 + j \cdot 0.790$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.05\text{dB}$, two matched amplifiers $G_1 = 9.2\text{dB}$ and $G_2 = 10.4\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.5dB). Assume the input power is 2.40mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

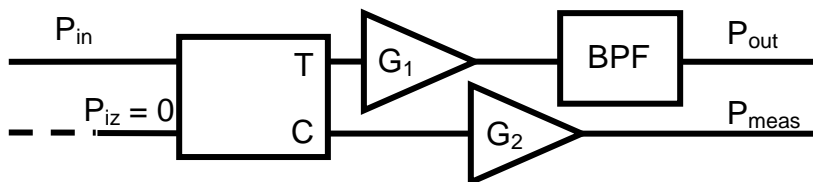

- A 50Ω source is connected to a $43.8\Omega + j \cdot 60.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.8dB and Noise Factor 1.14dB) and Device 2 (Gain 10.5dB and Noise Factor 1.05dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.4 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.636 | 139.8° | 1.686 | -27.8° | 0.090 | -32.8° | 0.550 | -153.6° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 33


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 62Ω resistor paralel with a 0.549 pF capacitor, at 6.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.130 - j\cdot 0.840$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.90\text{dB}$, two matched amplifiers $G_1 = 6.7\text{dB}$ and $G_2 = 9.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.0dB). Assume the input power is 2.00mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 20.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

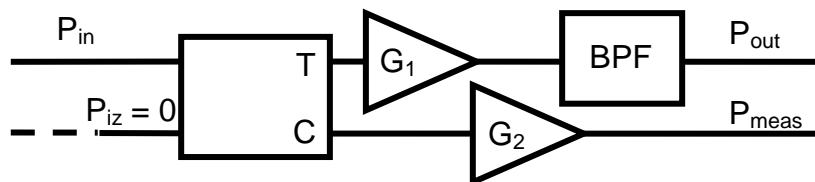

- A 50Ω source is connected to a $65.7\Omega - j\cdot 56.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.3dB and Noise Factor 1.16dB) and Device 2 (Gain 11.6dB and Noise Factor 0.94dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.9 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.603 | 121.2° | 1.618 | -46.7° | 0.099 | -41.2° | 0.559 | -167.1° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 34


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 53Ω resistor paralel with a 1.198 nH inductor, at 6.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.160 - j \cdot 1.010$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.85\text{dB}$, two matched amplifiers $G_1 = 8.3\text{dB}$ and $G_2 = 8.0\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.6dB). Assume the input power is 3.65mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.9dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

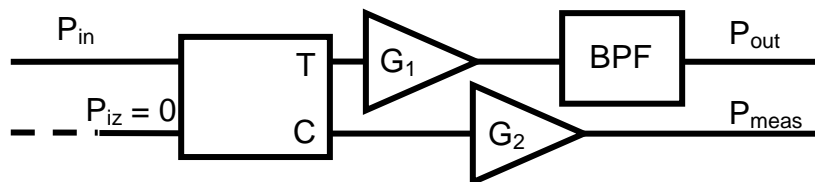

- A 50Ω source is connected to a $67.5\Omega - j \cdot 47.8\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.0dB and Noise Factor 1.14dB) and Device 2 (Gain 10.8dB and Noise Factor 0.95dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.633 | 135.9° | 1.669 | -31.4° | 0.090 | -33.4° | 0.550 | -156.3° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 35


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 42Ω resistor paralel with a 0.357 pF capacitor, at 8.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.970 - j\cdot 0.775$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.25\text{dB}$, two matched amplifiers $G_1 = 9.9\text{dB}$ and $G_2 = 8.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.5dB). Assume the input power is 2.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 15.5dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

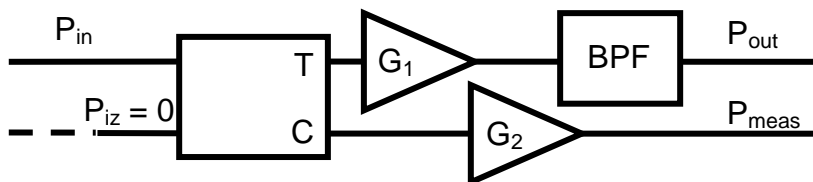

- A 50Ω source is connected to a $61.9\Omega + j\cdot 69.7\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.0dB and Noise Factor 1.20dB) and Device 2 (Gain 11.9dB and Noise Factor 0.98dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 14.2 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.624 | 129.6° | 1.644 | -37.6° | 0.092 | -35.6° | 0.552 | -160.8° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 36


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 58Ω resistor paralel with a 0.370 pF capacitor, at 9.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.290 + j \cdot 1.015$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.50\text{dB}$, two matched amplifiers $G_1 = 6.8\text{dB}$ and $G_2 = 9.6\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.4dB). Assume the input power is 2.35mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 18.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

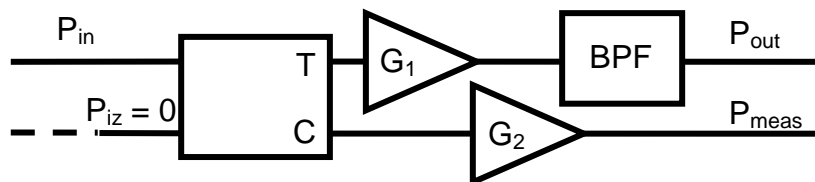

- A 50Ω source is connected to a $42.1\Omega + j \cdot 46.1\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.14dB) and Device 2 (Gain 10.2dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.3 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.637 | 141.1° | 1.692 | -26.6° | 0.090 | -32.6° | 0.550 | -152.7° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.37


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

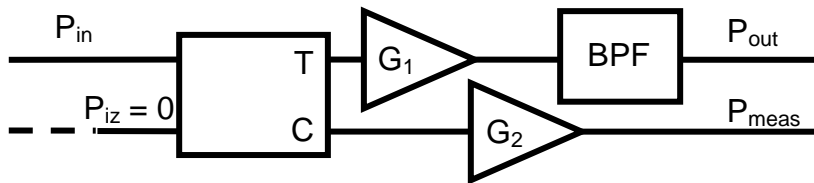1. For a load composed from a 31 Ω resistor paralel with a 0.817 nH inductor, at 6.8 GHz, compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
2. For a normalized admittance equal to $1.010 - j \cdot 0.920$ compute the impedance. (**1p**)
3. A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.15\text{dB}$, two matched amplifiers $G_1 = 8.4\text{dB}$ and $G_2 = 8.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.1dB). Assume the input power is 4.00mW.
 - a) Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - b) Compute the power at the measurement port P_{meas} (**0.5p**)
 - c) Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)



4. A 50Ω source is connected to a $33.1\Omega + j \cdot 53.7\Omega$ load .
 - a) Compute the reflection coefficient seen by the source. (**0.5p**)
 - b) Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - c) **Draw** the match schematic. (**0.5p**)
5. You must design a LNA using two amplifiers: Device 1 (Gain 9.9dB and Noise Factor 1.14dB) and Device 2 (Gain 11.8dB and Noise Factor 1.09dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
6. The scattering parameters of a transistor at 14.1 GHz are as follows:

| S ₁₁ | | S ₁₂ | | S ₂₁ | | S ₂₂ | |
|-----------------|--------|-----------------|--------|-----------------|--------|-----------------|---------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.627 | 130.8° | 1.648 | -36.3° | 0.091 | -34.8° | 0.551 | -159.9° |

- a) Prove that you can design a match for maximum gain (**0.5p**)
- b) Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- c) Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.38


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 45Ω resistor paralel with a 0.278 pF capacitor, at 8.3 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.980 + j\cdot 0.970$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.70\text{dB}$, two matched amplifiers $G_1 = 9.0\text{dB}$ and $G_2 = 9.7\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.5dB). Assume the input power is 1.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

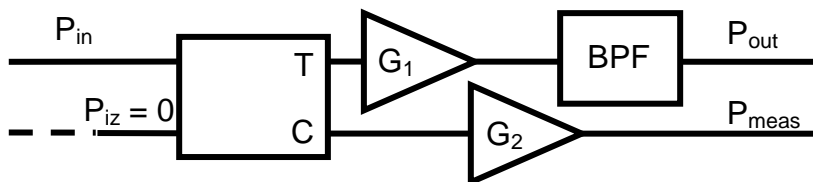

- A 50Ω source is connected to a $61.1\Omega + j\cdot 68.9\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.8dB and Noise Factor 1.22dB) and Device 2 (Gain 10.4dB and Noise Factor 0.98dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.3 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.611 | 178.5° | 2.342 | 11.1° | 0.080 | -2.5° | 0.520 | -111.7° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 39


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

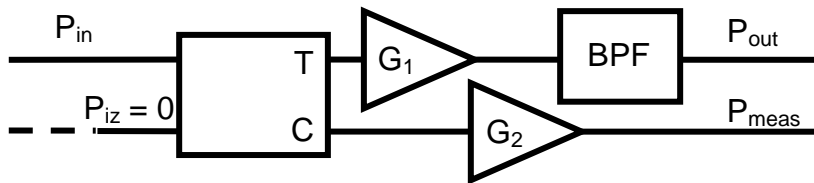1. For a load composed from a 67 Ω resistor paralel with a 0.275 pF capacitor, at 9.1 GHz, compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
2. For a normalized admittance equal to $0.920 - j \cdot 1.225$ compute the impedance. (**1p**)
3. A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.10\text{dB}$, two matched amplifiers $G_1 = 9.6\text{dB}$ and $G_2 = 8.5\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.8dB). Assume the input power is 2.05mW.
 - a) Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - b) Compute the power at the measurement port P_{meas} (**0.5p**)
 - c) Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)



4. A 50Ω source is connected to a $52.3\Omega + j \cdot 33.6\Omega$ load .
 - a) Compute the reflection coefficient seen by the source. (**0.5p**)
 - b) Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - c) **Draw** the match schematic. (**0.5p**)
5. You must design a LNA using two amplifiers: Device 1 (Gain 9.6dB and Noise Factor 1.14dB) and Device 2 (Gain 11.3dB and Noise Factor 1.01dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
6. The scattering parameters of a transistor at 14.0 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.630 | 132.0° | 1.652 | -35.0° | 0.090 | -34.0° | 0.550 | -159.0° |

- a) Prove that you can design a match for maximum gain (**0.5p**)
- b) Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- c) Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 40


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 39Ω resistor series with a 0.823 pF capacitor, at 7.6 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.805 - j \cdot 1.050$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.85\text{ dB}$, two matched amplifiers $G_1 = 6.9\text{ dB}$ and $G_2 = 8.4\text{ dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.9 dB). Assume the input power is 4.00 mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 16.1 dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

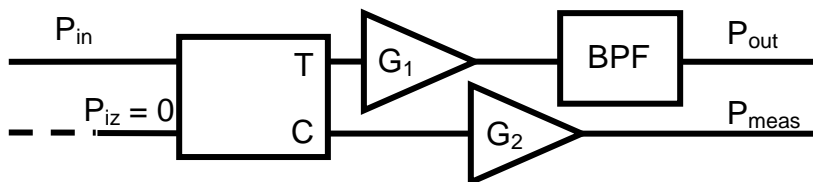

- A 50Ω source is connected to a $50.9\Omega - j \cdot 64.5\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.4 dB and Noise Factor 1.24 dB) and Device 2 (Gain 11.2 dB and Noise Factor 1.08 dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 9.1 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.647 | -165.3° | 2.495 | 26.7° | 0.071 | 2.6° | 0.520 | -109.0° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 41


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 45Ω resistor paralel with a 0.428 pF capacitor, at 8.9 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.130 - j\cdot 0.915$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.45\text{dB}$, two matched amplifiers $G_1 = 7.1\text{dB}$ and $G_2 = 11.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.7dB). Assume the input power is 2.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 18.1dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

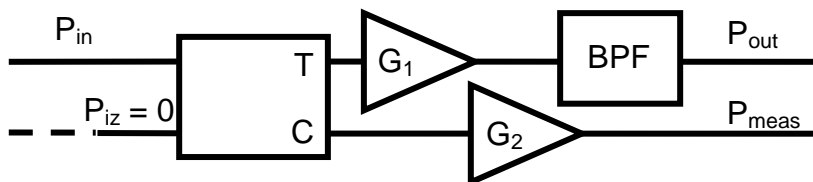

- A 50Ω source is connected to a $60.2\Omega + j\cdot 49.2\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.5dB and Noise Factor 1.25dB) and Device 2 (Gain 11.2dB and Noise Factor 0.94dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.659 | -160.1° | 2.559 | 32.2° | 0.070 | 4.8° | 0.517 | -103.3° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.42


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 33Ω resistor paralel with a 0.775 nH inductor, at 7.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.880 - j \cdot 1.205$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.75\text{dB}$, two matched amplifiers $G_1 = 6.5\text{dB}$ and $G_2 = 10.6\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 0.9dB). Assume the input power is 3.15mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.9dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

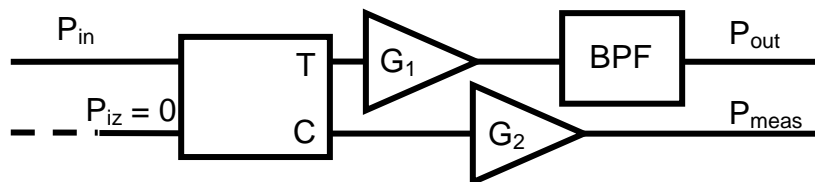

- A 50Ω source is connected to a $64.0\Omega + j \cdot 52.7\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.1dB and Noise Factor 1.21dB) and Device 2 (Gain 10.4dB and Noise Factor 1.03dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.1 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.639 | 143.7° | 1.703 | -24.2° | 0.090 | -32.2° | 0.550 | -150.9° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 43


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 46Ω resistor paralel with a 0.488 pF capacitor, at 9.4 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.870 + j \cdot 1.140$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.90\text{dB}$, two matched amplifiers $G_1 = 8.6\text{dB}$ and $G_2 = 10.3\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.3dB). Assume the input power is 2.15mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 23.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

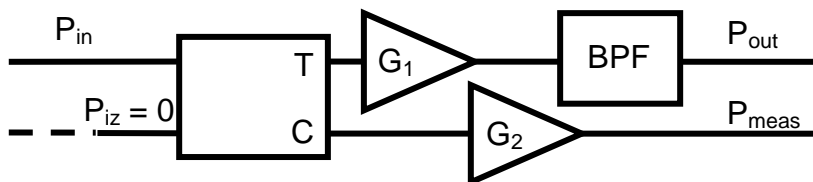

- A 50Ω source is connected to a $48.2\Omega - j \cdot 67.5\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.9dB and Noise Factor 1.25dB) and Device 2 (Gain 11.5dB and Noise Factor 0.97dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|-------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.605 | 175.5° | 2.318 | 8.5° | 0.080 | -3.5° | 0.520 | -113.5° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 44


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 41Ω resistor paralel with a 0.476 pF capacitor, at 6.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.010 - j \cdot 0.920$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 6.25\text{dB}$, two matched amplifiers $G_1 = 6.3\text{dB}$ and $G_2 = 11.8\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.9dB). Assume the input power is 3.45mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 23.8dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

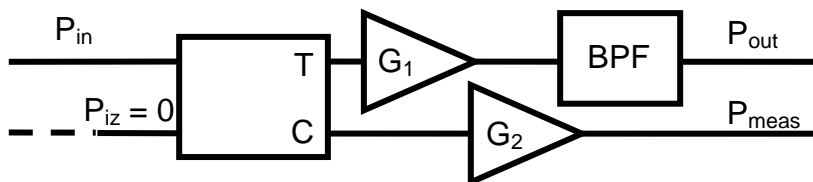

- A 50Ω source is connected to a $31.1\Omega - j \cdot 51.0\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.8dB and Noise Factor 1.21dB) and Device 2 (Gain 10.0dB and Noise Factor 0.93dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.4 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|-------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.608 | 177.0° | 2.330 | 9.8° | 0.080 | -3.0° | 0.520 | -112.6° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 45


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 44Ω resistor parallel with a 0.490 pF capacitor, at 10.0 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.740 + j \cdot 1.175$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.60\text{dB}$, two matched amplifiers $G_1 = 6.4\text{dB}$ and $G_2 = 9.7\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.1dB). Assume the input power is 1.65mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

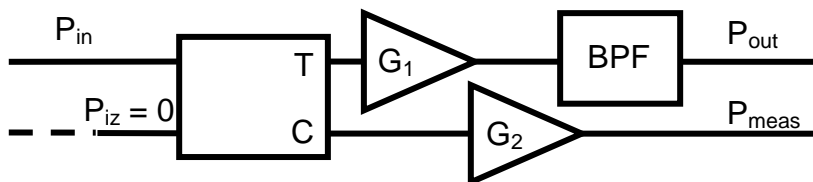

- A 50Ω source is connected to a $69.9\Omega + j \cdot 42.2\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.3dB and Noise Factor 1.20dB) and Device 2 (Gain 11.5dB and Noise Factor 0.91dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 8.4 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|----------------|----------|--------------|----------|-------------|----------|---------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.668 | -156.2° | 2.610 | 36.4° | 0.070 | 6.6° | 0.514 | -97.6° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 46


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

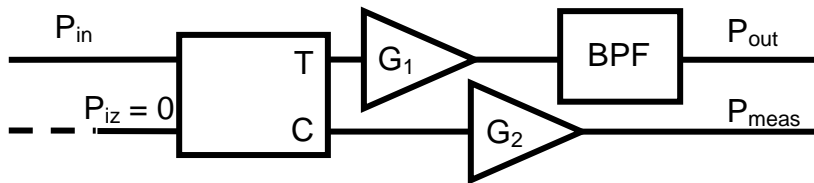1. For a load composed from a 48 Ω resistor series with a 0.334 pF capacitor, at 9.6 GHz, compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
2. For a normalized admittance equal to $0.815 - j \cdot 1.040$ compute the impedance. (**1p**)
3. A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.55\text{dB}$, two matched amplifiers $G_1 = 8.4\text{dB}$ and $G_2 = 9.1\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.2dB). Assume the input power is 3.30mW.
 - a) Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - b) Compute the power at the measurement port P_{meas} (**0.5p**)
 - c) Assume the same input signal is outside the filter passband at a frequency where the filter provides a 19.3dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)



4. A 50Ω source is connected to a $32.0\Omega - j \cdot 32.1\Omega$ load .
 - a) Compute the reflection coefficient seen by the source. (**0.5p**)
 - b) Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - c) **Draw** the match schematic. (**0.5p**)
5. You must design a LNA using two amplifiers: Device 1 (Gain 9.8dB and Noise Factor 1.16dB) and Device 2 (Gain 10.0dB and Noise Factor 0.93dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
6. The scattering parameters of a transistor at 14.8 GHz are as follows:

| S ₁₁ | | S ₁₂ | | S ₂₁ | | S ₂₂ | |
|-----------------|--------|-----------------|--------|-----------------|--------|-----------------|---------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.606 | 122.4° | 1.622 | -45.4° | 0.098 | -40.4° | 0.558 | -166.2° |

- a) Prove that you can design a match for maximum gain (**0.5p**)
- b) Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- c) Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 47


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 49Ω resistor paralel with a 0.371 pF capacitor, at 7.5 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.930 - j \cdot 1.070$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.65\text{dB}$, two matched amplifiers $G_1 = 7.1\text{dB}$ and $G_2 = 9.9\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.5dB). Assume the input power is 2.35mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 21.6dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

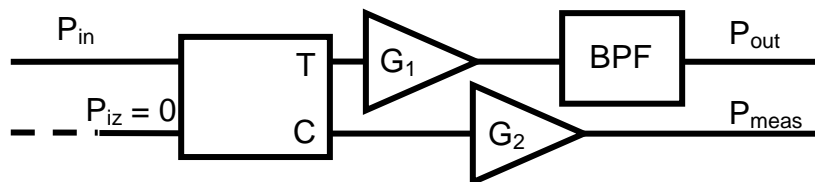

- A 50Ω source is connected to a $40.3\Omega - j \cdot 67.5\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.2dB and Noise Factor 1.19dB) and Device 2 (Gain 10.9dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.7 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|-------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.599 | 172.5° | 2.294 | 5.9° | 0.080 | -4.5° | 0.520 | -115.3° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 48


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 40Ω resistor series with a 0.394 pF capacitor, at 7.7 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $1.295 + j \cdot 1.230$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 5.45\text{dB}$, two matched amplifiers $G_1 = 8.6\text{dB}$ and $G_2 = 8.7\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 1.2dB). Assume the input power is 3.05mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 22.2dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

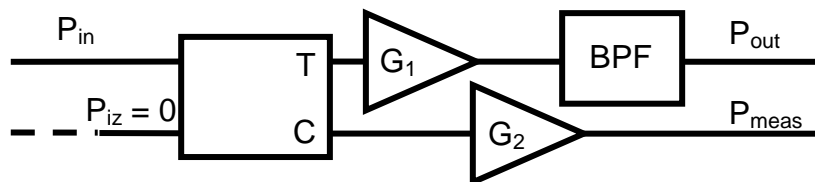

- A 50Ω source is connected to a $69.3\Omega + j \cdot 30.6\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 9.4dB and Noise Factor 1.13dB) and Device 2 (Gain 11.0dB and Noise Factor 0.93dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.8 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.632 | 134.6° | 1.663 | -32.6° | 0.090 | -33.6° | 0.550 | -157.2° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No. 49


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 40Ω resistor paralel with a 0.303 pF capacitor, at 8.0 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.765 + j \cdot 1.135$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.35\text{dB}$, two matched amplifiers $G_1 = 7.3\text{dB}$ and $G_2 = 11.6\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.9dB). Assume the input power is 1.85mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 19.4dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

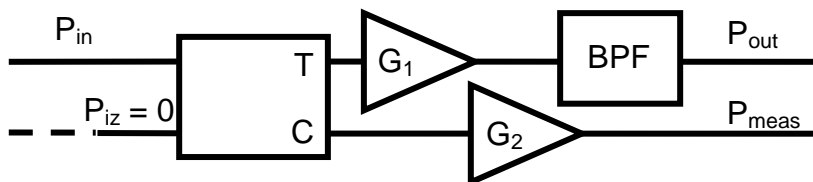

- A 50Ω source is connected to a $45.0\Omega + j \cdot 57.8\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.2dB and Noise Factor 1.24dB) and Device 2 (Gain 11.8dB and Noise Factor 1.03dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 13.5 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|---------------|----------|---------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.635 | 138.5° | 1.681 | -29.0° | 0.090 | -33.0° | 0.550 | -154.5° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2022

SUBJECT No.50


Time allowed: 2 hours; All materials/equipments authorized

Instructor: assoc. prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a load composed from a 25Ω resistor series with a 0.717 pF capacitor, at 7.8 GHz , compute the corresponding reflection coefficient (**1p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**1p**).
- For a normalized admittance equal to $0.745 + j \cdot 1.165$ compute the impedance. (**1p**)
- A measurement system contains an ideal lossless coupler (wide bandwidth, matched on all ports with infinite isolation) with a coupling factor $C = 4.65\text{dB}$, two matched amplifiers $G_1 = 7.4\text{dB}$ and $G_2 = 8.2\text{dB}$ and a band-pass filter (equal ripple filter with a ripple equal to 2.3dB). Assume the input power is 3.95mW .
 - Compute the minimum and maximum power at the output port P_{out} (**in mW**) for signals inside the filter passband (**2p**)
 - Compute the power at the measurement port P_{meas} (**0.5p**)
 - Assume the same input signal is outside the filter passband at a frequency where the filter provides a 23.7dB attenuation. Compute the power at the output port P_{out} (**in mW**) (**1p**)

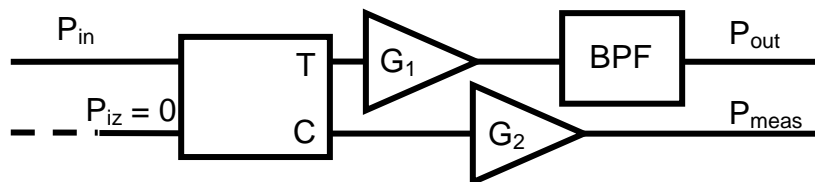

- A 50Ω source is connected to a $64.1\Omega + j \cdot 38.2\Omega$ load .
 - Compute the reflection coefficient seen by the source. (**0.5p**)
 - Design the match with single-stub matching sections (shunt stub, both solutions). (**1.5p**)
 - Draw** the match schematic. (**0.5p**)
- You must design a LNA using two amplifiers: Device 1 (Gain 8.4dB and Noise Factor 1.29dB) and Device 2 (Gain 11.7dB and Noise Factor 1.04dB). Which is the best order to place the two devices? Compute the gain and the noise factor of the cascaded schematic. (**1p**)
- The scattering parameters of a transistor at 10.2 GHz are as follows:

| S_{11} | | S_{12} | | S_{21} | | S_{22} | |
|----------|---------------|----------|--------------|----------|--------------|----------|----------------|
| Mag. | Ang. | Mag. | Ang. | Mag. | Ang. | Mag. | Ang. |
| 0.614 | 180.0° | 2.354 | 12.4° | 0.080 | -2.0° | 0.520 | -110.8° |

- Prove that you can design a match for maximum gain (**0.5p**)
- Compute the reflection coefficients required towards the source and the load for maximum gain (**1.5p**)
- Design the match at both input and output with single-stub matching sections (shunt stub solution) (**1.5p**)

