

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 1

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 37Ω resistor paralel with a 1.15nH inductor, at 7.1GHz, compute the normalized admittance (**1p**) and the normalized impedance (**1p**).
2. For a normalized impedance equal to $0.880 + j \cdot 1.020$ compute the corresponding reflection coefficient (**0.5p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**0.5p**).
3. A quarter wave transformer is designed to match a 26Ω load to a 50Ω source at 7.3GHz. Which is the impedance seen by the source at 2.9 GHz. (**2p**)
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.35\text{nH/cm}$ and $C = 2.65\text{pF/cm}$, is used as a capacitor at 8.3GHz. Find the value of the capacitance. (**2p**).
5. The scattering parameters of a transistor at 12.3 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	154.1°	0	0°	1.749	-13.9°	0.550	-143.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. (**1.5p**)
- b) Draw the match schematic. (**0.5p**)
- c) Which is the transducer power gain we obtain in this case (in dB)? (**1p**)
- d) For a 135μW input signal compute the power of the output signal (both mW and dBm). (**1p**)
- e) If however you know the real value of $S_{12} = 0.090 \angle -28.5^\circ$ check whether the transistor is stable with the match you designed at a). (**1p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.2

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 50Ω resistor series with a 0.78nH inductor, at 8.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.730 - j0.990$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 50Ω load to a 50Ω source at 9.0GHz. Which is the impedance seen by the source at 3.6 GHz. **(2p)**
4. A $\lambda/10$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.30\text{nH/cm}$ and $C = 3.20\text{pF/cm}$, is used as a capacitor at 12.4GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 9.7 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.692	-167.8°	0	0°	1.966	21.2°	0.560	-118.3°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 135μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.080 \angle -13.9^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 3

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 25Ω resistor series with a 1.00nH inductor, at 9.4GHz, compute the normalized admittance (**1p**) and the normalized impedance (**1p**).
2. For a normalized impedance equal to $0.895 - j \cdot 0.750$ compute the corresponding reflection coefficient (**0.5p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**0.5p**).
3. A quarter wave transformer is designed to match a 41Ω load to a 50Ω source at 6.7GHz. Which is the impedance seen by the source at 3.9 GHz. (**2p**)
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.50\text{nH/cm}$ and $C = 1.95\text{pF/cm}$, is used as a capacitor at 14.0GHz. Find the value of the capacitance. (**2p**).
5. The scattering parameters of a transistor at 14.7 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.688	103.7°	0	0°	1.686	-27.7°	0.298	153.2°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. (**1.5p**)
- b) Draw the match schematic. (**0.5p**)
- c) Which is the transducer power gain we obtain in this case (in dB)? (**1p**)
- d) For a 105μW input signal compute the power of the output signal (both mW and dBm). (**1p**)
- e) If however you know the real value of $S_{12} = 0.137 \angle 4.5^\circ$ check whether the transistor is stable with the match you designed at a). (**1p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 4

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 63Ω resistor paralel with a 1.13nH inductor, at 9.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.025 - j \cdot 1.000$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 37Ω load to a 50Ω source at 7.0GHz. Which is the impedance seen by the source at 4.0 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.90\text{nH/cm}$ and $C = 2.80\text{pF/cm}$, is used as a capacitor at 12.9GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.5 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.660	173.0°	0	0°	1.810	-3.0°	0.555	-135.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 130μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -24.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.5

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 61Ω resistor series with a 1.32nH inductor, at 6.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.290 + j \cdot 0.970$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 35Ω load to a 50Ω source at 7.1GHz. Which is the impedance seen by the source at 2.2 GHz. **(2p)**
4. A $\lambda/13$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.80\text{nH/cm}$ and $C = 4.85\text{pF/cm}$, is used as a capacitor at 14.4GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.8 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.871	6.6°	0.560	-128.2°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 140μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.088 \angle -20.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 6

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 25Ω resistor paralel with a 0.56pF capacitor, at 7.2GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.740 - j \cdot 1.055$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 50Ω load to a 50Ω source at 7.7GHz. Which is the impedance seen by the source at 2.4 GHz. **(2p)**
4. A $\lambda/6$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.45\text{nH/cm}$ and $C = 3.65\text{pF/cm}$, is used as a capacitor at 7.6GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.854	4.0°	0.560	-130.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 75μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -21.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.7

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 58Ω resistor paralel with a 0.26pF capacitor, at 9.6GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.725 - j0.800$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 43Ω load to a 50Ω source at 9.5GHz. Which is the impedance seen by the source at 2.0 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.55\text{nH/cm}$ and $C = 1.80\text{pF/cm}$, is used as a capacitor at 14.6GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	158.0°	0	0°	1.766	-10.0°	0.550	-140.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 110μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -27.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 8

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 57Ω resistor paralel with a 0.55nH inductor, at 8.6GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.190 + j \cdot 1.025$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 72Ω load to a 50Ω source at 8.8GHz. Which is the impedance seen by the source at 3.8 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.15\text{nH/cm}$ and $C = 2.00\text{pF/cm}$, is used as a capacitor at 10.1GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.7 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.880	7.9°	0.560	-127.3°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 120μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.087 \angle -19.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 9

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 68Ω resistor series with a 0.49nH inductor, at 8.3GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.815 - j \cdot 1.280$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 63Ω load to a 50Ω source at 7.1GHz. Which is the impedance seen by the source at 2.7 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.75\text{nH/cm}$ and $C = 4.60\text{pF/cm}$, is used as a capacitor at 9.3GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.7 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	148.9°	0	0°	1.726	-19.1°	0.550	-147.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 125μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -30.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.10

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 55Ω resistor paralel with a 0.71nH inductor, at 8.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.935 - j \cdot 0.740$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 48Ω load to a 50Ω source at 9.5GHz. Which is the impedance seen by the source at 3.5 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.45\text{nH/cm}$ and $C = 1.65\text{pF/cm}$, is used as a capacitor at 12.8GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.4 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.906	11.8°	0.560	-124.6°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 120μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.084 \angle -18.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 11

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 50Ω resistor series with a 0.99nH inductor, at 7.0GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.925 + j \cdot 1.175$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 27Ω load to a 50Ω source at 10.0GHz. Which is the impedance seen by the source at 4.1 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.60\text{nH/cm}$ and $C = 2.30\text{pF/cm}$, is used as a capacitor at 11.2GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.4 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.676	106.4°	0	0°	1.722	-24.4°	0.286	157.4°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 55μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.134 \angle 6.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.12

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 32Ω resistor series with a 0.38pF capacitor, at 8.9GHz, compute the normalized admittance (**1p**) and the normalized impedance (**1p**).
2. For a normalized impedance equal to $1.025 - j0.925$ compute the corresponding reflection coefficient (**0.5p**) and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point (**0.5p**).
3. A quarter wave transformer is designed to match a 57Ω load to a 50Ω source at 8.8GHz. Which is the impedance seen by the source at 3.4 GHz. (**2p**)
4. A $\lambda/13$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.60\text{nH/cm}$ and $C = 4.65\text{pF/cm}$, is used as a capacitor at 7.3GHz. Find the value of the capacitance. (**2p**).
5. The scattering parameters of a transistor at 10.6 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.888	9.2°	0.560	-126.4°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. (**1.5p**)
- b) Draw the match schematic. (**0.5p**)
- c) Which is the transducer power gain we obtain in this case (in dB)? (**1p**)
- d) For a 50μW input signal compute the power of the output signal (both mW and dBm). (**1p**)
- e) If however you know the real value of $S_{12} = 0.086\angle -19.0^\circ$ check whether the transistor is stable with the match you designed at a). (**1p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No. 13

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 67Ω resistor series with a 0.25pF capacitor, at 8.9GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.720 + j \cdot 1.185$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 47Ω load to a 50Ω source at 9.0GHz. Which is the impedance seen by the source at 2.9 GHz. **(2p)**
4. A $\lambda/8$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.40\text{nH/cm}$ and $C = 1.85\text{pF/cm}$, is used as a capacitor at 11.4GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 9.9 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.684	-170.6°	0	0°	1.948	18.4°	0.560	-120.1°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 70μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.080 \angle -15.3^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.14

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 57Ω resistor series with a 0.54nH inductor, at 9.7GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.050 + j \cdot 1.100$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 62Ω load to a 50Ω source at 7.0GHz. Which is the impedance seen by the source at 3.7 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.45\text{nH/cm}$ and $C = 4.30\text{pF/cm}$, is used as a capacitor at 11.2GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 13.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	145.0°	0	0°	1.709	-23.0°	0.550	-150.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 125μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -32.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.15

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 56Ω resistor series with a 0.37pF capacitor, at 7.0GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.755 + j \cdot 1.020$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 53Ω load to a 50Ω source at 9.9GHz. Which is the impedance seen by the source at 4.0 GHz. **(2p)**
4. A $\lambda/10$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.75\text{nH/cm}$ and $C = 3.55\text{pF/cm}$, is used as a capacitor at 13.8GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 9.8 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.688	-169.2°	0	0°	1.957	19.8°	0.560	-119.2°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 55μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.080 \angle -14.6^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 16

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 48Ω resistor paralel with a 0.30pF capacitor, at 7.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.265 - j \cdot 1.250$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 33Ω load to a 50Ω source at 8.1GHz. Which is the impedance seen by the source at 4.3 GHz. **(2p)**
4. A $\lambda/11$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.05\text{nH/cm}$ and $C = 2.75\text{pF/cm}$, is used as a capacitor at 13.1GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.6 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.684	104.6°	0	0°	1.698	-26.6°	0.294	154.6°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 145μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.136 \angle 5.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.17

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 59Ω resistor series with a 1.16nH inductor, at 9.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.070 - j0.865$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 71Ω load to a 50Ω source at 7.3GHz. Which is the impedance seen by the source at 2.8 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.60\text{nH/cm}$ and $C = 1.40\text{pF/cm}$, is used as a capacitor at 14.2GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.5 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.897	10.5°	0.560	-125.5°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 80μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.085 \angle -18.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.18

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 28Ω resistor series with a 1.14nH inductor, at 7.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.865 + j \cdot 1.135$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 27Ω load to a 50Ω source at 7.4GHz. Which is the impedance seen by the source at 2.8 GHz. **(2p)**
4. A $\lambda/8$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.50\text{nH/cm}$ and $C = 4.85\text{pF/cm}$, is used as a capacitor at 10.0GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.8 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.692	102.8°	0	0°	1.674	-28.8°	0.302	151.8°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 120μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.138 \angle 4.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No. 19

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 35Ω resistor paralel with a 0.60nH inductor, at 8.2GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.235 - j \cdot 0.760$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 26Ω load to a 50Ω source at 8.1GHz. Which is the impedance seen by the source at 2.9 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.90\text{nH/cm}$ and $C = 2.90\text{pF/cm}$, is used as a capacitor at 14.8GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.9 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	146.3°	0	0°	1.715	-21.7°	0.550	-149.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 70μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -31.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.20

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 68Ω resistor paralel with a 0.51nH inductor, at 8.7GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.025 + j \cdot 1.075$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 46Ω load to a 50Ω source at 9.7GHz. Which is the impedance seen by the source at 3.7 GHz. **(2p)**
4. A $\lambda/12$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.25\text{nH/cm}$ and $C = 4.70\text{pF/cm}$, is used as a capacitor at 14.7GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.5 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	105.5°	0	0°	1.710	-25.5°	0.290	156.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 75μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.135 \angle 5.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.21

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 31Ω resistor series with a 1.09nH inductor, at 8.4GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.005 - j0.820$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 57Ω load to a 50Ω source at 8.8GHz. Which is the impedance seen by the source at 2.5 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.95\text{nH/cm}$ and $C = 4.90\text{pF/cm}$, is used as a capacitor at 13.7GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.2 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.672	-178.0°	0	0°	1.836	1.2°	0.558	-132.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 100μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -22.2^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.22

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 56Ω resistor series with a 0.54nH inductor, at 9.4GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.180 + j \cdot 0.920$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 34Ω load to a 50Ω source at 7.7GHz. Which is the impedance seen by the source at 3.2 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.70\text{nH/cm}$ and $C = 1.60\text{pF/cm}$, is used as a capacitor at 9.0GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.1 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.676	-175.0°	0	0°	1.845	2.6°	0.559	-131.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 50μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -21.6^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.23

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 39Ω resistor paralel with a 0.66nH inductor, at 8.9GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.825 + j \cdot 1.075$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 68Ω load to a 50Ω source at 9.7GHz. Which is the impedance seen by the source at 3.1 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.55\text{nH/cm}$ and $C = 3.15\text{pF/cm}$, is used as a capacitor at 11.8GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.9 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.863	5.3°	0.560	-129.1°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 140μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.089 \angle -20.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.24

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 40Ω resistor paralel with a 1.19nH inductor, at 6.9GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.765 + j \cdot 0.710$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 46Ω load to a 50Ω source at 9.4GHz. Which is the impedance seen by the source at 2.1 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.15\text{nH/cm}$ and $C = 2.75\text{pF/cm}$, is used as a capacitor at 8.7GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.3 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.668	179.0°	0	0°	1.828	-0.2°	0.557	-133.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 85μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -22.8^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.25

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 61Ω resistor series with a 0.25pF capacitor, at 9.2GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.075 - j0.760$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 49Ω load to a 50Ω source at 9.0GHz. Which is the impedance seen by the source at 4.3 GHz. **(2p)**
4. A $\lambda/8$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.50\text{nH/cm}$ and $C = 4.00\text{pF/cm}$, is used as a capacitor at 9.6GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 9.6 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.696	-166.4°	0	0°	1.974	22.6°	0.560	-117.4°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 80μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.080 \angle -13.2^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.26

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 44Ω resistor series with a 1.24nH inductor, at 8.4GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.175 - j0.875$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 48Ω load to a 50Ω source at 7.8GHz. Which is the impedance seen by the source at 3.1 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.55\text{nH/cm}$ and $C = 2.50\text{pF/cm}$, is used as a capacitor at 13.5GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.6 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	150.2°	0	0°	1.732	-17.8°	0.550	-146.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 120μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -30.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.27

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 72Ω resistor paralel with a 0.83nH inductor, at 8.4GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.745 + j \cdot 0.985$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 74Ω load to a 50Ω source at 9.8GHz. Which is the impedance seen by the source at 3.8 GHz. **(2p)**
4. A $\lambda/12$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.20\text{nH/cm}$ and $C = 3.65\text{pF/cm}$, is used as a capacitor at 8.2GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.2 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.668	108.2°	0	0°	1.746	-22.2°	0.278	160.2°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 100μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.132 \angle 7.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.28

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 55Ω resistor paralel with a 1.62nH inductor, at 7.0GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.860 + j \cdot 1.220$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 47Ω load to a 50Ω source at 8.2GHz. Which is the impedance seen by the source at 3.1 GHz. **(2p)**
4. A $\lambda/8$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.55\text{nH/cm}$ and $C = 4.20\text{pF/cm}$, is used as a capacitor at 7.7GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 15.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.700	101.0°	0	0°	1.650	-31.0°	0.310	149.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 85μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.140 \angle 3.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.29

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 32Ω resistor paralel with a 1.31nH inductor, at 6.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.020 - j \cdot 0.765$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 59Ω load to a 50Ω source at 6.6GHz. Which is the impedance seen by the source at 4.0 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.20\text{nH/cm}$ and $C = 4.70\text{pF/cm}$, is used as a capacitor at 10.1GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.9 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.644	161.0°	0	0°	1.775	-8.6°	0.551	-139.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 100μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -26.4^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.30

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 52Ω resistor series with a 0.48pF capacitor, at 7.4GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.900 - j0.900$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 36Ω load to a 50Ω source at 9.3GHz. Which is the impedance seen by the source at 2.8 GHz. **(2p)**
4. A $\lambda/13$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.30\text{nH/cm}$ and $C = 3.70\text{pF/cm}$, is used as a capacitor at 12.2GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.660	110.0°	0	0°	1.770	-20.0°	0.270	163.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 85μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.130\angle 8.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.31

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 36Ω resistor paralel with a 1.16nH inductor, at 9.9GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.105 + j \cdot 0.765$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 72Ω load to a 50Ω source at 9.7GHz. Which is the impedance seen by the source at 2.2 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.75\text{nH/cm}$ and $C = 3.30\text{pF/cm}$, is used as a capacitor at 11.4GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.3 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.914	13.1°	0.560	-123.7°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 145μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.083 \angle -17.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.32

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 46Ω resistor paralel with a 0.60pF capacitor, at 6.7GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.835 + j \cdot 0.830$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 72Ω load to a 50Ω source at 10.0GHz. Which is the impedance seen by the source at 2.1 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.70\text{nH/cm}$ and $C = 1.60\text{pF/cm}$, is used as a capacitor at 9.3GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.8 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	147.6°	0	0°	1.720	-20.4°	0.550	-148.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 50μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -31.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.33

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 25Ω resistor series with a 0.30pF capacitor, at 7.8GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.290 - j \cdot 0.755$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 60Ω load to a 50Ω source at 7.0GHz. Which is the impedance seen by the source at 2.0 GHz. **(2p)**
4. A $\lambda/7$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.95\text{nH/cm}$ and $C = 3.10\text{pF/cm}$, is used as a capacitor at 14.9GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.3 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.672	107.3°	0	0°	1.734	-23.3°	0.282	158.8°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 55μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.133 \angle 6.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.34

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 58Ω resistor series with a 1.75nH inductor, at 6.5GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.870 + j \cdot 0.705$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 64Ω load to a 50Ω source at 8.2GHz. Which is the impedance seen by the source at 2.9 GHz. **(2p)**
4. A $\lambda/6$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.60\text{nH/cm}$ and $C = 1.60\text{pF/cm}$, is used as a capacitor at 8.1GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.4 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.664	176.0°	0	0°	1.819	-1.6°	0.556	-134.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 60μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -23.4^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.35

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 66Ω resistor paralel with a 0.54nH inductor, at 7.8GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.290 - j0.765$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 55Ω load to a 50Ω source at 8.5GHz. Which is the impedance seen by the source at 4.1 GHz. **(2p)**
4. A $\lambda/14$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.00\text{nH/cm}$ and $C = 3.50\text{pF/cm}$, is used as a capacitor at 8.8GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 12.5 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.640	151.5°	0	0°	1.737	-16.5°	0.550	-145.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 55μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -29.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.36

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 42Ω resistor paralel with a 0.94nH inductor, at 7.1GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.045 - j \cdot 1.195$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 48Ω load to a 50Ω source at 9.3GHz. Which is the impedance seen by the source at 2.4 GHz. **(2p)**
4. A $\lambda/10$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.80\text{nH/cm}$ and $C = 2.00\text{pF/cm}$, is used as a capacitor at 7.6GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 13.3 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.637	141.1°	0	0°	1.692	-26.6°	0.550	-152.7°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 65μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -32.6^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.37

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 38Ω resistor paralel with a 0.26pF capacitor, at 9.7GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.935 + j \cdot 1.065$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 73Ω load to a 50Ω source at 9.1GHz. Which is the impedance seen by the source at 4.4 GHz. **(2p)**
4. A $\lambda/9$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.20\text{nH/cm}$ and $C = 1.30\text{pF/cm}$, is used as a capacitor at 10.1GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 10.0 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.680	-172.0°	0	0°	1.940	17.0°	0.560	-121.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 70μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.080 \angle -16.0^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.38

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 44Ω resistor series with a 0.48nH inductor, at 8.8GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.885 - j0.875$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 57Ω load to a 50Ω source at 7.5GHz. Which is the impedance seen by the source at 2.2 GHz. **(2p)**
4. A $\lambda/8$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 2.05\text{nH/cm}$ and $C = 2.50\text{pF/cm}$, is used as a capacitor at 8.0GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 14.1 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.664	109.1°	0	0°	1.758	-21.1°	0.274	161.6°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 110μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.131 \angle 7.5^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____ / ___2019

SUBJECT No.39

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 72Ω resistor series with a 0.62pF capacitor, at 9.0GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $1.060 + j \cdot 0.940$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 56Ω load to a 50Ω source at 7.4GHz. Which is the impedance seen by the source at 3.0 GHz. **(2p)**
4. A $\lambda/11$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.00\text{nH/cm}$ and $C = 1.20\text{pF/cm}$, is used as a capacitor at 8.5GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 11.7 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.652	167.0°	0	0°	1.792	-5.8°	0.553	-137.0°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 105μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -25.2^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDOS412T

Enrollment Year: ___4___, Examination Session _____January_____/ __2019

SUBJECT No.40

Time allowed: 2 hours; All materials/equipments authorized

Instructor: conf. Radu Damian Student: _____ Grupa _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must be accompanied by the submission of the script/project at the end of the examination.

1. For a load composed from a 26Ω resistor series with a 0.67nH inductor, at 9.8GHz, compute the normalized admittance **(1p)** and the normalized impedance **(1p)**.
2. For a normalized impedance equal to $0.900 - j0.990$ compute the corresponding reflection coefficient **(0.5p)** and then plot on a Smith Chart (only the external circle and the complex plane axes) the corresponding point **(0.5p)**.
3. A quarter wave transformer is designed to match a 65Ω load to a 50Ω source at 8.2GHz. Which is the impedance seen by the source at 3.0 GHz. **(2p)**
4. A $\lambda/12$ section of an open-circuited transmission line, with parameters (per unit length) $R = G = 0$, $L = 1.30\text{nH/cm}$ and $C = 4.65\text{pF/cm}$, is used as a capacitor at 11.7GHz. Find the value of the capacitance. **(2p)**.
5. The scattering parameters of a transistor at 13.2 GHz are as follows:

S_{11}		S_{12}		S_{21}		S_{22}	
Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
0.638	142.4°	0	0°	1.698	-25.4°	0.550	-151.8°

- a) Design the match at both input and output with single-stub matching sections (shunt stub solution) which offers maximum gain. **(1.5p)**
- b) Draw the match schematic. **(0.5p)**
- c) Which is the transducer power gain we obtain in this case (in dB)? **(1p)**
- d) For a 105μW input signal compute the power of the output signal (both mW and dBm). **(1p)**
- e) If however you know the real value of $S_{12} = 0.090 \angle -32.4^\circ$ check whether the transistor is stable with the match you designed at a). **(1p)**

