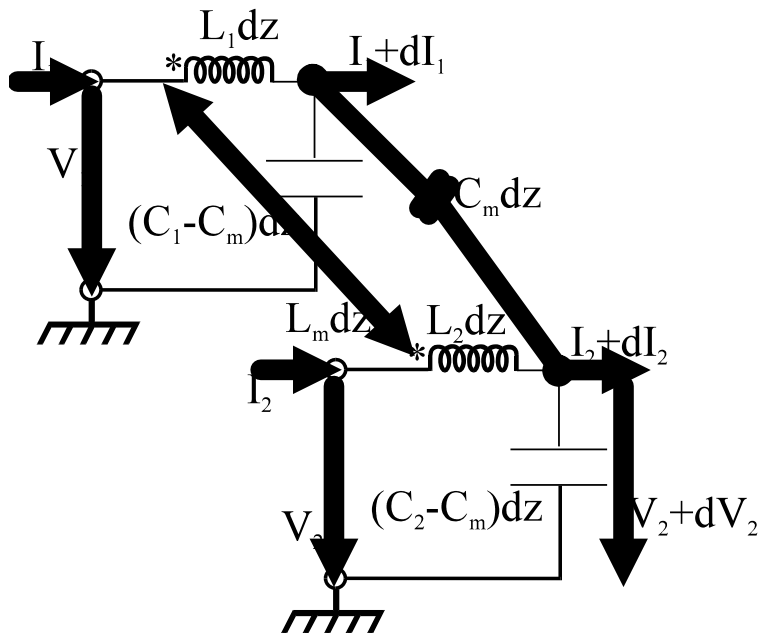


# LINII CUPLATE

# Ecuatiile diferențiale ale liniilor cuplate



$$\left\{ \begin{array}{l} -\frac{dV_1}{dz} = j\omega L_1 I_1 + j\omega L_m I_2 \\ -\frac{dV_2}{dz} = j\omega L_m I_1 + j\omega L_2 I_2 \\ -\frac{dI_1}{dz} = j\omega C_1 V_1 - j\omega C_m V_2 \\ -\frac{dI_2}{dz} = -j\omega C_m V_1 + j\omega C_2 V_2 \end{array} \right.$$

## Solutia ecuatiilor diferentiale

$$\left\{ \frac{d^2}{dz^2} - (j\omega)^2 [L][C] \right\} [V] = 0 \quad [C][L] = ([L][C])^T = \begin{bmatrix} L_1 C_1 - L_m C_m & C_1 L_m - C_m L_2 \\ -C_m L_1 + C_2 L_m & -L_m C_m + L_2 C_2 \end{bmatrix}$$

$$V = V_0 \cdot e^{-\gamma z}$$

$$\begin{cases} a_1 = (L_m C_m - L_1 C_1) \omega^2 \\ b_1 = (L_1 C_m - L_m C_2) \omega^2 \\ a_2 = (L_m C_m - L_2 C_2) \omega^2 \\ b_2 = -(L_m C_1 - L_2 C_m) \omega^2 \end{cases}$$

$$\gamma^4 - (a_1 + a_2) \gamma^2 + (a_1 a_2 - b_1 b_2) = 0$$

## Solutia ecuatiilor diferentiale-2

$$\gamma^4 - (a_1 + a_2)\gamma^2 + (a_1a_2 - b_1b_2) = 0$$

$$\gamma_{\pm}^2 = \frac{a_1 + a_2}{2} \pm \frac{1}{2} \sqrt{(a_1 - a_2)^2 + 4b_1b_2}$$

$$\left\{ \begin{array}{l} \gamma_+^2 \Rightarrow \left( \frac{V_2}{V_1} \right)_+ = \frac{1}{2b_1} \left[ (a_2 - a_1) + \sqrt{(a_2 - a_1)^2 + 4b_1b_2} \right] = R_+ \\ \gamma_-^2 \Rightarrow \left( \frac{V_2}{V_1} \right)_- = \frac{1}{2b_1} \left[ (a_2 - a_1) - \sqrt{(a_2 - a_1)^2 + 4b_1b_2} \right] = R_- \end{array} \right.$$

$$V_1 = A_1 \cdot e^{-\gamma_+ z} + A_2 \cdot e^{\gamma_+ z} + A_3 \cdot e^{-\gamma_- z} + A_4 \cdot e^{\gamma_- z}$$

$$V_2 = R_+ \left( A_1 \cdot e^{-\gamma_+ z} + A_2 \cdot e^{\gamma_+ z} \right) + R_- \left( A_3 \cdot e^{-\gamma_- z} + A_4 \cdot e^{\gamma_- z} \right)$$

# Linii simetrice

$$L_1 = L_2 = L_0$$

$$C_1 = C_2 = C_0$$

$$a_1 = a_2 = (L_m C_m - L_0 C_0) \omega^2 \quad \gamma_+^2 = a_1 + \sqrt{b_1 b_2} \stackrel{n}{=} \gamma_e^2$$

$$b_1 = b_2 = (L_0 C_m - L_m C_0) \omega^2 \quad \gamma_-^2 = a_1 - \sqrt{b_1 b_2} \stackrel{n}{=} \gamma_o^2$$


$$R_+ = \sqrt{\frac{b_2}{b_1}} = 1, R_- = -\sqrt{\frac{b_2}{b_1}} = -1$$

$$\begin{cases} V_1 = (A_1 \cdot e^{-\gamma_e z} + A_2 \cdot e^{\gamma_e z}) + (A_3 \cdot e^{-\gamma_o z} + A_4 \cdot e^{\gamma_o z}) \\ V_2 = (A_1 \cdot e^{-\gamma_e z} + A_2 \cdot e^{\gamma_e z}) - (A_3 \cdot e^{-\gamma_o z} + A_4 \cdot e^{\gamma_o z}) \\ I_1 = Y_{ce} (A_1 \cdot e^{-\gamma_e z} - A_2 \cdot e^{\gamma_e z}) + Y_{co} (A_3 \cdot e^{-\gamma_o z} - A_4 \cdot e^{\gamma_o z}) \\ I_2 = Y_{ce} (A_1 \cdot e^{-\gamma_e z} - A_2 \cdot e^{\gamma_e z}) - Y_{co} (A_3 \cdot e^{-\gamma_o z} - A_4 \cdot e^{\gamma_o z}) \end{cases}$$

$$\frac{j\omega\gamma_e (L_0 - L_m)}{D^2} = \frac{j\omega\gamma_e (L_0 - L_m)}{(j\omega)^2 (L_0^2 - L_m^2)} = \frac{-j\gamma_e}{(L_0 + L_m)\omega} \stackrel{n}{=} Y_{ce} =$$

$$\frac{j\omega\gamma_o (L_0 + L_m)}{D^2} = \frac{j\omega\gamma_o (L_0 + L_m)}{(j\omega)^2 (L_0^2 - L_m^2)} = \frac{-j\gamma_o}{(L_0 - L_m)\omega} \stackrel{n}{=} Y_{co} =$$
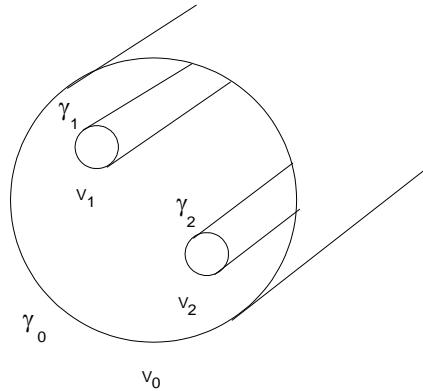
# Consideratii electromagnetice asupra liniilor cuplate



$$V(x, y) = V_1 U_1(x, y) + V_2 U_2(x, y)$$

$$\frac{\partial^2 U_i}{\partial x^2} + \frac{\partial^2 U_i}{\partial y^2} = 0, i = 1, 2$$

$$\begin{cases} U_1 = 1 \text{ pe } \gamma_1 \text{ si } 0 \text{ pe } \gamma_2 \\ U_2 = 0 \text{ pe } \gamma_1 \text{ si } 1 \text{ pe } \gamma_2 \end{cases}$$


$$U'_1 = U_1 + U_2 \quad U'_2 = U_1 - U_2$$

$$V = \frac{V_1 + V_2}{2} U'_1 + \frac{V_1 - V_2}{2} U'_2$$

$$\frac{\partial^2 U'_i}{\partial x^2} + \frac{\partial^2 U'_i}{\partial y^2} = 0, i = 1, 2$$


$$\begin{cases} U'_1 = 1 \text{ pe } \gamma_1, \gamma_2 \\ U'_2 = \begin{cases} 1 \text{ pe } \gamma_1 \\ -1 \text{ pe } \gamma_2 \end{cases} \end{cases}$$

# Exemplu

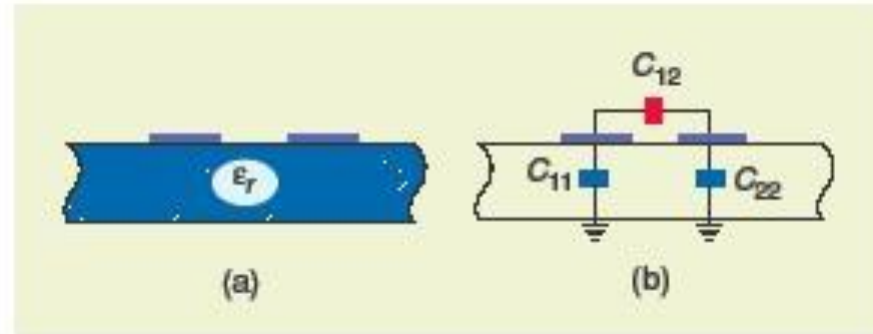


$$Z_{0e} = \frac{1}{vC_e}$$

$$Z_{0o} = \frac{1}{vC_o}$$

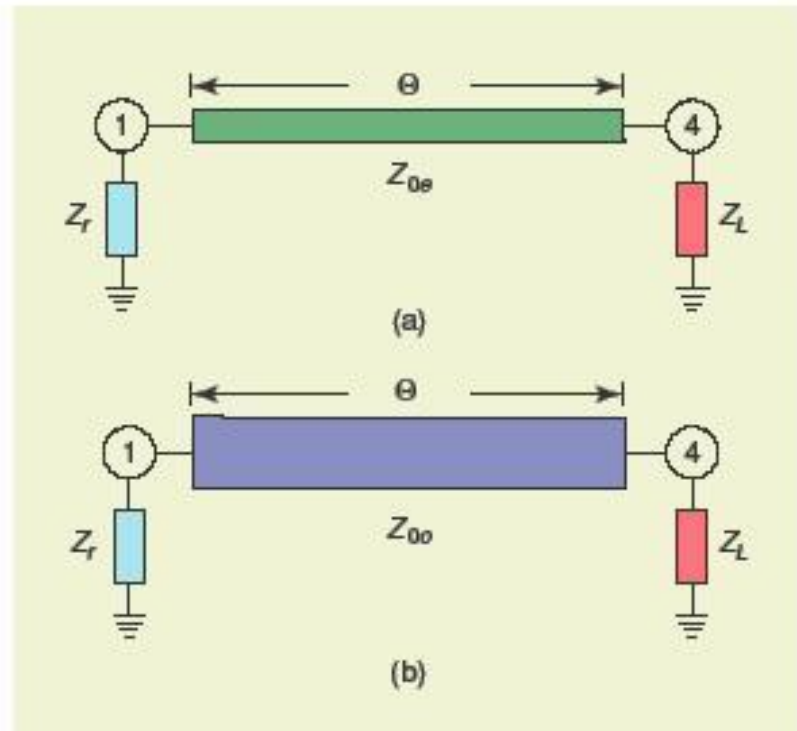

# Calculul pe modul par si impar

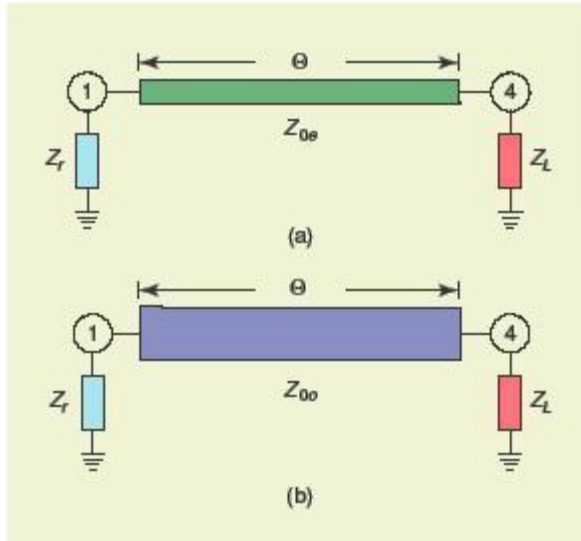

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} \cos \theta & jZ_{0e} \sin \theta \\ j \frac{\sin \theta}{Z_{0e}} & \cos \theta \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} \cos \theta & jZ_{0o} \sin \theta \\ j \frac{\sin \theta}{Z_{0o}} & \cos \theta \end{bmatrix}$$

$$\Gamma_e = \frac{(Z_L - Z_r) \cos \theta + j \left( Z_{0e} - \frac{1}{Z_{0e}} Z_L Z_r \right) \sin \theta}{(Z_L + Z_r) \cos \theta + j \left( Z_{0e} + \frac{1}{Z_{0e}} Z_L Z_r \right) \sin \theta}$$


$$\Gamma_o = \frac{(Z_L - Z_r) \cos \theta + j \left( Z_{0o} - \frac{1}{Z_{0o}} Z_L Z_r \right) \sin \theta}{(Z_L + Z_r) \cos \theta + j \left( Z_{0o} + \frac{1}{Z_{0o}} Z_L Z_r \right) \sin \theta}$$

$$T_e = \frac{2}{\left( \sqrt{\frac{Z_L}{Z_r}} + \sqrt{\frac{Z_r}{Z_L}} \right) \cos \theta + j \left( \frac{Z_{0e}}{\sqrt{Z_L Z_r}} + \frac{1}{Z_{0e}} \sqrt{Z_L Z_r} \right) \sin \theta}$$

$$T_e = \frac{2}{\left( \sqrt{\frac{Z_L}{Z_r}} + \sqrt{\frac{Z_r}{Z_L}} \right) \cos \theta + j \left( \frac{Z_{0o}}{\sqrt{Z_L Z_r}} + \frac{1}{Z_{0o}} \sqrt{Z_L Z_r} \right) \sin \theta}$$



## Parametrii S

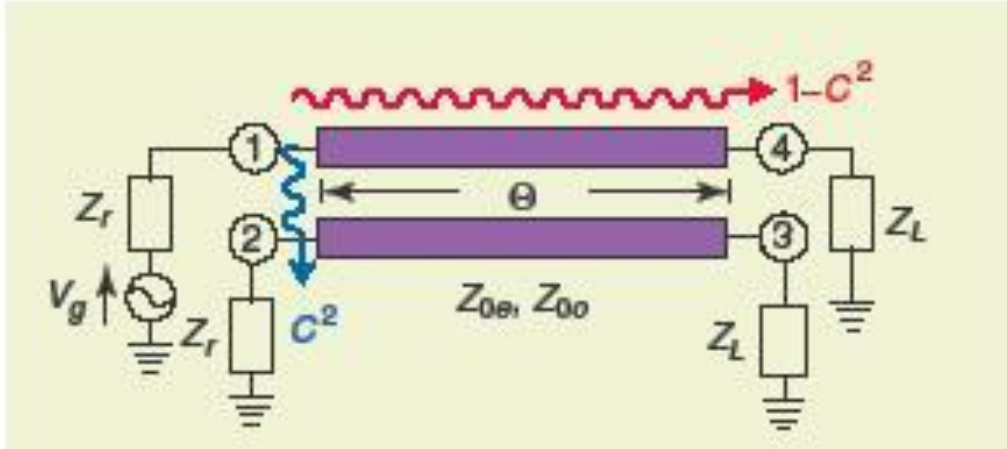

$$S_{11} = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o$$

$$S_{21} = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$

$$S_{31} = \frac{1}{2}T_e - \frac{1}{2}T_o$$


$$S_{41} = \frac{1}{2}T_e + \frac{1}{2}T_o$$

$$S_{11} = \frac{1}{2}(\Gamma_e + \Gamma_o) = \frac{\Re(N) + j\Im(N)}{D}$$

$$\Re(N) = (Z_L^2 - Z_r^2) \cos^2 \theta - \left[ \left( Z_{0e} Z_{0o} - \frac{1}{Z_{0e} Z_{0o}} (Z_L Z_r)^2 \right) \right] \sin^2 \theta$$

$$\Im(N) = \left[ (Z_{0e} + Z_{0o}) Z_L - Z_L Z_r \left( \frac{1}{Z_{0e}} + \frac{1}{Z_{0o}} \right) Z_r \right] \sin \theta \cos \theta$$

# Parametrii Z

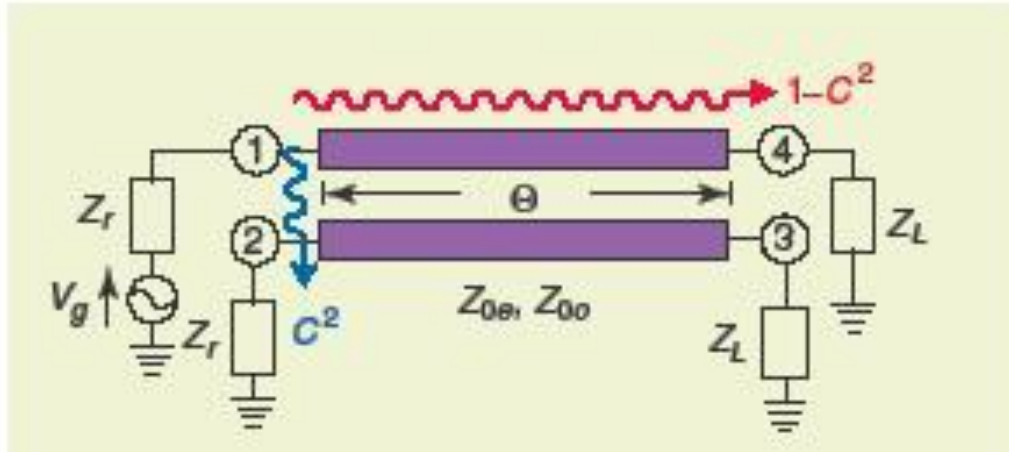

$$Z_c^+ = \frac{Z_{ce} + Z_{co}}{2}$$

$$Z_c^- = \frac{Z_{ce} - Z_{co}}{2}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} Z_c^+ \coth(\gamma z) & Z_c^- \coth(\gamma z) & \frac{Z_c^-}{\text{sh}(\gamma z)} & \frac{Z_c^+}{\text{sh}(\gamma z)} \\ Z_c^- \coth(\gamma z) & Z_c^+ \coth(\gamma z) & \frac{Z_c^+}{\text{sh}(\gamma z)} & \frac{Z_c^-}{\text{sh}(\gamma z)} \\ \frac{Z_c^-}{\text{sh}(\gamma z)} & \frac{Z_c^+}{\text{sh}(\gamma z)} & Z_c^+ \coth(\gamma z) & Z_c^- \coth(\gamma z) \\ \frac{Z_c^+}{\text{sh}(\gamma z)} & \frac{Z_c^-}{\text{sh}(\gamma z)} & Z_c^- \coth(\gamma z) & Z_c^+ \coth(\gamma z) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix}$$