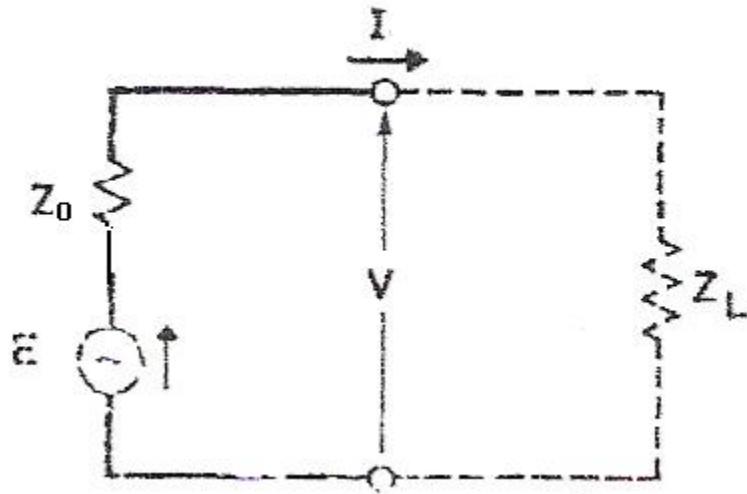


MATRICEA DE REPARTIȚIE

ADAPTAREA IN PUTERE



$$I = \frac{E}{Z_0 + Z_L}$$

$$V = \frac{EZ_L}{Z_0 + Z_L}$$

$$\Re e(Z_L |I|^2)$$

$$P_L = \Re e Z_L \left| \frac{E}{Z_L + Z_0} \right|^2 = \frac{R_L |E|^2}{(R_L + R_0)^2 + (X_L + X_0)^2}$$

$$P_L = \frac{|E|^2}{4R_0 + \frac{(R_L - R_0)^2}{R_L} + \frac{(X_L + X_0)^2}{R_L}}$$

Conditia de adaptare

$$R_L = R_0 \quad X_L = -X_0$$

$$P_a = \frac{|E|^2}{4R_0} \quad (R_0 > 0)$$

$$P_e = \frac{|E|^2}{4R_0} \quad (R_0 \neq 0)$$

Unde de putere

$$a = \frac{V + Z_0 I}{2\sqrt{|ReZ_0|}}$$

$$b = \frac{V - Z_0^* I}{2\sqrt{|ReZ_0|}}$$

$$V = \frac{p}{\sqrt{|ReZ_0|}} \left(Z_0^* a + Z_0 b \right)$$

$$I = \frac{p}{\sqrt{|ReZ_0|}} (a - b)$$

$$p = \begin{cases} 1, & ReZ_0 > 0 \\ -1, & ReZ_0 < 0 \end{cases}$$

Unde de putere - 2

$$|a|^2 = \frac{|E|^2}{4|R_0|} \quad P_e = p|a|^2$$

$$|a|^2 - |b|^2 = \frac{(V + Z_0 I)(V^* + Z_0^* I^*) - (V - Z_0^* I)(V^* - Z_0 I^*)}{4|R_0|} =$$

$$= \frac{(Z_0 + Z_0^*)(VI^* + V^*I)}{4|R_0|} = p \Re e \{ VI^* \}$$

$$\Re e \{ VI^* \} = p(|a|^2 - |b|^2)$$

Coeficienti de reflexie

$$\Gamma = \frac{b}{a}$$

$$\Gamma = \frac{Z_L - Z_0^*}{Z_L + Z_0}$$

$$\Gamma = \frac{R_L + j(X_L + X_0) - R_0}{R_L + j(X_L + X_0) + R_0}$$

$$|\Gamma|^2 = \left| \frac{Z_L - Z_0^*}{Z_L + Z_0} \right|^2$$

$$\Gamma' = \frac{Z_0 - Z_L^*}{Z_0 + Z_L}$$

$$|\Gamma'|^2 = \left| \frac{Z_0 - Z_L^*}{Z_0 + Z_L} \right|^2$$

$$|Z_0 - Z_L^*| = |Z_0^* - Z_L| = |Z_L - Z_0^*|$$

Matricea de repartitie

$$a = F(v + Gi) \quad b = F(v - G^+i)$$

$$v = Zi$$

$$b = Sa$$

$$F(Z - G^+)i = SF(Z + G)i$$

$$S = F(Z - G^+)(Z + G)^{-1}F^{-1}$$

Proprietati ale matricei de repartitie

- Circuite reciproce

$$[S] = [S]^T$$

- Circuite fara pierderi

$$[S]^* [S] = [S] [S]^* = [1]$$


Exemplu

cuadripol reactiv

$$\begin{cases} |S_{11}|^2 + |S_{12}|^2 = 1 & \text{(a)} \\ S_{11}^* S_{12} + S_{12}^* S_{22} = 0 & \text{(b)} \\ S_{12}^* S_{11} + S_{22}^* S_{12} = 0 & \text{(c)} \\ |S_{12}|^2 + |S_{22}|^2 = 1 & \text{(d)} \end{cases}$$


$$[S] = \begin{bmatrix} a \cdot e^{j\varphi_{11}} & \pm j\sqrt{1-a^2} \cdot e^{j\frac{\varphi_{11}+\varphi_{22}}{2}} \\ \pm j\sqrt{1-a^2} \cdot e^{j\frac{\varphi_{11}+\varphi_{22}}{2}} & a \cdot e^{j\varphi_{22}} \end{bmatrix}$$

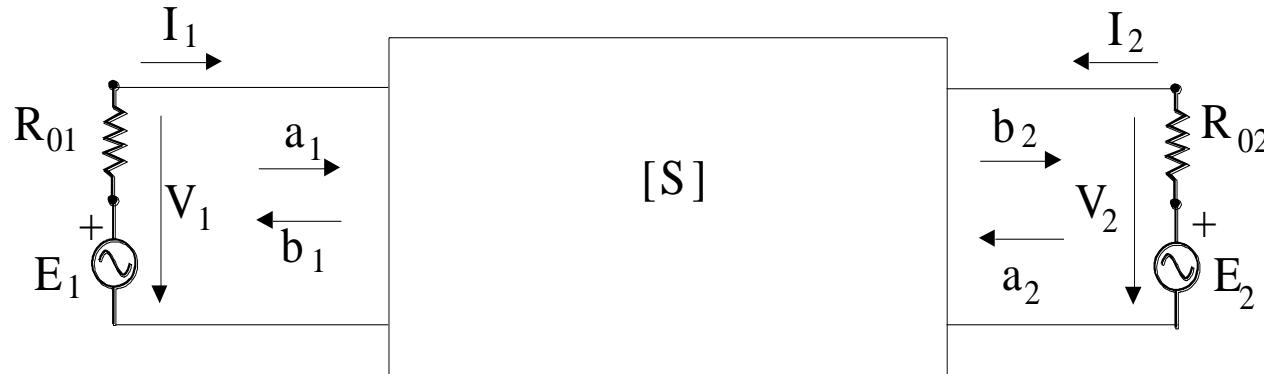Semnificatia parametrilor S pentru un cuadripol



$$S_{11} = \frac{Z_{11} - R_{01}}{Z_{11} + R_{01}}$$


$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

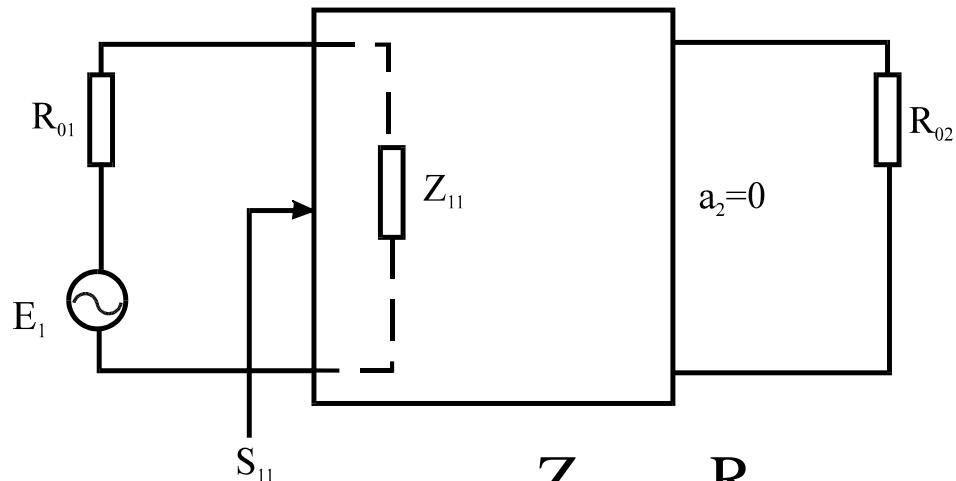

$$S_{11} = \frac{Z_{11} - R_{01}}{Z_{11} + R_{01}}$$


S22

$$S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$

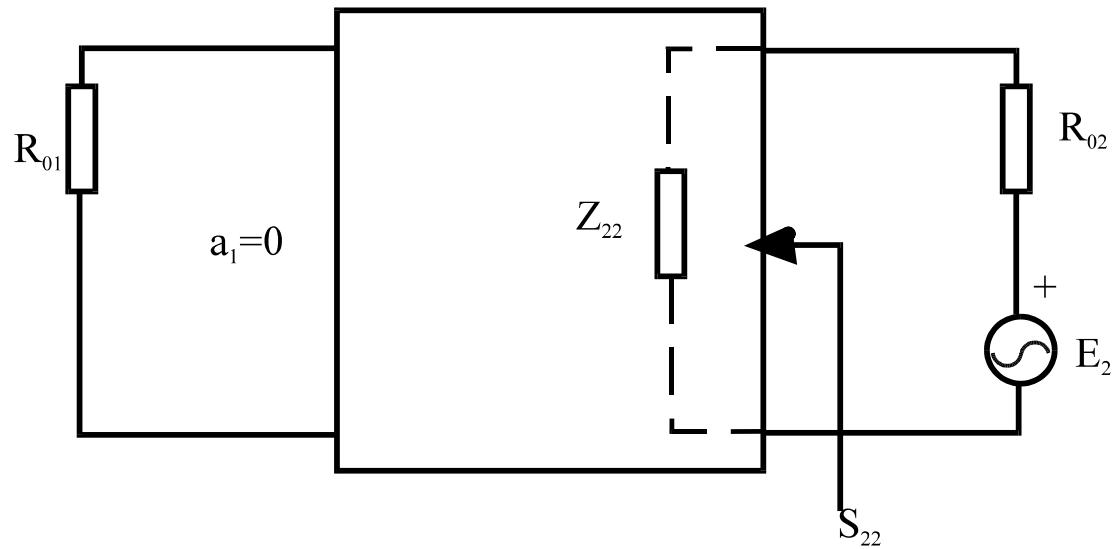

$$S_{22} = \frac{Z_{22} - R_{02}}{Z_{22} + R_{02}}$$

S21

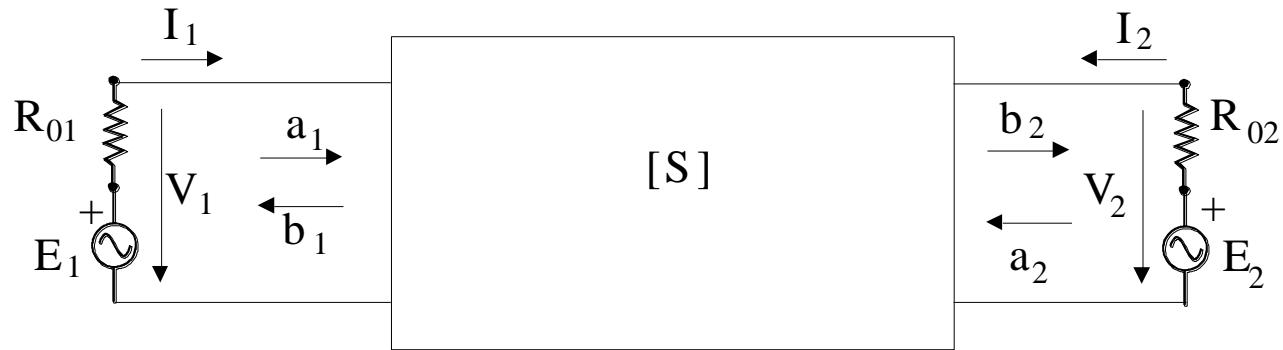


$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{21} = \frac{V_2 / \sqrt{R_{02}}}{\frac{1}{2} E_1 / \sqrt{R_{01}}}$$

$$|S_{21}|^2 = \frac{P_{L2}}{P_{A1}}$$

S12

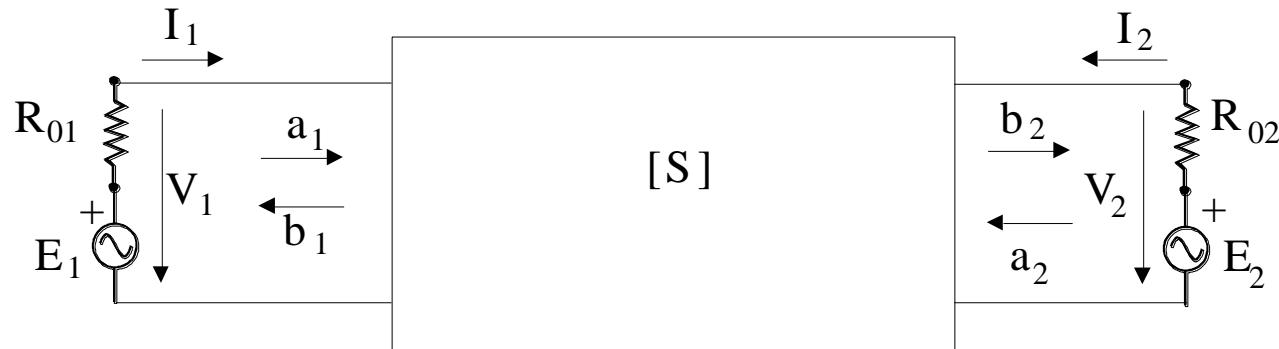

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a1=0},$$

$$S_{12} = \frac{V_1 / \sqrt{R_{01}}}{\frac{1}{2} E_2 / \sqrt{R_{02}}}$$

$$|S_{12}|^2 = \frac{P_{L1}}{P_{A2}} =$$

Legatura intre matricea S si matricea Y

$$S_{11} = \frac{(1 - y_{11})(1 + y_{22}) + y_{12}y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12}y_{21}}$$

$$S_{12} = \frac{-2y_{12}}{(1 + y_{11})(1 + y_{22}) - y_{12}y_{21}}$$

$$S_{21} = \frac{-2y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12}y_{21}}$$

$$S_{22} = \frac{(1 + y_{11})(1 - y_{22}) + y_{12}y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12}y_{21}}$$

Legatura dintre matricea S si matricea ABCD

$$S_{11} = \frac{AZ_{02} + B - CZ_{01}Z_{02} - DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{12} = \frac{2(AD - BC)\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{21} = \frac{2\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{22} = \frac{-AZ_{02} + B - CZ_{01}Z_{02} + DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$