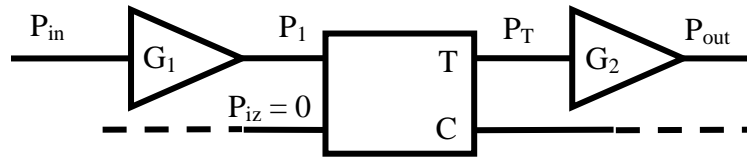


Subject no. 1

1. $z = 0.735 + j \cdot 1.035$; $Y = 1 / 50\Omega / (0.735 + j \cdot 1.035) = 0.0091S + j \cdot (-0.0128)S$; $\Gamma = (z-1)/(z+1) = (0.735 + j \cdot 1.035 - 1)/(0.735 + j \cdot 1.035 + 1) = 0.150 + j \cdot (0.507) = 0.529 \angle 73.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

2. $P_{in} = 1.65mW = 2.17dBm$; $P_1 = P_{in} + G_1 = 2.17dBm + 9.3dB = 11.47dBm = 14.04mW$; $P_c = P_1 - C = 11.47dBm - 4.25dB = 7.22dBm = 5.28mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 14.04mW - 5.28mW = 8.77mW = 9.43dBm$; $P_{out} = P_T + G_2 = 9.43dBm + 11.1dB = 20.53dBm = 112.92mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.323 + j \cdot 0.314 + 1)/[1 - (-0.323 + j \cdot 0.314)] = 21.56\Omega + j \cdot 16.98\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 10.78\Omega + j \cdot 8.49\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.614 + j \cdot 0.225 = 0.654 \angle 159.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.654$, $\arg(\Gamma) = 159.8^\circ$
 $\theta_{S1} = 165.5^\circ$; $\text{Im}(y_S) = -1.729$; $\theta_{P1} = 120.0^\circ$ **and** $\theta_{S2} = 34.7^\circ$; $\text{Im}(y_S) = 1.729$; $\theta_{P2} = 60.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.90dB$): $G(1,2) = G_1 + G_2 = 8.3 + 11.6 = 19.9dB$; $G(1,4) = G_1 + G_4 = 8.3 + 8.0 = 16.3dB$; $G(2,3) = G_2 + G_3 = 11.6 + 6.5 = 18.1dB$; $G(2,4) = G_2 + G_4 = 11.6 + 8.0 = 19.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.92dB = 1.236$, $F_2 = 1.23dB = 1.327$, $F_3 = 0.50dB = 1.122$, $F_4 = 0.85dB = 1.216$, $G_3 = 6.5dB = 4.467$, $G_4 = 8.0dB = 6.310$;

$F(4,1) = 1.216 + (1.236 - 1)/6.310 = 1.254 = 0.98dB$; $F(3,2) = 1.122 + (1.327 - 1)/4.467 = 1.195 = 0.77dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.4	$0.216 + j \cdot (-0.302)$	0.372	0.601	0.551
3.1	$-0.031 + j \cdot (-0.576)$	0.577	0.959	0.911

b) $\mu(1.4GHz) < \mu(3.1GHz)$ so the transistor has better stability at 3.1 GHz

c) we use S parameters for f = 3.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 36.22 = 15.59dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.150$, $U_{minus} = -1.217dB$, $U_{plus} = 1.416dB$ (L8/2021, S142)

Subject no. 2

1. $z = 1.190 + j \cdot 1.110$; $Y = 1 / 50\Omega / (1.190 + j \cdot 1.110) = 0.0090S + j \cdot (-0.0084)S$; $\Gamma = (z-1)/(z+1) = (1.190 + j \cdot 1.110 - 1)/(1.190 + j \cdot 1.110 + 1) = 0.273 + j \cdot (0.368) = 0.459 \angle 53.4^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

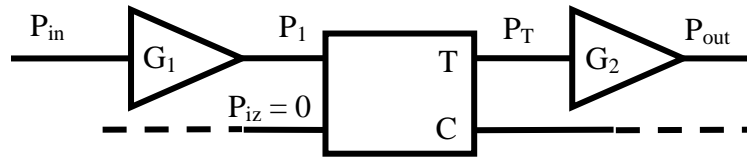2. $P_{in} = 2.15mW = 3.32dBm$; $P_1 = P_{in} + G_1 = 3.32dBm + 8.2dB = 11.52dBm = 14.20mW$; $P_c = P_1 - C = 11.52dBm - 6.25dB = 5.27dBm = 3.37mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 14.20mW - 3.37mW = 10.84mW = 10.35dBm$; $P_{out} = P_T + G_2 = 10.35dBm + 10.5dB = 20.85dBm = 121.59mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.296 + j \cdot 0.365 + 1)/[1 - (-0.296 + j \cdot 0.365)] = 21.49\Omega + j \cdot 20.13\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 10.74\Omega + j \cdot 10.07\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.602 + j \cdot 0.266 = 0.658 \angle 156.2^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.658$, $\arg(\Gamma) = 156.2^\circ$; $\theta_{S1} = 167.5^\circ$; $\text{Im}(y_S) = -1.748$; $\theta_{P1} = 119.8^\circ$ **and** $\theta_{S2} = 36.3^\circ$; $\text{Im}(y_S) = 1.748$; $\theta_{P2} = 60.2^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.60dB$): $G(1,2) = G_1 + G_2 = 8.4 + 10.5 = 18.9dB$; $G(1,4) = G_1 + G_4 = 8.4 + 7.4 = 15.8dB$; $G(2,3) = G_2 + G_3 = 10.5 + 5.8 = 16.3dB$; $G(2,4) = G_2 + G_4 = 10.5 + 7.4 = 17.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.97dB = 1.250$, $F_2 = 1.28dB = 1.343$, $F_3 = 0.53dB = 1.130$, $F_4 = 0.84dB = 1.213$, $G_3 = 5.8dB = 3.802$, $G_4 = 7.4dB = 5.495$;

$F(4,1) = 1.213 + (1.250 - 1)/5.495 = 1.259 = 1.00dB$; $F(3,2) = 1.130 + (1.343 - 1)/3.802 = 1.220 = 0.86dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
0.1	$0.275 + j \cdot (0.048)$	0.280	0.112	0.095
1.5	$0.429 + j \cdot (-0.311)$	0.530	0.188	0.212

b) $\mu(0.1GHz) < \mu(1.5GHz)$ so the transistor has better stability at 1.5 GHz

c) we use S parameters for $f = 1.5GHz$ and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)

$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 1029.20 = 30.12dB$


d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 1.717$, $U_{minus} = -8.683dB$, $U_{plus} = 2.885dB$

(L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 3

1. $z = 1.260 - j \cdot 0.850$; $Y = 1 / 50\Omega / (1.260 - j \cdot 0.850) = 0.0109S + j \cdot (0.0074)S$; $\Gamma = (z-1)/(z+1) = (1.260 - j \cdot 0.850 - 1)/(1.260 - j \cdot 0.850 + 1) = 0.225 + j \cdot (-0.292) = 0.368 \angle -52.4^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

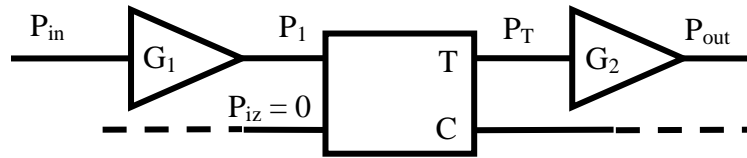2. $P_{in} = 1.15mW = 0.61dBm$; $P_1 = P_{in} + G_1 = 0.61dBm + 6.0dB = 6.61dBm = 4.58mW$; $P_c = P_1 - C = 6.61dBm - 4.85dB = 1.76dBm = 1.50mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 4.58mW - 1.50mW = 3.08mW = 4.88dBm$; $P_{out} = P_T + G_2 = 4.88dBm + 10.1dB = 14.98dBm = 31.51mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.272 + j \cdot 0.688 + 1)/[1 - (-0.272 + j \cdot 0.688)] = 10.82\Omega + j \cdot 32.90\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.41\Omega + j \cdot 16.45\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.659 + j \cdot 0.492 = 0.822 \angle 143.2^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.822$, $\arg(\Gamma) = 143.2^\circ$
 $\theta_{S1} = 1.0^\circ$; $\text{Im}(y_S) = -2.889$; $\theta_{P1} = 109.1^\circ$ **and** $\theta_{S2} = 35.7^\circ$; $\text{Im}(y_S) = 2.889$; $\theta_{P2} = 70.9^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.35dB$): $G(1,2) = G_1 + G_2 = 8.3 + 10.2 = 18.5dB$; $G(1,4) = G_1 + G_4 = 8.3 + 8.2 = 16.5dB$; $G(2,3) = G_2 + G_3 = 10.2 + 5.8 = 16.0dB$; $G(2,4) = G_2 + G_4 = 10.2 + 8.2 = 18.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.05dB = 1.274$, $F_2 = 1.20dB = 1.318$, $F_3 = 0.57dB = 1.140$, $F_4 = 0.78dB = 1.197$, $G_3 = 5.8dB = 3.802$, $G_4 = 8.2dB = 6.607$;

$F(4,1) = 1.197 + (1.274 - 1)/6.607 = 1.238 = 0.93dB$; $F(3,2) = 1.140 + (1.318 - 1)/3.802 = 1.224 = 0.88dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
3.1	$-0.058 + j \cdot (-0.345)$	0.350	0.952	0.970
2.0	$0.355 + j \cdot (-0.385)$	0.523	0.229	0.836

b) $\mu'(3.1GHz) > \mu'(2.0GHz)$ so the transistor has better stability at 3.1 GHz

c) we use S parameters for f = 3.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 37.08 = 15.69dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.044$, $U_{minus} = -0.372dB$, $U_{plus} = 0.389dB$ (L8/2021, S142)

Subject no. 4

1. $z = 1.045 - j \cdot 0.955$; $Y = 1 / 50\Omega / (1.045 - j \cdot 0.955) = 0.0104S + j \cdot (0.0095)S$; $\Gamma = (z-1)/(z+1) = (1.045 - j \cdot 0.955 - 1)/(1.045 - j \cdot 0.955 + 1) = 0.197 + j \cdot (-0.375) = 0.424 \angle -62.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

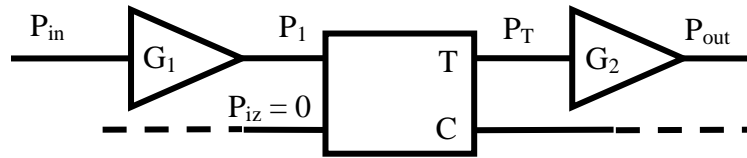2. $P_{in} = 1.80mW = 2.55dBm$; $P_1 = P_{in} + G_1 = 2.55dBm + 9.5dB = 12.05dBm = 16.04mW$; $P_c = P_1 - C = 12.05dBm - 4.25dB = 7.80dBm = 6.03mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 16.04mW - 6.03mW = 10.01mW = 10.01dBm$; $P_{out} = P_T + G_2 = 10.01dBm + 9.4dB = 19.41dBm = 87.21mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.186 + j \cdot 0.223 + 1)/[1 - (-0.186 + j \cdot 0.223)] = 31.44\Omega + j \cdot 15.31\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 15.72\Omega + j \cdot 7.66\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.501 + j \cdot 0.175 = 0.531 \angle 160.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.531$, $\arg(\Gamma) = 160.8^\circ$
 $\theta_{S1} = 160.7^\circ$; $\text{Im}(y_S) = -1.253$; $\theta_{P1} = 128.6^\circ$ **and** $\theta_{S2} = 38.6^\circ$; $\text{Im}(y_S) = 1.253$; $\theta_{P2} = 51.4^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.05dB$): $G(1,2) = G_1 + G_2 = 8.0 + 11.2 = 19.2dB$; $G(1,4) = G_1 + G_4 = 8.0 + 8.6 = 16.6dB$; $G(2,3) = G_2 + G_3 = 11.2 + 5.7 = 16.9dB$; $G(2,4) = G_2 + G_4 = 11.2 + 8.6 = 19.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.04dB=1.271$, $F_2 = 1.18dB=1.312$, $F_3 = 0.66dB=1.164$, $F_4 = 0.85dB=1.216$, $G_3 = 5.7dB=3.715$, $G_4 = 8.6dB=7.244$;

$F(4,1) = 1.216 + (1.271-1)/7.244 = 1.254 = 0.98dB$; $F(3,2) = 1.164 + (1.312-1)/3.715 = 1.248 = 0.96dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.5	$0.046 + j \cdot (-0.344)$	0.347	0.862	0.825
3.2	$0.138 + j \cdot (-0.486)$	0.505	0.314	0.344

b) $\mu(2.5GHz) > \mu(3.2GHz)$ so the transistor has better stability at 2.5 GHz

c) we use S parameters for f = 2.5 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 55.64 = 17.45dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.063$, $U_{minus} = -0.530dB$, $U_{plus} = 0.564dB$ (L8/2021, S142)

Subject no. 5

1. $z = 1.225 + j \cdot 1.045$; $Y = 1 / 50\Omega / (1.225 + j \cdot 1.045) = 0.0094S + j \cdot (-0.0081)S$; $\Gamma = (z-1)/(z+1) = (1.225 + j \cdot 1.045 - 1)/(1.225 + j \cdot 1.045 + 1) = 0.264 + j \cdot (0.346) = 0.435 \angle 52.7^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

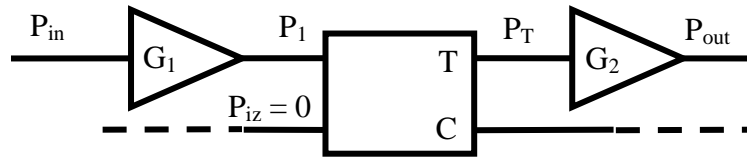2. $P_{in} = 1.15mW = 0.61dBm$; $P_1 = P_{in} + G_1 = 0.61dBm + 8.9dB = 9.51dBm = 8.93mW$; $P_c = P_1 - C = 9.51dBm - 5.50dB = 4.01dBm = 2.52mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.93mW - 2.52mW = 6.41mW = 8.07dBm$; $P_{out} = P_T + G_2 = 8.07dBm + 11.9dB = 19.97dBm = 99.29mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.468 + j \cdot 0.605 + 1)/[1 - (-0.468 + j \cdot 0.605)] = 8.23\Omega + j \cdot 24.00\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 4.11\Omega + j \cdot 12.00\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.761 + j \cdot 0.391 = 0.856 \angle 152.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.856$, $\arg(\Gamma) = 152.8^\circ$
 $\theta_{S1} = 178.0^\circ$; $\text{Im}(y_S) = -3.307$; $\theta_{P1} = 106.8^\circ$ **and** $\theta_{S2} = 29.2^\circ$; $\text{Im}(y_S) = 3.307$; $\theta_{P2} = 73.2^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 17.15dB$): $G(1,2) = G_1 + G_2 = 8.9 + 11.6 = 20.5dB$; $G(1,4) = G_1 + G_4 = 8.9 + 8.6 = 17.5dB$; $G(2,3) = G_2 + G_3 = 11.6 + 6.9 = 18.5dB$; $G(2,4) = G_2 + G_4 = 11.6 + 8.6 = 20.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.93dB = 1.239$, $F_2 = 1.20dB = 1.318$, $F_3 = 0.64dB = 1.159$, $F_4 = 0.71dB = 1.178$, $G_3 = 6.9dB = 4.898$, $G_4 = 8.6dB = 7.244$;

$F(4,1) = 1.178 + (1.239 - 1)/7.244 = 1.211 = 0.83dB$; $F(3,2) = 1.159 + (1.318 - 1)/4.898 = 1.224 = 0.88dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
0.5	$0.437 + j \cdot (0.045)$	0.439	0.349	0.272
2.1	$0.337 + j \cdot (-0.397)$	0.521	0.234	0.263

b) $\mu(0.5GHz) > \mu(2.1GHz)$ so the transistor has better stability at 0.5 GHz

c) we use S parameters for f = 0.5 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 1049.68 = 30.21dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.474$, $U_{minus} = -3.372dB$, $U_{plus} = 5.585dB$ (L8/2021, S142)

Subject no. 6

1. $z = 0.800 - j \cdot 1.065$; $Y = 1 / 50\Omega / (0.800 - j \cdot 1.065) = 0.0090S + j \cdot (0.0120)S$; $\Gamma = (z-1)/(z+1) = (0.800 - j \cdot 1.065 - 1)/(0.800 - j \cdot 1.065 + 1) = 0.177 + j \cdot (-0.487) = 0.518 \angle -70.0^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

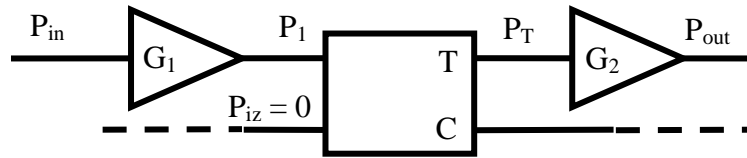2. $P_{in} = 2.60mW = 4.15dBm$; $P_1 = P_{in} + G_1 = 4.15dBm + 6.4dB = 10.55dBm = 11.35mW$; $P_c = P_1 - C = 10.55dBm - 6.85dB = 3.70dBm = 2.34mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 11.35mW - 2.34mW = 9.01mW = 9.54dBm$; $P_{out} = P_T + G_2 = 9.54dBm + 11.9dB = 21.44dBm = 139.48mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.184 + j \cdot 0.176 + 1)/[1 - (0.184 + j \cdot 0.176)] = 67.10\Omega + j \cdot 25.26\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 33.55\Omega + j \cdot 12.63\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.170 + j \cdot 0.177 = 0.245 \angle 133.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.245$, $\arg(\Gamma) = 133.9^\circ$ $\theta_{S1} = 165.2^\circ$; $\text{Im}(y_S) = -0.506$; $\theta_{P1} = 153.1^\circ$ **and** $\theta_{S2} = 61.0^\circ$; $\text{Im}(y_S) = 0.506$; $\theta_{P2} = 26.9^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.45dB$): $G(1,2) = G_1 + G_2 = 8.3 + 10.3 = 18.6dB$; $G(1,4) = G_1 + G_4 = 8.3 + 7.5 = 15.8dB$; $G(2,3) = G_2 + G_3 = 10.3 + 6.1 = 16.4dB$; $G(2,4) = G_2 + G_4 = 10.3 + 7.5 = 17.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.94dB=1.242$, $F_2 = 1.24dB=1.330$, $F_3 = 0.66dB=1.164$, $F_4 = 0.89dB=1.227$, $G_3 = 6.1dB=4.074$, $G_4 = 7.5dB=5.623$;

$F(4,1) = 1.227 + (1.242-1)/5.623 = 1.270 = 1.04dB$; $F(3,2) = 1.164 + (1.330-1)/4.074 = 1.245 = 0.95dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.2	$0.482 + j \cdot (-0.208)$	0.525	0.641	0.723
2.8	$0.215 + j \cdot (-0.465)$	0.512	0.285	0.802

b) $\mu'(1.2GHz) < \mu'(2.8GHz)$ so the transistor has better stability at 2.8 GHz

c) we use S parameters for f = 2.8 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 373.35 = 25.72dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 1.070$, $U_{minus} = -6.319dB$, $U_{plus} = 23.118dB$ (L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 7

1. $z = 1.035 + j \cdot 0.745$; $Y = 1 / 50\Omega / (1.035 + j \cdot 0.745) = 0.0127S + j \cdot (-0.0092)S$; $\Gamma = (z-1)/(z+1) = (1.035 + j \cdot 0.745 - 1)/(1.035 + j \cdot 0.745 + 1) = 0.133 + j \cdot (0.317) = 0.344 \angle 67.2^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

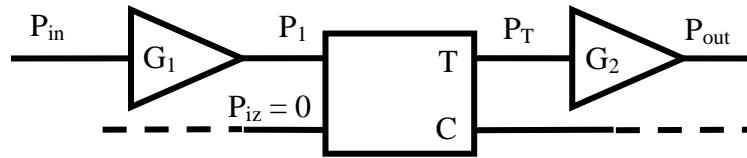2. $P_{in} = 4.05mW = 6.07dBm$; $P_1 = P_{in} + G_1 = 6.07dBm + 8.7dB = 14.77dBm = 30.02mW$; $P_c = P_1 - C = 14.77dBm - 5.50dB = 9.27dBm = 8.46mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 30.02mW - 8.46mW = 21.56mW = 13.34dBm$; $P_{out} = P_T + G_2 = 13.34dBm + 10.3dB = 23.64dBm = 231.03mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.699 + j \cdot 0.258 + 1)/[1 - (-0.699 + j \cdot 0.258)] = 7.53\Omega + j \cdot 8.74\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 3.77\Omega + j \cdot 4.37\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.848 + j \cdot 0.150 = 0.861 \angle 170.0^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.861$, $\arg(\Gamma) = 170.0^\circ$; $\theta_{S1} = 169.7^\circ$; $\text{Im}(y_S) = -3.384$; $\theta_{P1} = 106.5^\circ$ **and** $\theta_{S2} = 20.3^\circ$; $\text{Im}(y_S) = 3.384$; $\theta_{P2} = 73.5^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 13.60dB$): $G(1,2) = G_1 + G_2 = 8.0 + 11.4 = 19.4dB$; $G(1,4) = G_1 + G_4 = 8.0 + 7.2 = 15.2dB$; $G(2,3) = G_2 + G_3 = 11.4 + 5.2 = 16.6dB$; $G(2,4) = G_2 + G_4 = 11.4 + 7.2 = 18.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.00dB = 1.259$, $F_2 = 1.19dB = 1.315$, $F_3 = 0.52dB = 1.127$, $F_4 = 0.74dB = 1.186$, $G_3 = 5.2dB = 3.311$, $G_4 = 7.2dB = 5.248$;

$F(4,1) = 1.186 + (1.259 - 1)/5.248 = 1.235 = 0.92dB$; $F(3,2) = 1.127 + (1.315 - 1)/3.311 = 1.222 = 0.87dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.8	$0.157 + j \cdot (-0.322)$	0.358	0.715	0.665
3.5	$0.081 + j \cdot (-0.492)$	0.498	0.345	0.375

b) $\mu(1.8GHz) > \mu(3.5GHz)$ so the transistor has better stability at 1.8 GHz

c) we use S parameters for f = 1.8 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 104.32 = 20.18dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.108$, $U_{minus} = -0.888dB$, $U_{plus} = 0.989dB$ (L8/2021, S142)

Subject no. 8

1. $z = 0.970 + j \cdot 1.190$; $Y = 1 / 50\Omega / (0.970 + j \cdot 1.190) = 0.0082S + j \cdot (-0.0101)S$; $\Gamma = (z-1)/(z+1) = (0.970 + j \cdot 1.190 - 1)/(0.970 + j \cdot 1.190 + 1) = 0.256 + j \cdot (0.449) = 0.517 \angle 60.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

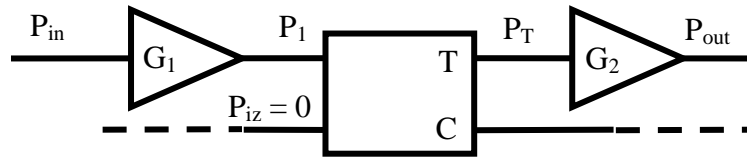2. $P_{in} = 3.10mW = 4.91dBm$; $P_1 = P_{in} + G_1 = 4.91dBm + 9.0dB = 13.91dBm = 24.62mW$; $P_c = P_1 - C = 13.91dBm - 5.20dB = 8.71dBm = 7.44mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 24.62mW - 7.44mW = 17.19mW = 12.35dBm$; $P_{out} = P_T + G_2 = 12.35dBm + 8.3dB = 20.65dBm = 116.20mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.296 + j \cdot 0.359 + 1)/[1 - (-0.296 + j \cdot 0.359)] = 21.66\Omega + j \cdot 19.85\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 10.83\Omega + j \cdot 9.93\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.601 + j \cdot 0.261 = 0.656 \angle 156.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.656$, $\arg(\Gamma) = 156.5^\circ$
 $\theta_{S1} = 167.2^\circ$; $\text{Im}(y_S) = -1.736$; $\theta_{P1} = 119.9^\circ$ **and** $\theta_{S2} = 36.3^\circ$; $\text{Im}(y_S) = 1.736$; $\theta_{P2} = 60.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.60dB$): $G(1,2) = G_1 + G_2 = 8.5 + 11.1 = 19.6dB$; $G(1,4) = G_1 + G_4 = 8.5 + 8.8 = 17.3dB$; $G(2,3) = G_2 + G_3 = 11.1 + 5.7 = 16.8dB$; $G(2,4) = G_2 + G_4 = 11.1 + 8.8 = 19.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.95dB = 1.245$, $F_2 = 1.25dB = 1.334$, $F_3 = 0.54dB = 1.132$, $F_4 = 0.79dB = 1.199$, $G_3 = 5.7dB = 3.715$, $G_4 = 8.8dB = 7.586$;

$F(4,1) = 1.199 + (1.245 - 1)/7.586 = 1.232 = 0.91dB$; $F(3,2) = 1.132 + (1.334 - 1)/3.715 = 1.222 = 0.87dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.8	$0.076 + j \cdot (-0.565)$	0.570	0.933	0.866
0.8	$0.508 + j \cdot (-0.179)$	0.539	0.111	0.127

b) $\mu(2.8GHz) > \mu(0.8GHz)$ so the transistor has better stability at 2.8 GHz

c) we use S parameters for f = 2.8 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 43.68 = 16.40dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.150$, $U_{minus} = -1.212dB$, $U_{plus} = 1.408dB$ (L8/2021, S142)

Subject no. 9

1. $z = 0.945 - j \cdot 1.160$; $Y = 1 / 50\Omega / (0.945 - j \cdot 1.160) = 0.0084S + j \cdot (0.0104)S$; $\Gamma = (z-1)/(z+1) = (0.945 - j \cdot 1.160 - 1)/(0.945 - j \cdot 1.160 + 1) = 0.242 + j \cdot (-0.452) = 0.513 \angle -61.9^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

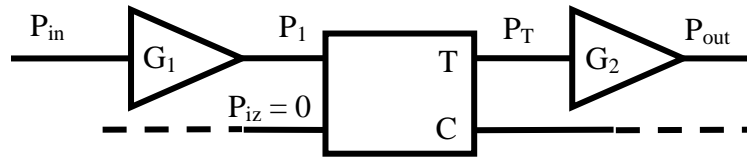2. $P_{in} = 2.90mW = 4.62dBm$; $P_1 = P_{in} + G_1 = 4.62dBm + 9.4dB = 14.02dBm = 25.26mW$; $P_c = P_1 - C = 14.02dBm - 4.30dB = 9.72dBm = 9.38mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 25.26mW - 9.38mW = 15.87mW = 12.01dBm$; $P_{out} = P_T + G_2 = 12.01dBm + 8.5dB = 20.51dBm = 112.38mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.119 + j \cdot 0.398 + 1)/[1 - (0.119 + j \cdot 0.398)] = 44.27\Omega + j \cdot 42.59\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 22.13\Omega + j \cdot 21.29\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.275 + j \cdot 0.376 = 0.466 \angle 126.2^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.466$, $\arg(\Gamma) = 126.2^\circ$ $\theta_{S1} = 175.8^\circ$; $\text{Im}(y_S) = -1.054$; $\theta_{P1} = 133.5^\circ$ **and** $\theta_{S2} = 58.0^\circ$; $\text{Im}(y_S) = 1.054$; $\theta_{P2} = 46.5^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.95dB$): $G(1,2) = G_1 + G_2 = 9.3 + 10.9 = 20.2dB$; $G(1,4) = G_1 + G_4 = 9.3 + 8.5 = 17.8dB$; $G(2,3) = G_2 + G_3 = 10.9 + 5.6 = 16.5dB$; $G(2,4) = G_2 + G_4 = 10.9 + 8.5 = 19.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.94dB=1.242$, $F_2 = 1.15dB=1.303$, $F_3 = 0.66dB=1.164$, $F_4 = 0.86dB=1.219$, $G_3 = 5.6dB=3.631$, $G_4 = 8.5dB=7.079$;

$F(4,1) = 1.219 + (1.242-1)/7.079 = 1.253 = 0.98dB$; $F(3,2) = 1.164 + (1.303-1)/3.631 = 1.248 = 0.96dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.8	$0.384 + j \cdot (-0.394)$	0.550	0.795	0.832
2.5	$0.270 + j \cdot (-0.440)$	0.516	0.262	0.811

b) $\mu' (1.8GHz) > \mu' (2.5 GHz)$ so the transistor has better stability at 1.8 GHz

c) we use S parameters for f = 1.8 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 99.35 = 19.97dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.180$, $U_{minus} = -1.441dB$, $U_{plus} = 1.729dB$ (L8/2021, S142)

Subject no. 10

1. $z = 0.980 + j \cdot 0.740$; $Y = 1 / 50\Omega / (0.980 + j \cdot 0.740) = 0.0130S + j \cdot (-0.0098)S$; $\Gamma = (z-1)/(z+1) = (0.980 + j \cdot 0.740 - 1)/(0.980 + j \cdot 0.740 + 1) = 0.114 + j \cdot (0.331) = 0.350 \angle 71.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

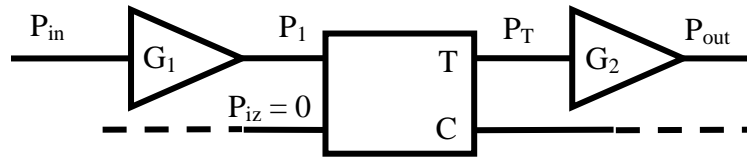2. $P_{in} = 1.60mW = 2.04dBm$; $P_1 = P_{in} + G_1 = 2.04dBm + 7.5dB = 9.54dBm = 9.00mW$; $P_c = P_1 - C = 9.54dBm - 4.05dB = 5.49dBm = 3.54mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 9.00mW - 3.54mW = 5.46mW = 7.37dBm$; $P_{out} = P_T + G_2 = 7.37dBm + 8.7dB = 16.07dBm = 40.45mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.065 + j \cdot 0.637 + 1)/[1 - (-0.065 + j \cdot 0.637)] = 19.16\Omega + j \cdot 41.36\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 9.58\Omega + j \cdot 20.68\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.498 + j \cdot 0.520 = 0.720 \angle 133.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.720$, $\arg(\Gamma) = 133.8^\circ$
 $\theta_{S1} = 1.1^\circ$; $\text{Im}(y_S) = -2.075$; $\theta_{P1} = 115.7^\circ$ **and** $\theta_{S2} = 45.1^\circ$; $\text{Im}(y_S) = 2.075$; $\theta_{P2} = 64.3^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.35dB$): $G(1,2) = G_1 + G_2 = 9.3 + 10.2 = 19.5dB$; $G(1,4) = G_1 + G_4 = 9.3 + 7.4 = 16.7dB$; $G(2,3) = G_2 + G_3 = 10.2 + 6.9 = 17.1dB$; $G(2,4) = G_2 + G_4 = 10.2 + 7.4 = 17.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.91dB = 1.233$, $F_2 = 1.20dB = 1.318$, $F_3 = 0.64dB = 1.159$, $F_4 = 0.89dB = 1.227$, $G_3 = 6.9dB = 4.898$, $G_4 = 7.4dB = 5.495$;

$F(4,1) = 1.227 + (1.233 - 1)/5.495 = 1.270 = 1.04dB$; $F(3,2) = 1.159 + (1.318 - 1)/4.898 = 1.224 = 0.88dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.6	$0.187 + j \cdot (-0.311)$	0.363	0.661	0.611
4.1	$-0.022 + j \cdot (-0.487)$	0.488	0.399	0.428

b) $\mu(1.6GHz) > \mu(4.1GHz)$ so the transistor has better stability at 1.6 GHz

c) we use S parameters for $f = 1.6GHz$ and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 131.20 = 21.18dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.131$, $U_{minus} = -1.067dB$, $U_{plus} = 1.217dB$ (L8/2021, S142)

Subject no. 11

1. $z = 0.750 + j \cdot 1.105$; $Y = 1 / 50\Omega / (0.750 + j \cdot 1.105) = 0.0084S + j \cdot (-0.0124)S$; $\Gamma = (z-1)/(z+1) = (0.750 + j \cdot 1.105 - 1)/(0.750 + j \cdot 1.105 + 1) = 0.183 + j \cdot (0.516) = 0.547 \angle 70.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

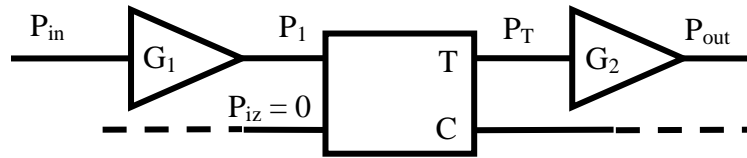2. $P_{in} = 3.20mW = 5.05dBm$; $P_1 = P_{in} + G_1 = 5.05dBm + 7.3dB = 12.35dBm = 17.19mW$; $P_c = P_1 - C = 12.35dBm - 6.60dB = 5.75dBm = 3.76mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.19mW - 3.76mW = 13.43mW = 11.28dBm$; $P_{out} = P_T + G_2 = 11.28dBm + 10.3dB = 21.58dBm = 143.86mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.713 + j \cdot 0.180 + 1)/[1 - (0.713 + j \cdot 0.180)] = 200.07\Omega + j \cdot 156.84\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 100.03\Omega + j \cdot 78.42\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.476 + j \cdot 0.274 = 0.549 \angle 29.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.549$, $\arg(\Gamma) = 29.9^\circ$; $\theta_{S1} = 46.7^\circ$; $\text{Im}(y_S) = -1.315$; $\theta_{P1} = 127.2^\circ$ **and** $\theta_{S2} = 103.4^\circ$; $\text{Im}(y_S) = 1.315$; $\theta_{P2} = 52.8^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.40dB$): $G(1,2) = G_1 + G_2 = 9.7 + 10.6 = 20.3dB$; $G(1,4) = G_1 + G_4 = 9.7 + 8.3 = 18.0dB$; $G(2,3) = G_2 + G_3 = 10.6 + 6.0 = 16.6dB$; $G(2,4) = G_2 + G_4 = 10.6 + 8.3 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.99dB = 1.256$, $F_2 = 1.18dB = 1.312$, $F_3 = 0.65dB = 1.161$, $F_4 = 0.77dB = 1.194$, $G_3 = 6.0dB = 3.981$, $G_4 = 8.3dB = 6.761$;

$F(4,1) = 1.194 + (1.256 - 1)/6.761 = 1.232 = 0.91dB$; $F(3,2) = 1.161 + (1.312 - 1)/3.981 = 1.240 = 0.93dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.4	$0.461 + j \cdot (-0.278)$	0.538	0.699	0.574
2.4	$0.289 + j \cdot (-0.431)$	0.519	0.254	0.278

b) $\mu(1.4GHz) > \mu(2.4GHz)$ so the transistor has better stability at 1.4 GHz

c) we use S parameters for f = 1.4 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 160.09 = 22.04dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.215$, $U_{minus} = -1.691dB$, $U_{plus} = 2.101dB$ (L8/2021, S142)

Subject no. 12

1. $z = 0.750 - j \cdot 0.940$; $Y = 1 / 50\Omega / (0.750 - j \cdot 0.940) = 0.0104S + j \cdot (0.0130)S$; $\Gamma = (z-1)/(z+1) = (0.750 - j \cdot 0.940 - 1)/(0.750 - j \cdot 0.940 + 1) = 0.113 + j \cdot (-0.476) = 0.490 \angle -76.7^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

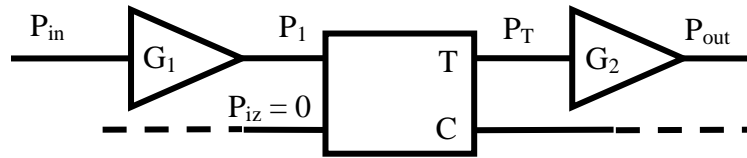2. $P_{in} = 3.95mW = 5.97dBm$; $P_1 = P_{in} + G_1 = 5.97dBm + 6.9dB = 12.87dBm = 19.35mW$; $P_c = P_1 - C = 12.87dBm - 4.70dB = 8.17dBm = 6.56mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 19.35mW - 6.56mW = 12.79mW = 11.07dBm$; $P_{out} = P_T + G_2 = 11.07dBm + 11.2dB = 22.27dBm = 168.62mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.379 + j \cdot 0.251 + 1)/[1 - (-0.379 + j \cdot 0.251)] = 20.19\Omega + j \cdot 12.78\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 10.10\Omega + j \cdot 6.39\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.645 + j \cdot 0.175 = 0.669 \angle 164.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.669$, $\arg(\Gamma) = 164.8^\circ$
 $\theta_{S1} = 163.6^\circ$; $\text{Im}(y_S) = -1.799$; $\theta_{P1} = 119.1^\circ$ **and** $\theta_{S2} = 31.6^\circ$; $\text{Im}(y_S) = 1.799$; $\theta_{P2} = 60.9^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.60dB$): $G(1,2) = G_1 + G_2 = 9.0 + 10.8 = 19.8dB$; $G(1,4) = G_1 + G_4 = 9.0 + 8.0 = 17.0dB$; $G(2,3) = G_2 + G_3 = 10.8 + 6.0 = 16.8dB$; $G(2,4) = G_2 + G_4 = 10.8 + 8.0 = 18.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.97dB = 1.250$, $F_2 = 1.13dB = 1.297$, $F_3 = 0.51dB = 1.125$, $F_4 = 0.83dB = 1.211$, $G_3 = 6.0dB = 3.981$, $G_4 = 8.0dB = 6.310$;

$F(4,1) = 1.211 + (1.250 - 1)/6.310 = 1.250 = 0.97dB$; $F(3,2) = 1.125 + (1.297 - 1)/3.981 = 1.199 = 0.79dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.6	$0.424 + j \cdot (-0.335)$	0.541	0.754	0.802
2.6	$0.252 + j \cdot (-0.449)$	0.515	0.270	0.809

b) $\mu'(1.6GHz) < \mu'(2.6GHz)$ so the transistor has better stability at 2.6 GHz

c) we use S parameters for f = 2.6 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 421.63 = 26.25dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 1.144$, $U_{minus} = -6.625dB$, $U_{plus} = 16.819dB$ (L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 13

1. $z = 0.890 - j \cdot 0.950$; $Y = 1 / 50\Omega / (0.890 - j \cdot 0.950) = 0.0105S + j \cdot (0.0112)S$; $\Gamma = (z-1)/(z+1) = (0.890 - j \cdot 0.950 - 1)/(0.890 - j \cdot 0.950 + 1) = 0.155 + j \cdot (-0.425) = 0.452 \angle -69.9^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

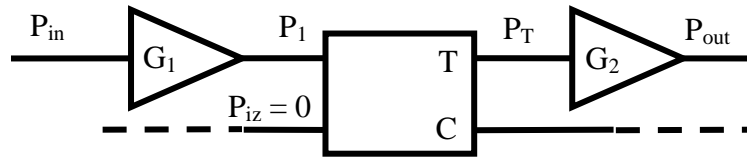2. $P_{in} = 3.25mW = 5.12dBm$; $P_1 = P_{in} + G_1 = 5.12dBm + 6.6dB = 11.72dBm = 14.86mW$; $P_c = P_1 - C = 11.72dBm - 5.25dB = 6.47dBm = 4.43mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 14.86mW - 4.43mW = 10.42mW = 10.18dBm$; $P_{out} = P_T + G_2 = 10.18dBm + 11.9dB = 22.08dBm = 161.39mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.062 + j \cdot 0.446 + 1)/[1 - (0.062 + j \cdot 0.446)] = 36.95\Omega + j \cdot 41.34\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 18.48\Omega + j \cdot 20.67\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.338 + j \cdot 0.404 = 0.527 \angle 129.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.527$, $\arg(\Gamma) = 129.9^\circ$ $\theta_{S1} = 175.9^\circ$; $\text{Im}(y_S) = -1.240$; $\theta_{P1} = 128.9^\circ$ **and** $\theta_{S2} = 54.1^\circ$; $\text{Im}(y_S) = 1.240$; $\theta_{P2} = 51.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.65dB$): $G(1,2) = G_1 + G_2 = 9.2 + 10.1 = 19.3dB$; $G(1,4) = G_1 + G_4 = 9.2 + 7.1 = 16.3dB$; $G(2,3) = G_2 + G_3 = 10.1 + 5.3 = 15.4dB$; $G(2,4) = G_2 + G_4 = 10.1 + 7.1 = 17.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.00dB=1.259$, $F_2 = 1.21dB=1.321$, $F_3 = 0.59dB=1.146$, $F_4 = 0.70dB=1.175$, $G_3 = 5.3dB=3.388$, $G_4 = 7.1dB=5.129$;

$F(4,1) = 1.175 + (1.259-1)/5.129 = 1.225 = 0.88dB$; $F(3,2) = 1.146 + (1.321-1)/3.388 = 1.240 = 0.94dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.2	$0.250 + j \cdot (-0.294)$	0.386	0.538	0.489
3.8	$0.027 + j \cdot (-0.492)$	0.493	0.371	0.402

b) $\mu(1.2GHz) > \mu(3.8GHz)$ so the transistor has better stability at 1.2 GHz

c) we use S parameters for f = 1.2 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 232.30 = 23.66dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.213$, $U_{minus} = -1.674dB$, $U_{plus} = 2.075dB$ (L8/2021, S142)

Subject no. 14

1. $z = 0.830 - j \cdot 0.955$; $Y = 1 / 50\Omega / (0.830 - j \cdot 0.955) = 0.0104S + j \cdot (0.0119)S$; $\Gamma = (z-1)/(z+1) = (0.830 - j \cdot 0.955 - 1)/(0.830 - j \cdot 0.955 + 1) = 0.141 + j \cdot (-0.448) = 0.470 \angle -72.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

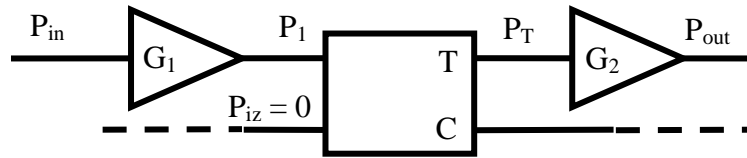2. $P_{in} = 2.55mW = 4.07dBm$; $P_1 = P_{in} + G_1 = 4.07dBm + 6.4dB = 10.47dBm = 11.13mW$; $P_c = P_1 - C = 10.47dBm - 4.10dB = 6.37dBm = 4.33mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 11.13mW - 4.33mW = 6.80mW = 8.33dBm$; $P_{out} = P_T + G_2 = 8.33dBm + 9.4dB = 17.73dBm = 59.23mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.006 + j \cdot 0.340 + 1)/[1 - (0.006 + j \cdot 0.340)] = 40.07\Omega + j \cdot 30.81\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 20.03\Omega + j \cdot 15.40\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.362 + j \cdot 0.300 = 0.470 \angle 140.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.470$, $\arg(\Gamma) = 140.4^\circ$ $\theta_{S1} = 168.8^\circ$; $\text{Im}(y_S) = -1.065$; $\theta_{P1} = 133.2^\circ$ **and** $\theta_{S2} = 50.8^\circ$; $\text{Im}(y_S) = 1.065$; $\theta_{P2} = 46.8^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.70dB$): $G(1,2) = G_1 + G_2 = 9.4 + 10.5 = 19.9dB$; $G(1,4) = G_1 + G_4 = 9.4 + 8.1 = 17.5dB$; $G(2,3) = G_2 + G_3 = 10.5 + 5.1 = 15.6dB$; $G(2,4) = G_2 + G_4 = 10.5 + 8.1 = 18.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.04dB=1.271$, $F_2 = 1.25dB=1.334$, $F_3 = 0.62dB=1.153$, $F_4 = 0.77dB=1.194$, $G_3 = 5.1dB=3.236$, $G_4 = 8.1dB=6.457$;

$F(4,1) = 1.194 + (1.271-1)/6.457 = 1.236 = 0.92dB$; $F(3,2) = 1.153 + (1.334-1)/3.236 = 1.257 = 0.99dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.1	$0.268 + j \cdot (-0.287)$	0.392	0.507	0.460
3.0	$0.177 + j \cdot (-0.477)$	0.509	0.297	0.326

b) $\mu(1.1GHz) > \mu(3.0GHz)$ so the transistor has better stability at 1.1 GHz

c) we use S parameters for f = 1.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 275.89 = 24.41dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.243$, $U_{minus} = -1.892dB$, $U_{plus} = 2.422dB$ (L8/2021, S142)

Subject no. 15

1. $z = 0.795 - j \cdot 0.735$; $Y = 1 / 50\Omega / (0.795 - j \cdot 0.735) = 0.0136S + j \cdot (0.0125)S$; $\Gamma = (z-1)/(z+1) = (0.795 - j \cdot 0.735 - 1)/(0.795 - j \cdot 0.735 + 1) = 0.046 + j \cdot (-0.391) = 0.393 \angle -83.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

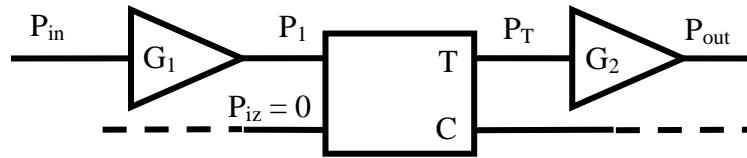2. $P_{in} = 2.85mW = 4.55dBm$; $P_1 = P_{in} + G_1 = 4.55dBm + 7.9dB = 12.45dBm = 17.57mW$; $P_c = P_1 - C = 12.45dBm - 5.15dB = 7.30dBm = 5.37mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.57mW - 5.37mW = 12.20mW = 10.87dBm$; $P_{out} = P_T + G_2 = 10.87dBm + 10.0dB = 20.87dBm = 122.05mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.210 + j \cdot 0.145 + 1) / [1 - (-0.210 + j \cdot 0.145)] = 31.47\Omega + j \cdot 9.76\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 15.74\Omega + j \cdot 4.88\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.513 + j \cdot 0.112 = 0.525 \angle 167.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.525$, $\arg(\Gamma) = 167.6^\circ$
 $\theta_{S1} = 157.0^\circ$; $\text{Im}(y_S) = -1.234$; $\theta_{P1} = 129.0^\circ$ **and** $\theta_{S2} = 35.3^\circ$; $\text{Im}(y_S) = 1.234$; $\theta_{P2} = 51.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.10dB$): $G(1,2) = G_1 + G_2 = 9.0 + 11.9 = 20.9dB$; $G(1,4) = G_1 + G_4 = 9.0 + 7.8 = 16.8dB$; $G(2,3) = G_2 + G_3 = 11.9 + 6.7 = 18.6dB$; $G(2,4) = G_2 + G_4 = 11.9 + 7.8 = 19.7dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.03dB = 1.268$, $F_2 = 1.24dB = 1.330$, $F_3 = 0.67dB = 1.167$, $F_4 = 0.71dB = 1.178$, $G_3 = 6.7dB = 4.677$, $G_4 = 7.8dB = 6.026$;

$F(4,1) = 1.178 + (1.268 - 1)/6.026 = 1.222 = 0.87dB$; $F(3,2) = 1.167 + (1.330 - 1)/4.677 = 1.237 = 0.93dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.2	$0.275 + j \cdot (-0.485)$	0.558	0.862	0.763
3.2	$-0.064 + j \cdot (-0.575)$	0.578	0.966	0.925

b) $\mu(2.2GHz) < \mu(3.2GHz)$ so the transistor has better stability at 3.2 GHz

c) we use S parameters for f = 3.2 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 34.28 = 15.35dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.152$, $U_{minus} = -1.231dB$, $U_{plus} = 1.435dB$ (L8/2021, S142)

Subject no. 16

1. $z = 0.810 - j \cdot 0.770$; $Y = 1 / 50\Omega / (0.810 - j \cdot 0.770) = 0.0130S + j \cdot (0.0123)S$; $\Gamma = (z-1)/(z+1) = (0.810 - j \cdot 0.770 - 1)/(0.810 - j \cdot 0.770 + 1) = 0.064 + j \cdot (-0.398) = 0.403 \angle -80.8^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

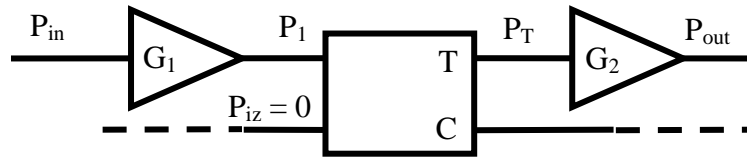2. $P_{in} = 3.75mW = 5.74dBm$; $P_1 = P_{in} + G_1 = 5.74dBm + 8.9dB = 14.64dBm = 29.11mW$; $P_c = P_1 - C = 14.64dBm - 6.55dB = 8.09dBm = 6.44mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 29.11mW - 6.44mW = 22.67mW = 13.55dBm$; $P_{out} = P_T + G_2 = 13.55dBm + 9.6dB = 23.15dBm = 206.73mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.099 + j \cdot 0.092 + 1)/[1 - (0.099 + j \cdot 0.092)] = 59.84\Omega + j \cdot 11.22\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 29.92\Omega + j \cdot 5.61\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.245 + j \cdot 0.087 = 0.260 \angle 160.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.260$, $\arg(\Gamma) = 160.4^\circ$
 $\theta_{S1} = 152.4^\circ$; $\text{Im}(y_S) = -0.539$; $\theta_{P1} = 151.7^\circ$ **and** $\theta_{S2} = 47.3^\circ$; $\text{Im}(y_S) = 0.539$; $\theta_{P2} = 28.3^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.30dB$): $G(1,2) = G_1 + G_2 = 8.0 + 10.7 = 18.7dB$; $G(1,4) = G_1 + G_4 = 8.0 + 7.7 = 15.7dB$; $G(2,3) = G_2 + G_3 = 10.7 + 5.0 = 15.7dB$; $G(2,4) = G_2 + G_4 = 10.7 + 7.7 = 18.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.00dB=1.259$, $F_2 = 1.25dB=1.334$, $F_3 = 0.52dB=1.127$, $F_4 = 0.71dB=1.178$, $G_3 = 5.0dB=3.162$, $G_4 = 7.7dB=5.888$;

$F(4,1) = 1.178 + (1.259-1)/5.888 = 1.222 = 0.87dB$; $F(3,2) = 1.127 + (1.334-1)/3.162 = 1.233 = 0.91dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
0.2	$0.324 + j \cdot (0.084)$	0.335	0.188	0.151
3.0	$0.007 + j \cdot (-0.572)$	0.572	0.952	0.900

b) $\mu(0.2GHz) < \mu(3.0GHz)$ so the transistor has better stability at 3.0 GHz

c) we use S parameters for f = 3.0 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 38.54 = 15.86dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.150$, $U_{minus} = -1.212dB$, $U_{plus} = 1.409dB$ (L8/2021, S142)

Subject no. 17

1. $z = 1.105 - j \cdot 1.140$; $Y = 1 / 50\Omega / (1.105 - j \cdot 1.140) = 0.0088S + j \cdot (0.0090)S$; $\Gamma = (z-1)/(z+1) = (1.105 - j \cdot 1.140 - 1)/(1.105 - j \cdot 1.140 + 1) = 0.265 + j \cdot (-0.398) = 0.478 \angle -56.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

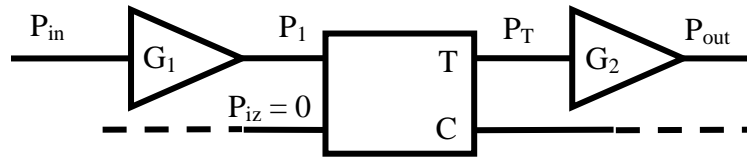2. $P_{in} = 1.75mW = 2.43dBm$; $P_1 = P_{in} + G_1 = 2.43dBm + 8.7dB = 11.13dBm = 12.97mW$; $P_c = P_1 - C = 11.13dBm - 4.30dB = 6.83dBm = 4.82mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 12.97mW - 4.82mW = 8.15mW = 9.11dBm$; $P_{out} = P_T + G_2 = 9.11dBm + 10.0dB = 19.11dBm = 81.53mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.065 + j \cdot 0.107 + 1)/[1 - (0.065 + j \cdot 0.107)] = 55.57\Omega + j \cdot 12.08\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 27.78\Omega + j \cdot 6.04\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.278 + j \cdot 0.099 = 0.295 \angle 160.3^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.295$, $\arg(\Gamma) = 160.3^\circ$
 $\theta_{S1} = 153.4^\circ$; $\text{Im}(y_S) = -0.618$; $\theta_{P1} = 148.3^\circ$ **and** $\theta_{S2} = 46.2^\circ$; $\text{Im}(y_S) = 0.618$; $\theta_{P2} = 31.7^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.70dB$): $G(1,2) = G_1 + G_2 = 9.9 + 11.4 = 21.3dB$; $G(1,4) = G_1 + G_4 = 9.9 + 7.1 = 17.0dB$; $G(2,3) = G_2 + G_3 = 11.4 + 5.9 = 17.3dB$; $G(2,4) = G_2 + G_4 = 11.4 + 7.1 = 18.5dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.03dB = 1.268$, $F_2 = 1.29dB = 1.346$, $F_3 = 0.68dB = 1.169$, $F_4 = 0.83dB = 1.211$, $G_3 = 5.9dB = 3.890$, $G_4 = 7.1dB = 5.129$;

$F(4,1) = 1.211 + (1.268 - 1)/5.129 = 1.263 = 1.01dB$; $F(3,2) = 1.169 + (1.346 - 1)/3.890 = 1.258 = 1.00dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.2	$0.093 + j \cdot (-0.339)$	0.351	0.800	0.755
3.1	$0.156 + j \cdot (-0.482)$	0.507	0.302	0.331

b) $\mu(2.2GHz) > \mu(3.1GHz)$ so the transistor has better stability at 2.2 GHz

c) we use S parameters for f = 2.2 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 71.34 = 18.53dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.079$, $U_{minus} = -0.663dB$, $U_{plus} = 0.718dB$ (L8/2021, S142)

Subject no. 18

1. $z = 0.810 - j \cdot 1.140$; $Y = 1 / 50\Omega / (0.810 - j \cdot 1.140) = 0.0083S + j \cdot (0.0117)S$; $\Gamma = (z-1)/(z+1) = (0.810 - j \cdot 1.140 - 1)/(0.810 - j \cdot 1.140 + 1) = 0.209 + j \cdot (-0.498) = 0.540 \angle -67.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

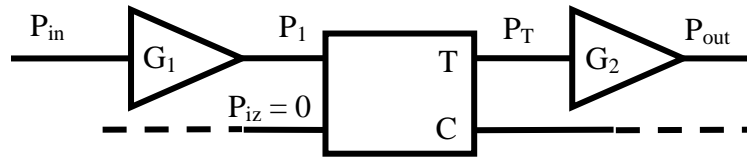2. $P_{in} = 3.45mW = 5.38dBm$; $P_1 = P_{in} + G_1 = 5.38dBm + 9.0dB = 14.38dBm = 27.40mW$; $P_c = P_1 - C = 14.38dBm - 4.60dB = 9.78dBm = 9.50mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 27.40mW - 9.50mW = 17.90mW = 12.53dBm$; $P_{out} = P_T + G_2 = 12.53dBm + 8.8dB = 21.33dBm = 135.80mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.503 + j \cdot 0.257 + 1)/[1 - (-0.503 + j \cdot 0.257)] = 14.64\Omega + j \cdot 11.05\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 7.32\Omega + j \cdot 5.53\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.728 + j \cdot 0.167 = 0.747 \angle 167.1^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.747$, $\arg(\Gamma) = 167.1^\circ$
 $\theta_{S1} = 165.6^\circ$; $\text{Im}(y_S) = -2.249$; $\theta_{P1} = 114.0^\circ$ **and** $\theta_{S2} = 27.3^\circ$; $\text{Im}(y_S) = 2.249$; $\theta_{P2} = 66.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.30dB$): $G(1,2) = G_1 + G_2 = 8.2 + 10.9 = 19.1dB$; $G(1,4) = G_1 + G_4 = 8.2 + 7.0 = 15.2dB$; $G(2,3) = G_2 + G_3 = 10.9 + 5.0 = 15.9dB$; $G(2,4) = G_2 + G_4 = 10.9 + 7.0 = 17.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.03dB = 1.268$, $F_2 = 1.14dB = 1.300$, $F_3 = 0.55dB = 1.135$, $F_4 = 0.79dB = 1.199$, $G_3 = 5.0dB = 3.162$, $G_4 = 7.0dB = 5.012$;

$F(4,1) = 1.199 + (1.268 - 1)/5.012 = 1.253 = 0.98dB$; $F(3,2) = 1.135 + (1.300 - 1)/3.162 = 1.230 = 0.90dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
0.8	$0.495 + j \cdot (-0.064)$	0.499	0.488	0.626
1.0	$0.490 + j \cdot (-0.218)$	0.536	0.130	0.895

b) $\mu'(0.8GHz) < \mu'(1.0GHz)$ so the transistor has better stability at 1.0 GHz

c) we use S parameters for f = 1.0 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 2196.07 = 33.42dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 2.578$, $U_{minus} = -11.073dB$, $U_{plus} = -3.963dB$ (L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 19

1. $z = 0.765 + j \cdot 1.005$; $Y = 1 / 50\Omega / (0.765 + j \cdot 1.005) = 0.0096S + j \cdot (-0.0126)S$; $\Gamma = (z-1)/(z+1) = (0.765 + j \cdot 1.005 - 1)/(0.765 + j \cdot 1.005 + 1) = 0.144 + j \cdot (0.487) = 0.508 \angle 73.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

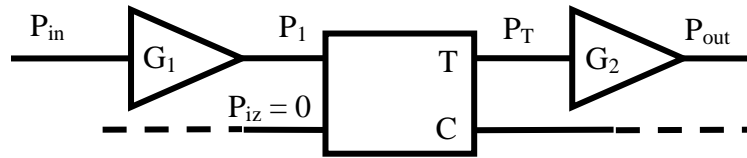2. $P_{in} = 4.05mW = 6.07dBm$; $P_1 = P_{in} + G_1 = 6.07dBm + 6.4dB = 12.47dBm = 17.68mW$; $P_c = P_1 - C = 12.47dBm - 6.80dB = 5.67dBm = 3.69mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.68mW - 3.69mW = 13.99mW = 11.46dBm$; $P_{out} = P_T + G_2 = 11.46dBm + 9.4dB = 20.86dBm = 121.81mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.281 + j \cdot 0.668 + 1)/[1 - (-0.281 + j \cdot 0.668)] = 11.37\Omega + j \cdot 32.00\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.69\Omega + j \cdot 16.00\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.659 + j \cdot 0.477 = 0.813 \angle 144.1^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.813$, $\arg(\Gamma) = 144.1^\circ$
 $\theta_{S1} = 0.1^\circ$; $\text{Im}(y_S) = -2.794$; $\theta_{P1} = 109.7^\circ$ **and** $\theta_{S2} = 35.7^\circ$; $\text{Im}(y_S) = 2.794$; $\theta_{P2} = 70.3^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.80dB$): $G(1,2) = G_1 + G_2 = 9.1 + 10.3 = 19.4dB$; $G(1,4) = G_1 + G_4 = 9.1 + 7.1 = 16.2dB$; $G(2,3) = G_2 + G_3 = 10.3 + 5.6 = 15.9dB$; $G(2,4) = G_2 + G_4 = 10.3 + 7.1 = 17.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.92dB = 1.236$, $F_2 = 1.27dB = 1.340$, $F_3 = 0.51dB = 1.125$, $F_4 = 0.70dB = 1.175$, $G_3 = 5.6dB = 3.631$, $G_4 = 7.1dB = 5.129$;

$F(4,1) = 1.175 + (1.236 - 1)/5.129 = 1.221 = 0.87dB$; $F(3,2) = 1.125 + (1.340 - 1)/3.631 = 1.218 = 0.86dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.9	$-0.024 + j \cdot (-0.347)$	0.348	0.922	0.951
1.8	$0.388 + j \cdot (-0.355)$	0.526	0.207	0.843

b) $\mu'(2.9GHz) > \mu'(1.8GHz)$ so the transistor has better stability at 2.9 GHz

c) we use S parameters for f = 2.9 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 42.21 = 16.25dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.049$, $U_{minus} = -0.418dB$, $U_{plus} = 0.439dB$ (L8/2021, S142)

Subject no. 20

1. $z = 1.230 - j \cdot 0.950$; $Y = 1 / 50\Omega / (1.230 - j \cdot 0.950) = 0.0102S + j \cdot (0.0079)S$; $\Gamma = (z-1)/(z+1) = (1.230 - j \cdot 0.950 - 1)/(1.230 - j \cdot 0.950 + 1) = 0.241 + j \cdot (-0.323) = 0.403 \angle -53.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

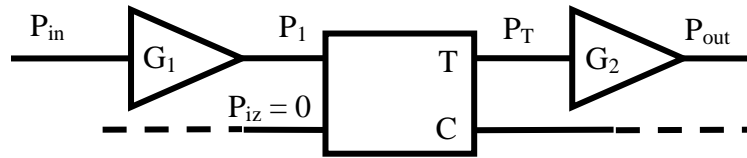2. $P_{in} = 3.75mW = 5.74dBm$; $P_1 = P_{in} + G_1 = 5.74dBm + 8.6dB = 14.34dBm = 27.17mW$; $P_c = P_1 - C = 14.34dBm - 4.40dB = 9.94dBm = 9.86mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 27.17mW - 9.86mW = 17.30mW = 12.38dBm$; $P_{out} = P_T + G_2 = 12.38dBm + 11.9dB = 24.28dBm = 267.99mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.193 + j \cdot 0.052 + 1)/[1 - (0.193 + j \cdot 0.052)] = 73.40\Omega + j \cdot 7.95\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 36.70\Omega + j \cdot 3.98\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.151 + j \cdot 0.053 = 0.160 \angle 160.7^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.160$, $\arg(\Gamma) = 160.7^\circ$
 $\theta_{S1} = 149.2^\circ$; $\text{Im}(y_S) = -0.324$; $\theta_{P1} = 162.0^\circ$ **and** $\theta_{S2} = 50.0^\circ$; $\text{Im}(y_S) = 0.324$; $\theta_{P2} = 18.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.70dB$): $G(1,2) = G_1 + G_2 = 9.6 + 10.5 = 20.1dB$; $G(1,4) = G_1 + G_4 = 9.6 + 7.3 = 16.9dB$; $G(2,3) = G_2 + G_3 = 10.5 + 6.0 = 16.5dB$; $G(2,4) = G_2 + G_4 = 10.5 + 7.3 = 17.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.98dB = 1.253$, $F_2 = 1.18dB = 1.312$, $F_3 = 0.58dB = 1.143$, $F_4 = 0.75dB = 1.189$, $G_3 = 6.0dB = 3.981$, $G_4 = 7.3dB = 5.370$;

$F(4,1) = 1.189 + (1.253 - 1)/5.370 = 1.236 = 0.92dB$; $F(3,2) = 1.143 + (1.312 - 1)/3.981 = 1.221 = 0.87dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.1	$0.493 + j \cdot (-0.174)$	0.523	0.609	0.699
1.1	$0.478 + j \cdot (-0.239)$	0.535	0.153	0.891

b) $\mu'(1.1GHz) < \mu'(1.1 GHz)$ so the transistor has better stability at 1.1 GHz

c) we use S parameters for f = 1.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 1668.44 = 32.22dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 2.099$, $U_{minus} = -9.825dB$, $U_{plus} = -0.821dB$ (L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 21

1. $z = 0.960 - j \cdot 0.850$; $Y = 1 / 50\Omega / (0.960 - j \cdot 0.850) = 0.0117S + j \cdot (0.0103)S$; $\Gamma = (z-1)/(z+1) = (0.960 - j \cdot 0.850 - 1)/(0.960 - j \cdot 0.850 + 1) = 0.141 + j \cdot (-0.372) = 0.398 \angle -69.2^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

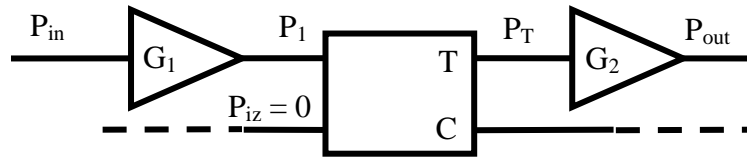2. $P_{in} = 1.10mW = 0.41dBm$; $P_1 = P_{in} + G_1 = 0.41dBm + 7.7dB = 8.11dBm = 6.48mW$; $P_c = P_1 - C = 8.11dBm - 4.50dB = 3.61dBm = 2.30mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 6.48mW - 2.30mW = 4.18mW = 6.21dBm$; $P_{out} = P_T + G_2 = 6.21dBm + 8.3dB = 14.51dBm = 28.25mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.367 + j \cdot 0.183 + 1)/[1 - (0.367 + j \cdot 0.183)] = 95.79\Omega + j \cdot 42.15\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 47.90\Omega + j \cdot 21.07\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.024 + j \cdot 0.210 = 0.211 \angle 83.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.211$, $\arg(\Gamma) = 83.6^\circ$
 $\theta_{S1} = 9.3^\circ$; $\text{Im}(y_S) = -0.433$; $\theta_{P1} = 156.6^\circ$ **and** $\theta_{S2} = 87.1^\circ$; $\text{Im}(y_S) = 0.433$; $\theta_{P2} = 23.4^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.50dB$): $G(1,2) = G_1 + G_2 = 8.8 + 10.6 = 19.4dB$; $G(1,4) = G_1 + G_4 = 8.8 + 7.3 = 16.1dB$; $G(2,3) = G_2 + G_3 = 10.6 + 6.5 = 17.1dB$; $G(2,4) = G_2 + G_4 = 10.6 + 7.3 = 17.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.92dB = 1.236$, $F_2 = 1.17dB = 1.309$, $F_3 = 0.53dB = 1.130$, $F_4 = 0.75dB = 1.189$, $G_3 = 6.5dB = 4.467$, $G_4 = 7.3dB = 5.370$;

$F(4,1) = 1.189 + (1.236 - 1)/5.370 = 1.232 = 0.91dB$; $F(3,2) = 1.130 + (1.309 - 1)/4.467 = 1.199 = 0.79dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.3	$0.232 + j \cdot (-0.294)$	0.374	0.576	0.712
1.7	$0.403 + j \cdot (-0.340)$	0.528	0.197	0.847

b) $\mu'(1.3GHz) < \mu'(1.7GHz)$ so the transistor has better stability at 1.7 GHz

c) we use S parameters for $f = 1.7GHz$ and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)

$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 856.64 = 29.33dB$


d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 1.640$, $U_{minus} = -8.432dB$, $U_{plus} = 3.876dB$

(L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 22

1. $z = 1.205 - j \cdot 1.270$; $Y = 1 / 50\Omega / (1.205 - j \cdot 1.270) = 0.0079S + j \cdot (0.0083)S$; $\Gamma = (z-1)/(z+1) = (1.205 - j \cdot 1.270 - 1)/(1.205 - j \cdot 1.270 + 1) = 0.319 + j \cdot (-0.392) = 0.506 \angle -50.9^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

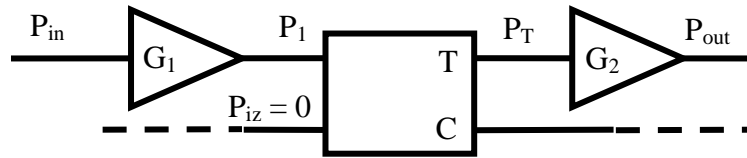2. $P_{in} = 3.30mW = 5.19dBm$; $P_1 = P_{in} + G_1 = 5.19dBm + 8.8dB = 13.99dBm = 25.03mW$; $P_c = P_1 - C = 13.99dBm - 5.00dB = 8.99dBm = 7.92mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 25.03mW - 7.92mW = 17.12mW = 12.33dBm$; $P_{out} = P_T + G_2 = 12.33dBm + 9.0dB = 21.33dBm = 135.96mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.606 + j \cdot 0.132 + 1)/[1 - (-0.606 + j \cdot 0.132)] = 11.85\Omega + j \cdot 5.08\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.92\Omega + j \cdot 2.54\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.784 + j \cdot 0.081 = 0.789 \angle 174.1^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.789$, $\arg(\Gamma) = 174.1^\circ$
 $\theta_{S1} = 164.0^\circ$; $\text{Im}(y_S) = -2.565$; $\theta_{P1} = 111.3^\circ$ **and** $\theta_{S2} = 21.9^\circ$; $\text{Im}(y_S) = 2.565$; $\theta_{P2} = 68.7^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.40dB$): $G(1,2) = G_1 + G_2 = 9.4 + 11.4 = 20.8dB$; $G(1,4) = G_1 + G_4 = 9.4 + 8.8 = 18.2dB$; $G(2,3) = G_2 + G_3 = 11.4 + 5.1 = 16.5dB$; $G(2,4) = G_2 + G_4 = 11.4 + 8.8 = 20.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.93dB = 1.239$, $F_2 = 1.24dB = 1.330$, $F_3 = 0.58dB = 1.143$, $F_4 = 0.85dB = 1.216$, $G_3 = 5.1dB = 3.236$, $G_4 = 8.8dB = 7.586$;

$F(4,1) = 1.216 + (1.239 - 1)/7.586 = 1.248 = 0.96dB$; $F(3,2) = 1.143 + (1.330 - 1)/3.236 = 1.245 = 0.95dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.0	$0.501 + j \cdot (-0.139)$	0.520	0.571	0.454
3.3	$-0.099 + j \cdot (-0.571)$	0.580	0.973	0.940

b) $\mu(1.0GHz) < \mu(3.3GHz)$ so the transistor has better stability at 3.3 GHz

c) we use S parameters for f = 3.3 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{T_{Umax}} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 32.49 = 15.12dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.153$, $U_{minus} = -1.239dB$, $U_{plus} = 1.445dB$ (L8/2021, S142)

Subject no. 23

1. $z = 1.195 + j \cdot 0.920$; $Y = 1 / 50\Omega / (1.195 + j \cdot 0.920) = 0.0105S + j \cdot (-0.0081)S$; $\Gamma = (z-1)/(z+1) = (1.195 + j \cdot 0.920 - 1)/(1.195 + j \cdot 0.920 + 1) = 0.225 + j \cdot (0.325) = 0.395 \angle 55.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

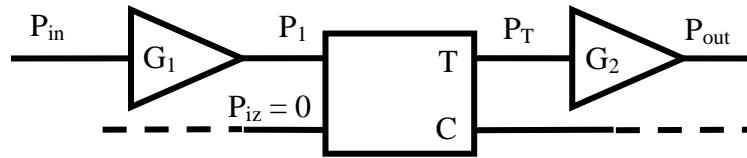2. $P_{in} = 3.15mW = 4.98dBm$; $P_1 = P_{in} + G_1 = 4.98dBm + 7.0dB = 11.98dBm = 15.79mW$; $P_c = P_1 - C = 11.98dBm - 4.55dB = 7.43dBm = 5.54mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 15.79mW - 5.54mW = 10.25mW = 10.11dBm$; $P_{out} = P_T + G_2 = 10.11dBm + 11.0dB = 21.11dBm = 129.04mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.334 + j \cdot 0.212 + 1)/[1 - (0.334 + j \cdot 0.212)] = 86.34\Omega + j \cdot 43.40\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 43.17\Omega + j \cdot 21.70\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.018 + j \cdot 0.237 = 0.238 \angle 94.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.238$, $\arg(\Gamma) = 94.4^\circ$; $\theta_{S1} = 4.7^\circ$; $\text{Im}(y_S) = -0.490$; $\theta_{P1} = 153.9^\circ$ **and** $\theta_{S2} = 80.9^\circ$; $\text{Im}(y_S) = 0.490$; $\theta_{P2} = 26.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.65dB$): $G(1,2) = G_1 + G_2 = 8.9 + 11.7 = 20.6dB$; $G(1,4) = G_1 + G_4 = 8.9 + 8.3 = 17.2dB$; $G(2,3) = G_2 + G_3 = 11.7 + 5.5 = 17.2dB$; $G(2,4) = G_2 + G_4 = 11.7 + 8.3 = 20.0dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.05dB = 1.274$, $F_2 = 1.15dB = 1.303$, $F_3 = 0.52dB = 1.127$, $F_4 = 0.85dB = 1.216$, $G_3 = 5.5dB = 3.548$, $G_4 = 8.3dB = 6.761$;

$F(4,1) = 1.216 + (1.274 - 1)/6.761 = 1.257 = 0.99dB$; $F(3,2) = 1.127 + (1.303 - 1)/3.548 = 1.213 = 0.84dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.1	$0.305 + j \cdot (-0.466)$	0.557	0.848	0.872
3.6	$0.064 + j \cdot (-0.493)$	0.497	0.350	0.785

b) $\mu'(2.1GHz) > \mu'(3.6GHz)$ so the transistor has better stability at 2.1 GHz

c) we use S parameters for f = 2.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 74.31 = 18.71dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.165$, $U_{minus} = -1.325dB$, $U_{plus} = 1.563dB$ (L8/2021, S142)

Subject no. 24

1. $z = 1.100 + j \cdot 1.285$; $Y = 1 / 50\Omega / (1.100 + j \cdot 1.285) = 0.0077S + j \cdot (-0.0090)S$; $\Gamma = (z-1)/(z+1) = (1.100 + j \cdot 1.285 - 1)/(1.100 + j \cdot 1.285 + 1) = 0.307 + j \cdot (0.424) = 0.524 \angle 54.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

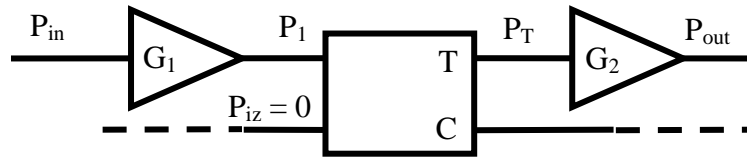2. $P_{in} = 3.65mW = 5.62dBm$; $P_1 = P_{in} + G_1 = 5.62dBm + 9.0dB = 14.62dBm = 28.99mW$; $P_c = P_1 - C = 14.62dBm - 4.70dB = 9.92dBm = 9.82mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 28.99mW - 9.82mW = 19.17mW = 12.83dBm$; $P_{out} = P_T + G_2 = 12.83dBm + 9.1dB = 21.93dBm = 155.81mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.415 + j \cdot 0.337 + 1)/[1 - (-0.415 + j \cdot 0.337)] = 16.88\Omega + j \cdot 15.93\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 8.44\Omega + j \cdot 7.96\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.680 + j \cdot 0.229 = 0.717 \angle 161.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.717$, $\arg(\Gamma) = 161.4^\circ$
 $\theta_{S1} = 167.2^\circ$; $\text{Im}(y_S) = -2.060$; $\theta_{P1} = 115.9^\circ$ **and** $\theta_{S2} = 31.4^\circ$; $\text{Im}(y_S) = 2.060$; $\theta_{P2} = 64.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.25dB$): $G(1,2) = G_1 + G_2 = 9.2 + 11.7 = 20.9dB$; $G(1,4) = G_1 + G_4 = 9.2 + 7.2 = 16.4dB$; $G(2,3) = G_2 + G_3 = 11.7 + 6.2 = 17.9dB$; $G(2,4) = G_2 + G_4 = 11.7 + 7.2 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.91dB = 1.233$, $F_2 = 1.19dB = 1.315$, $F_3 = 0.57dB = 1.140$, $F_4 = 0.84dB = 1.213$, $G_3 = 6.2dB = 4.169$, $G_4 = 7.2dB = 5.248$;

$F(4,1) = 1.213 + (1.233 - 1)/5.248 = 1.258 = 1.00dB$; $F(3,2) = 1.140 + (1.315 - 1)/4.169 = 1.216 = 0.85dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
3.0	$-0.041 + j \cdot (-0.349)$	0.352	0.933	0.958
2.3	$0.306 + j \cdot (-0.420)$	0.519	0.245	0.818

b) $\mu'(3.0GHz) > \mu'(2.3GHz)$ so the transistor has better stability at 3.0 GHz

c) we use S parameters for f = 3.0 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 39.53 = 15.97dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.047$, $U_{minus} = -0.398dB$, $U_{plus} = 0.417dB$ (L8/2021, S142)

Subject no. 25

1. $z = 1.035 + j \cdot 0.820$; $Y = 1 / 50\Omega / (1.035 + j \cdot 0.820) = 0.0119S + j \cdot (-0.0094)S$; $\Gamma = (z-1)/(z+1) = (1.035 + j \cdot 0.820 - 1)/(1.035 + j \cdot 0.820 + 1) = 0.154 + j \cdot (0.341) = 0.374 \angle 65.6^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

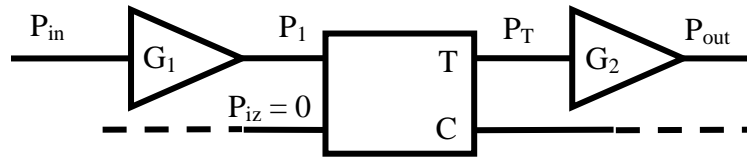2. $P_{in} = 1.20mW = 0.79dBm$; $P_1 = P_{in} + G_1 = 0.79dBm + 8.4dB = 9.19dBm = 8.30mW$; $P_c = P_1 - C = 9.19dBm - 6.40dB = 2.79dBm = 1.90mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.30mW - 1.90mW = 6.40mW = 8.06dBm$; $P_{out} = P_T + G_2 = 8.06dBm + 10.6dB = 18.66dBm = 73.48mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.658 + j \cdot 0.359 + 1)/[1 - (0.658 + j \cdot 0.359)] = 89.11\Omega + j \cdot 146.03\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 44.56\Omega + j \cdot 73.01\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.337 + j \cdot 0.512 = 0.613 \angle 56.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.613$, $\arg(\Gamma) = 56.6^\circ$; $\theta_{S1} = 35.6^\circ$; $\text{Im}(y_S) = -1.551$; $\theta_{P1} = 122.8^\circ$ **and** $\theta_{S2} = 87.8^\circ$; $\text{Im}(y_S) = 1.551$; $\theta_{P2} = 57.2^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.40dB$): $G(1,2) = G_1 + G_2 = 8.3 + 10.2 = 18.5dB$; $G(1,4) = G_1 + G_4 = 8.3 + 7.3 = 15.6dB$; $G(2,3) = G_2 + G_3 = 10.2 + 5.9 = 16.1dB$; $G(2,4) = G_2 + G_4 = 10.2 + 7.3 = 17.5dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.99dB = 1.256$, $F_2 = 1.23dB = 1.327$, $F_3 = 0.60dB = 1.148$, $F_4 = 0.81dB = 1.205$, $G_3 = 5.9dB = 3.890$, $G_4 = 7.3dB = 5.370$;

$F(4,1) = 1.205 + (1.256 - 1)/5.370 = 1.253 = 0.98dB$; $F(3,2) = 1.148 + (1.327 - 1)/3.890 = 1.232 = 0.91dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
1.5	$0.444 + j \cdot (-0.307)$	0.540	0.727	0.781
4.6	$-0.112 + j \cdot (-0.459)$	0.472	0.461	0.791

b) $\mu'(1.5GHz) < \mu'(4.6GHz)$ so the transistor has better stability at 4.6 GHz

c) we use S parameters for f = 4.6 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 141.31 = 21.50dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.555$, $U_{minus} = -3.833dB$, $U_{plus} = 7.028dB$ (L8/2021, S142)

Subject no. 26

1. $z = 0.720 + j \cdot 1.235$; $Y = 1 / 50\Omega / (0.720 + j \cdot 1.235) = 0.0070S + j \cdot (-0.0121)S$; $\Gamma = (z-1)/(z+1) = (0.720 + j \cdot 1.235 - 1)/(0.720 + j \cdot 1.235 + 1) = 0.233 + j \cdot (-0.551) = 0.598 \angle 67.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

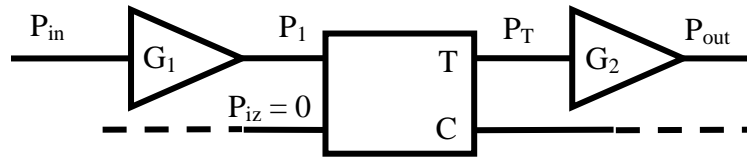2. $P_{in} = 1.75mW = 2.43dBm$; $P_1 = P_{in} + G_1 = 2.43dBm + 7.0dB = 9.43dBm = 8.77mW$; $P_c = P_1 - C = 9.43dBm - 5.95dB = 3.48dBm = 2.23mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.77mW - 2.23mW = 6.54mW = 8.16dBm$; $P_{out} = P_T + G_2 = 8.16dBm + 9.7dB = 17.86dBm = 61.05mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.351 + j \cdot 0.499 + 1)/[1 - (0.351 + j \cdot 0.499)] = 46.84\Omega + j \cdot 74.46\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 23.42\Omega + j \cdot 37.23\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.083 + j \cdot 0.549 = 0.556 \angle 98.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.556$, $\arg(\Gamma) = 98.6^\circ$; $\theta_{S1} = 12.6^\circ$; $\text{Im}(y_S) = -1.337$; $\theta_{P1} = 126.8^\circ$ **and** $\theta_{S2} = 68.8^\circ$; $\text{Im}(y_S) = 1.337$; $\theta_{P2} = 53.2^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.80dB$): $G(1,2) = G_1 + G_2 = 8.5 + 10.7 = 19.2dB$; $G(1,4) = G_1 + G_4 = 8.5 + 8.2 = 16.7dB$; $G(2,3) = G_2 + G_3 = 10.7 + 5.8 = 16.5dB$; $G(2,4) = G_2 + G_4 = 10.7 + 8.2 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.90dB = 1.230$, $F_2 = 1.20dB = 1.318$, $F_3 = 0.60dB = 1.148$, $F_4 = 0.84dB = 1.213$, $G_3 = 5.8dB = 3.802$, $G_4 = 8.2dB = 6.607$;

$F(4,1) = 1.213 + (1.230 - 1)/6.607 = 1.248 = 0.96dB$; $F(3,2) = 1.148 + (1.318 - 1)/3.802 = 1.232 = 0.91dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.9	$0.357 + j \cdot (-0.418)$	0.550	0.811	0.698
2.7	$0.233 + j \cdot (-0.458)$	0.513	0.279	0.306

b) $\mu(1.9GHz) > \mu(2.7GHz)$ so the transistor has better stability at 1.9 GHz

c) we use S parameters for f = 1.9 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 90.26 = 19.56dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.175$, $U_{minus} = -1.398dB$, $U_{plus} = 1.666dB$ (L8/2021, S142)

Subject no. 27

1. $z = 1.220 - j \cdot 0.980$; $Y = 1 / 50\Omega / (1.220 - j \cdot 0.980) = 0.0100S + j \cdot (0.0080)S$; $\Gamma = (z-1)/(z+1) = (1.220 - j \cdot 0.980 - 1)/(1.220 - j \cdot 0.980 + 1) = 0.246 + j \cdot (-0.333) = 0.414 \angle -53.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

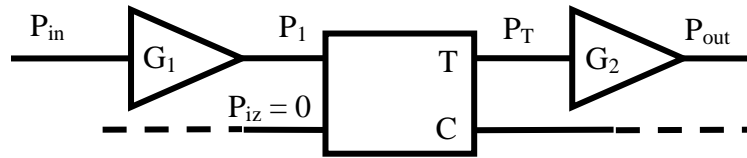2. $P_{in} = 3.90mW = 5.91dBm$; $P_1 = P_{in} + G_1 = 5.91dBm + 7.1dB = 13.01dBm = 20.00mW$; $P_c = P_1 - C = 13.01dBm - 5.75dB = 7.26dBm = 5.32mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 20.00mW - 5.32mW = 14.68mW = 11.67dBm$; $P_{out} = P_T + G_2 = 11.67dBm + 10.7dB = 22.37dBm = 172.47mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.498 + j \cdot 0.110 + 1)/[1 - (0.498 + j \cdot 0.110)] = 140.08\Omega + j \cdot 41.65\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 70.04\Omega + j \cdot 20.83\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.191 + j \cdot 0.140 = 0.237 \angle 36.3^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.237$, $\arg(\Gamma) = 36.3^\circ$; $\theta_{S1} = 33.7^\circ$; $\text{Im}(y_S) = -0.488$; $\theta_{P1} = 154.0^\circ$ **and** $\theta_{S2} = 110.0^\circ$; $\text{Im}(y_S) = 0.488$; $\theta_{P2} = 26.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 14.95dB$): $G(1,2) = G_1 + G_2 = 8.3 + 11.9 = 20.2dB$; $G(1,4) = G_1 + G_4 = 8.3 + 7.3 = 15.6dB$; $G(2,3) = G_2 + G_3 = 11.9 + 6.1 = 18.0dB$; $G(2,4) = G_2 + G_4 = 11.9 + 7.3 = 19.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.99dB = 1.256$, $F_2 = 1.10dB = 1.288$, $F_3 = 0.65dB = 1.161$, $F_4 = 0.74dB = 1.186$, $G_3 = 6.1dB = 4.074$, $G_4 = 7.3dB = 5.370$;

$F(4,1) = 1.186 + (1.256 - 1)/5.370 = 1.233 = 0.91dB$; $F(3,2) = 1.161 + (1.288 - 1)/4.074 = 1.232 = 0.91dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
0.7	$0.482 + j \cdot (-0.024)$	0.483	0.443	0.604
4.5	$-0.093 + j \cdot (-0.467)$	0.476	0.442	0.785

b) $\mu'(0.7GHz) < \mu'(4.5GHz)$ so the transistor has better stability at 4.5 GHz

c) we use S parameters for f = 4.5 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{T_{Umax}} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 149.13 = 21.74dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.589$, $U_{minus} = -4.021dB$, $U_{plus} = 7.716dB$ (L8/2021, S142)

Subject no. 28

1. $z = 1.095 + j \cdot 1.065$; $Y = 1 / 50\Omega / (1.095 + j \cdot 1.065) = 0.0094S + j \cdot (-0.0091)S$; $\Gamma = (z-1)/(z+1) = (1.095 + j \cdot 1.065 - 1)/(1.095 + j \cdot 1.065 + 1) = 0.241 + j \cdot (0.386) = 0.455 \angle 58.0^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

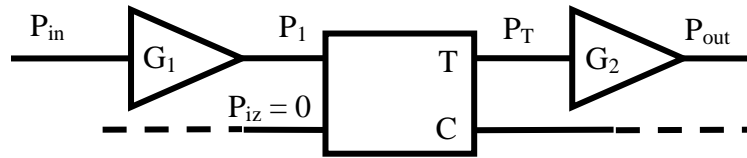2. $P_{in} = 2.65mW = 4.23dBm$; $P_1 = P_{in} + G_1 = 4.23dBm + 8.1dB = 12.33dBm = 17.11mW$; $P_c = P_1 - C = 12.33dBm - 4.45dB = 7.88dBm = 6.14mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.11mW - 6.14mW = 10.97mW = 10.40dBm$; $P_{out} = P_T + G_2 = 10.40dBm + 11.1dB = 21.50dBm = 141.30mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.018 + j \cdot 0.720 + 1)/[1 - (-0.018 + j \cdot 0.720)] = 15.48\Omega + j \cdot 46.31\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 7.74\Omega + j \cdot 23.16\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.492 + j \cdot 0.598 = 0.775 \angle 129.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.775$, $\arg(\Gamma) = 129.4^\circ$
 $\theta_{S1} = 5.7^\circ$; $\text{Im}(y_S) = -2.450$; $\theta_{P1} = 112.2^\circ$ **and** $\theta_{S2} = 44.9^\circ$; $\text{Im}(y_S) = 2.450$; $\theta_{P2} = 67.8^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.30dB$): $G(1,2) = G_1 + G_2 = 8.6 + 10.0 = 18.6dB$; $G(1,4) = G_1 + G_4 = 8.6 + 7.0 = 15.6dB$; $G(2,3) = G_2 + G_3 = 10.0 + 6.5 = 16.5dB$; $G(2,4) = G_2 + G_4 = 10.0 + 7.0 = 17.0dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.93dB = 1.239$, $F_2 = 1.16dB = 1.306$, $F_3 = 0.67dB = 1.167$, $F_4 = 0.78dB = 1.197$, $G_3 = 6.5dB = 4.467$, $G_4 = 7.0dB = 5.012$;

$F(4,1) = 1.197 + (1.239 - 1)/5.012 = 1.244 = 0.95dB$; $F(3,2) = 1.167 + (1.306 - 1)/4.467 = 1.235 = 0.92dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.0	$0.334 + j \cdot (-0.446)$	0.557	0.828	0.856
0.9	$0.498 + j \cdot (-0.203)$	0.538	0.121	0.909

b) $\mu'(2.0GHz) < \mu'(0.9GHz)$ so the transistor has better stability at 0.9 GHz

c) we use S parameters for f = 0.9 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 2614.62 = 34.17dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 2.639$, $U_{minus} = -11.220dB$, $U_{plus} = -4.292dB$ (L8/2021, S142) (irrelevant plus gain deviation, $U > 1$)

Subject no. 29

1. $z = 1.010 - j \cdot 1.015$; $Y = 1 / 50\Omega / (1.010 - j \cdot 1.015) = 0.0099S + j \cdot (0.0099)S$; $\Gamma = (z-1)/(z+1) = (1.010 - j \cdot 1.015 - 1)/(1.010 - j \cdot 1.015 + 1) = 0.207 + j \cdot (-0.400) = 0.451 \angle -62.6^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

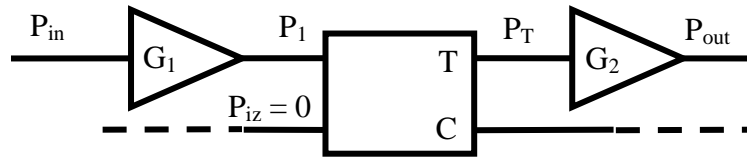2. $P_{in} = 2.65mW = 4.23dBm$; $P_1 = P_{in} + G_1 = 4.23dBm + 9.9dB = 14.13dBm = 25.90mW$; $P_c = P_1 - C = 14.13dBm - 5.70dB = 8.43dBm = 6.97mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 25.90mW - 6.97mW = 18.93mW = 12.77dBm$; $P_{out} = P_T + G_2 = 12.77dBm + 8.8dB = 21.57dBm = 143.57mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.485 + j \cdot 0.279 + 1)/[1 - (0.485 + j \cdot 0.279)] = 100.12\Omega + j \cdot 81.33\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 50.06\Omega + j \cdot 40.66\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = 0.142 + j \cdot 0.349 = 0.376 \angle 67.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.376$, $\arg(\Gamma) = 67.8^\circ$
 $\theta_{S1} = 22.2^\circ$; $\text{Im}(y_S) = -0.813$; $\theta_{P1} = 140.9^\circ$ **and** $\theta_{S2} = 90.0^\circ$; $\text{Im}(y_S) = 0.813$; $\theta_{P2} = 39.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.10dB$): $G(1,2) = G_1 + G_2 = 9.3 + 11.0 = 20.3dB$; $G(1,4) = G_1 + G_4 = 9.3 + 8.6 = 17.9dB$; $G(2,3) = G_2 + G_3 = 11.0 + 5.3 = 16.3dB$; $G(2,4) = G_2 + G_4 = 11.0 + 8.6 = 19.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.08dB=1.282$, $F_2 = 1.28dB=1.343$, $F_3 = 0.64dB=1.159$, $F_4 = 0.76dB=1.191$, $G_3 = 5.3dB=3.388$, $G_4 = 8.6dB=7.244$;

$F(4,1) = 1.191 + (1.282-1)/7.244 = 1.230 = 0.90dB$; $F(3,2) = 1.159 + (1.343-1)/3.388 = 1.260 = 1.00dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.3	$0.245 + j \cdot (-0.506)$	0.563	0.874	0.893
1.2	$0.466 + j \cdot (-0.259)$	0.533	0.162	0.886

b) $\mu'(2.3GHz) > \mu'(1.2 GHz)$ so the transistor has better stability at 2.3 GHz

c) we use S parameters for f = 2.3 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 62.71 = 17.97dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.159$, $U_{minus} = -1.285dB$, $U_{plus} = 1.508dB$ (L8/2021, S142)

Subject no. 30

1. $z = 1.260 + j \cdot 1.295$; $Y = 1 / 50\Omega / (1.260 + j \cdot 1.295) = 0.0077S + j \cdot (-0.0079)S$; $\Gamma = (z-1)/(z+1) = (1.260 + j \cdot 1.295 - 1)/(1.260 + j \cdot 1.295 + 1) = 0.334 + j \cdot (0.382) = 0.507 \angle 48.8^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

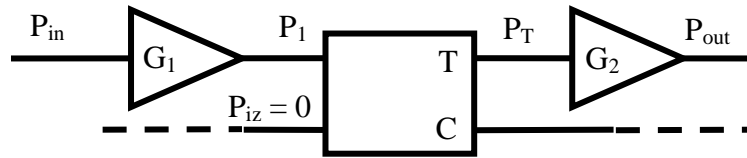2. $P_{in} = 2.85mW = 4.55dBm$; $P_1 = P_{in} + G_1 = 4.55dBm + 8.0dB = 12.55dBm = 17.98mW$; $P_c = P_1 - C = 12.55dBm - 6.15dB = 6.40dBm = 4.36mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.98mW - 4.36mW = 13.62mW = 11.34dBm$; $P_{out} = P_T + G_2 = 11.34dBm + 11.7dB = 23.04dBm = 201.44mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.072 + j \cdot 0.459 + 1)/[1 - (-0.072 + j \cdot 0.459)] = 28.83\Omega + j \cdot 33.75\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 14.42\Omega + j \cdot 16.88\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.453 + j \cdot 0.381 = 0.591 \angle 139.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.591$, $\arg(\Gamma) = 139.9^\circ$ $\theta_{S1} = 173.2^\circ$; $\text{Im}(y_S) = -1.467$; $\theta_{P1} = 124.3^\circ$ **and** $\theta_{S2} = 46.9^\circ$; $\text{Im}(y_S) = 1.467$; $\theta_{P2} = 55.7^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.35dB$): $G(1,2) = G_1 + G_2 = 9.9 + 11.1 = 21.0dB$; $G(1,4) = G_1 + G_4 = 9.9 + 7.6 = 17.5dB$; $G(2,3) = G_2 + G_3 = 11.1 + 6.4 = 17.5dB$; $G(2,4) = G_2 + G_4 = 11.1 + 7.6 = 18.7dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.94dB=1.242$, $F_2 = 1.27dB=1.340$, $F_3 = 0.67dB=1.167$, $F_4 = 0.79dB=1.199$, $G_3 = 6.4dB=4.365$, $G_4 = 7.6dB=5.754$;

$F(4,1) = 1.199 + (1.242-1)/5.754 = 1.241 = 0.94dB$; $F(3,2) = 1.167 + (1.340-1)/4.365 = 1.245 = 0.95dB$; $F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.5	$0.200 + j \cdot (-0.302)$	0.362	0.635	0.586
5.0	$-0.166 + j \cdot (-0.425)$	0.457	0.515	0.550

b) $\mu(1.5GHz) > \mu(5.0GHz)$ so the transistor has better stability at 1.5 GHz

c) we use S parameters for f = 1.5 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 149.06 = 21.73dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.144$, $U_{minus} = -1.171dB$, $U_{plus} = 1.354dB$ (L8/2021, S142)

Subject no. 31

1. $z = 1.120 - j \cdot 1.025$; $Y = 1 / 50\Omega / (1.120 - j \cdot 1.025) = 0.0097S + j \cdot (0.0089)S$; $\Gamma = (z-1)/(z+1) = (1.120 - j \cdot 1.025 - 1)/(1.120 - j \cdot 1.025 + 1) = 0.235 + j \cdot (-0.370) = 0.438 \angle -57.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

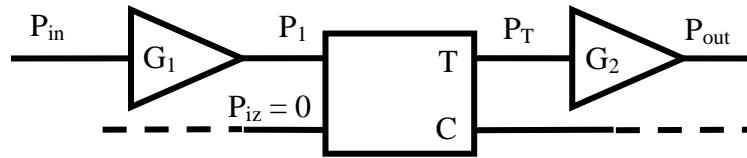2. $P_{in} = 4.05mW = 6.07dBm$; $P_1 = P_{in} + G_1 = 6.07dBm + 9.5dB = 15.57dBm = 36.10mW$; $P_c = P_1 - C = 15.57dBm - 5.35dB = 10.22dBm = 10.53mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 36.10mW - 10.53mW = 25.57mW = 14.08dBm$; $P_{out} = P_T + G_2 = 14.08dBm + 10.3dB = 24.38dBm = 273.93mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.066 + j \cdot 0.323 + 1)/[1 - (0.066 + j \cdot 0.323)] = 45.63\Omega + j \cdot 33.07\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 22.81\Omega + j \cdot 16.54\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.306 + j \cdot 0.297 = 0.426 \angle 135.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.426$, $\arg(\Gamma) = 135.9^\circ$ $\theta_{S1} = 169.7^\circ$; $\text{Im}(y_S) = -0.942$; $\theta_{P1} = 136.7^\circ$ **and** $\theta_{S2} = 54.4^\circ$; $\text{Im}(y_S) = 0.942$; $\theta_{P2} = 43.3^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.65dB$): $G(1,2) = G_1 + G_2 = 8.5 + 11.8 = 20.3dB$; $G(1,4) = G_1 + G_4 = 8.5 + 7.8 = 16.3dB$; $G(2,3) = G_2 + G_3 = 11.8 + 5.7 = 17.5dB$; $G(2,4) = G_2 + G_4 = 11.8 + 7.8 = 19.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.99dB=1.256$, $F_2 = 1.12dB=1.294$, $F_3 = 0.67dB=1.167$, $F_4 = 0.72dB=1.180$, $G_3 = 5.7dB=3.715$, $G_4 = 7.8dB=6.026$;

$F(4,1) = 1.180 + (1.256-1)/6.026 = 1.223 = 0.87dB$; $F(3,2) = 1.167 + (1.294-1)/3.715 = 1.246 = 0.96dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.7	$0.408 + j \cdot (-0.368)$	0.549	0.770	0.649
4.9	$-0.151 + j \cdot (-0.435)$	0.461	0.497	0.530

b) $\mu(1.7GHz) > \mu(4.9GHz)$ so the transistor has better stability at 1.7 GHz

c) we use S parameters for f = 1.7 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 111.05 = 20.46dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.190$, $U_{minus} = -1.508dB$, $U_{plus} = 1.827dB$ (L8/2021, S142)

Subject no. 32

1. $z = 0.925 - j \cdot 0.760$; $Y = 1 / 50\Omega / (0.925 - j \cdot 0.760) = 0.0129S + j \cdot (0.0106)S$; $\Gamma = (z-1)/(z+1) = (0.925 - j \cdot 0.760 - 1)/(0.925 - j \cdot 0.760 + 1) = 0.101 + j \cdot (-0.355) = 0.369 \angle -74.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

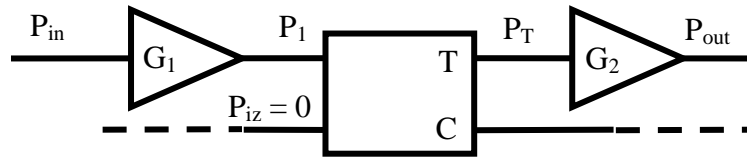2. $P_{in} = 1.15mW = 0.61dBm$; $P_1 = P_{in} + G_1 = 0.61dBm + 9.6dB = 10.21dBm = 10.49mW$; $P_c = P_1 - C = 10.21dBm - 6.95dB = 3.26dBm = 2.12mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 10.49mW - 2.12mW = 8.37mW = 9.23dBm$; $P_{out} = P_T + G_2 = 9.23dBm + 10.7dB = 19.93dBm = 98.35mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.093 + j \cdot 0.067 + 1)/[1 - (0.093 + j \cdot 0.067)] = 59.66\Omega + j \cdot 8.10\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 29.83\Omega + j \cdot 4.05\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.249 + j \cdot 0.063 = 0.257 \angle 165.7^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.257$, $\arg(\Gamma) = 165.7^\circ$
 $\theta_{S1} = 149.6^\circ$; $\text{Im}(y_S) = -0.533$; $\theta_{P1} = 152.0^\circ$ **and** $\theta_{S2} = 44.7^\circ$; $\text{Im}(y_S) = 0.533$; $\theta_{P2} = 28.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 17.25dB$): $G(1,2) = G_1 + G_2 = 9.8 + 10.7 = 20.5dB$; $G(1,4) = G_1 + G_4 = 9.8 + 7.9 = 17.7dB$; $G(2,3) = G_2 + G_3 = 10.7 + 6.8 = 17.5dB$; $G(2,4) = G_2 + G_4 = 10.7 + 7.9 = 18.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.06dB=1.276$, $F_2 = 1.20dB=1.318$, $F_3 = 0.56dB=1.138$, $F_4 = 0.72dB=1.180$, $G_3 = 6.8dB=4.786$, $G_4 = 7.9dB=6.166$;

$F(4,1) = 1.180 + (1.276-1)/6.166 = 1.225 = 0.88dB$; $F(3,2) = 1.138 + (1.318-1)/4.786 = 1.204 = 0.81dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.0	$0.125 + j \cdot (-0.330)$	0.353	0.760	0.713
2.2	$0.325 + j \cdot (-0.407)$	0.521	0.243	0.269

b) $\mu(2.0GHz) > \mu(2.2GHz)$ so the transistor has better stability at 2.0 GHz

c) we use S parameters for f = 2.0 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 85.05 = 19.30dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.092$, $U_{minus} = -0.761dB$, $U_{plus} = 0.835dB$ (L8/2021, S142)

Subject no. 33

1. $z = 1.095 - j \cdot 0.755$; $Y = 1 / 50\Omega / (1.095 - j \cdot 0.755) = 0.0124S + j \cdot (0.0085)S$; $\Gamma = (z-1)/(z+1) = (1.095 - j \cdot 0.755 - 1)/(1.095 - j \cdot 0.755 + 1) = 0.155 + j \cdot (-0.304) = 0.342 \angle -63.0^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

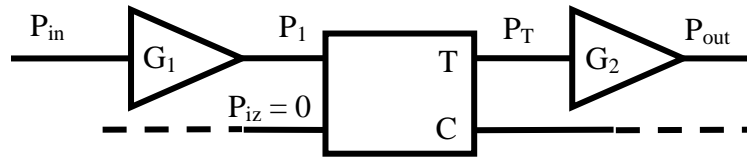2. $P_{in} = 1.95mW = 2.90dBm$; $P_1 = P_{in} + G_1 = 2.90dBm + 8.2dB = 11.10dBm = 12.88mW$; $P_c = P_1 - C = 11.10dBm - 5.55dB = 5.55dBm = 3.59mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 12.88mW - 3.59mW = 9.29mW = 9.68dBm$; $P_{out} = P_T + G_2 = 9.68dBm + 10.4dB = 20.08dBm = 101.91mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.623 + j \cdot 0.246 + 1)/[1 - (-0.623 + j \cdot 0.246)] = 10.23\Omega + j \cdot 9.13\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.12\Omega + j \cdot 4.56\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.802 + j \cdot 0.149 = 0.816 \angle 169.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.816$, $\arg(\Gamma) = 169.5^\circ$
 $\theta_{S1} = 167.6^\circ$; $\text{Im}(y_S) = -2.821$; $\theta_{P1} = 109.5^\circ$ **and** $\theta_{S2} = 22.9^\circ$; $\text{Im}(y_S) = 2.821$; $\theta_{P2} = 70.5^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.65dB$): $G(1,2) = G_1 + G_2 = 8.6 + 10.2 = 18.8dB$; $G(1,4) = G_1 + G_4 = 8.6 + 7.8 = 16.4dB$; $G(2,3) = G_2 + G_3 = 10.2 + 6.0 = 16.2dB$; $G(2,4) = G_2 + G_4 = 10.2 + 7.8 = 18.0dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.08dB = 1.282$, $F_2 = 1.18dB = 1.312$, $F_3 = 0.55dB = 1.135$, $F_4 = 0.71dB = 1.178$, $G_3 = 6.0dB = 3.981$, $G_4 = 7.8dB = 6.026$;

$F(4,1) = 1.178 + (1.282 - 1)/6.026 = 1.224 = 0.88dB$; $F(3,2) = 1.135 + (1.312 - 1)/3.981 = 1.213 = 0.84dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
0.4	$0.402 + j \cdot (0.068)$	0.408	0.250	0.557
5.3	$-0.201 + j \cdot (-0.397)$	0.445	0.556	0.813

b) $\mu'(0.4GHz) < \mu'(5.3GHz)$ so the transistor has better stability at 5.3 GHz

c) we use S parameters for f = 5.3 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 99.58 = 19.98dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.408$, $U_{minus} = -2.972dB$, $U_{plus} = 4.553dB$ (L8/2021, S142)

Subject no. 34

1. $z = 1.005 + j \cdot 1.000$; $Y = 1 / 50\Omega / (1.005 + j \cdot 1.000) = 0.0100S + j \cdot (-0.0100)S$; $\Gamma = (z-1)/(z+1) = (1.005 + j \cdot 1.000 - 1)/(1.005 + j \cdot 1.000 + 1) = 0.201 + j \cdot (0.398) = 0.446 \angle 63.2^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

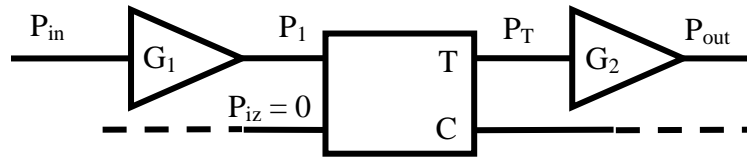2. $P_{in} = 1.20mW = 0.79dBm$; $P_1 = P_{in} + G_1 = 0.79dBm + 6.1dB = 6.89dBm = 4.89mW$; $P_c = P_1 - C = 6.89dBm - 6.60dB = 0.29dBm = 1.07mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 4.89mW - 1.07mW = 3.82mW = 5.82dBm$; $P_{out} = P_T + G_2 = 5.82dBm + 11.3dB = 17.12dBm = 51.52mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.077 + j \cdot 0.311 + 1)/[1 - (-0.077 + j \cdot 0.311)] = 35.70\Omega + j \cdot 24.75\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 17.85\Omega + j \cdot 12.37\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.426 + j \cdot 0.260 = 0.499 \angle 148.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.499$, $\arg(\Gamma) = 148.6^\circ$
 $\theta_{S1} = 165.7^\circ$; $\text{Im}(y_S) = -1.153$; $\theta_{P1} = 130.9^\circ$ **and** $\theta_{S2} = 45.7^\circ$; $\text{Im}(y_S) = 1.153$; $\theta_{P2} = 49.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.90dB$): $G(1,2) = G_1 + G_2 = 8.6 + 11.0 = 19.6dB$; $G(1,4) = G_1 + G_4 = 8.6 + 8.6 = 17.2dB$; $G(2,3) = G_2 + G_3 = 11.0 + 6.4 = 17.4dB$; $G(2,4) = G_2 + G_4 = 11.0 + 8.6 = 19.6dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.09dB = 1.285$, $F_2 = 1.22dB = 1.324$, $F_3 = 0.63dB = 1.156$, $F_4 = 0.82dB = 1.208$, $G_3 = 6.4dB = 4.365$, $G_4 = 8.6dB = 7.244$;

$F(4,1) = 1.208 + (1.285 - 1)/7.244 = 1.247 = 0.96dB$; $F(3,2) = 1.156 + (1.324 - 1)/4.365 = 1.230 = 0.90dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.3	$0.077 + j \cdot (-0.339)$	0.347	0.826	0.784
4.0	$-0.009 + j \cdot (-0.489)$	0.489	0.387	0.418

b) $\mu(2.3GHz) > \mu(4.0GHz)$ so the transistor has better stability at 2.3 GHz

c) we use S parameters for f = 2.3 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 65.10 = 18.14dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.072$, $U_{minus} = -0.605dB$, $U_{plus} = 0.651dB$ (L8/2021, S142)

Subject no. 35

1. $z = 1.135 + j \cdot 0.885$; $Y = 1 / 50\Omega / (1.135 + j \cdot 0.885) = 0.0110S + j \cdot (-0.0085)S$; $\Gamma = (z-1)/(z+1) = (1.135 + j \cdot 0.885 - 1)/(1.135 + j \cdot 0.885 + 1) = 0.201 + j \cdot (0.331) = 0.387 \angle 58.8^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

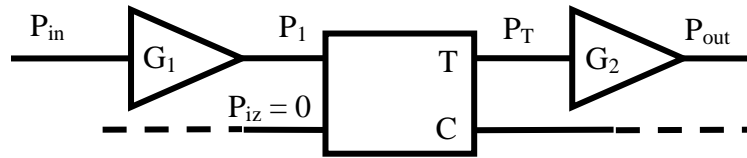2. $P_{in} = 1.25mW = 0.97dBm$; $P_1 = P_{in} + G_1 = 0.97dBm + 9.9dB = 10.87dBm = 12.22mW$; $P_c = P_1 - C = 10.87dBm - 5.90dB = 4.97dBm = 3.14mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 12.22mW - 3.14mW = 9.08mW = 9.58dBm$; $P_{out} = P_T + G_2 = 9.58dBm + 9.6dB = 19.18dBm = 82.77mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.191 + j \cdot 0.767 + 1)/[1 - (0.191 + j \cdot 0.767)] = 15.10\Omega + j \cdot 61.72\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 7.55\Omega + j \cdot 30.86\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.350 + j \cdot 0.724 = 0.804 \angle 115.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.804$, $\arg(\Gamma) = 115.8^\circ$
 $\theta_{S1} = 13.9^\circ$; $\text{Im}(y_S) = -2.701$; $\theta_{P1} = 110.3^\circ$ **and** $\theta_{S2} = 50.4^\circ$; $\text{Im}(y_S) = 2.701$; $\theta_{P2} = 69.7^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.85dB$): $G(1,2) = G_1 + G_2 = 9.8 + 10.3 = 20.1dB$; $G(1,4) = G_1 + G_4 = 9.8 + 8.7 = 18.5dB$; $G(2,3) = G_2 + G_3 = 10.3 + 6.7 = 17.0dB$; $G(2,4) = G_2 + G_4 = 10.3 + 8.7 = 19.0dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.08dB = 1.282$, $F_2 = 1.12dB = 1.294$, $F_3 = 0.62dB = 1.153$, $F_4 = 0.73dB = 1.183$, $G_3 = 6.7dB = 4.677$, $G_4 = 8.7dB = 7.413$;

$F(4,1) = 1.183 + (1.282 - 1)/7.413 = 1.221 = 0.87dB$; $F(3,2) = 1.153 + (1.294 - 1)/4.677 = 1.216 = 0.85dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.8	$-0.007 + j \cdot (-0.350)$	0.350	0.908	0.942
1.3	$0.454 + j \cdot (-0.280)$	0.533	0.169	0.880

b) $\mu'(2.8GHz) > \mu'(1.3GHz)$ so the transistor has better stability at 2.8 GHz

c) we use S parameters for f = 2.8 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 44.84 = 16.52dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.052$, $U_{minus} = -0.443dB$, $U_{plus} = 0.467dB$ (L8/2021, S142)

Subject no. 36

1. $z = 0.725 - j \cdot 0.960$; $Y = 1 / 50\Omega / (0.725 - j \cdot 0.960) = 0.0100S + j \cdot (0.0133)S$; $\Gamma = (z-1)/(z+1) = (0.725 - j \cdot 0.960 - 1)/(0.725 - j \cdot 0.960 + 1) = 0.115 + j \cdot (-0.493) = 0.506 \angle -76.9^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

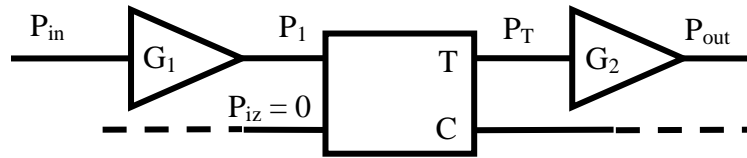2. $P_{in} = 2.50mW = 3.98dBm$; $P_1 = P_{in} + G_1 = 3.98dBm + 8.0dB = 11.98dBm = 15.77mW$; $P_c = P_1 - C = 11.98dBm - 5.20dB = 6.78dBm = 4.76mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 15.77mW - 4.76mW = 11.01mW = 10.42dBm$; $P_{out} = P_T + G_2 = 10.42dBm + 9.3dB = 19.72dBm = 93.71mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.093 + j \cdot 0.068 + 1)/[1 - (0.093 + j \cdot 0.068)] = 59.64\Omega + j \cdot 8.22\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 29.82\Omega + j \cdot 4.11\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.250 + j \cdot 0.064 = 0.258 \angle 165.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.258$, $\arg(\Gamma) = 165.5^\circ$
 $\theta_{S1} = 149.7^\circ$; $\text{Im}(y_S) = -0.533$; $\theta_{P1} = 151.9^\circ$ **and** $\theta_{S2} = 44.8^\circ$; $\text{Im}(y_S) = 0.533$; $\theta_{P2} = 28.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.85dB$): $G(1,2) = G_1 + G_2 = 9.2 + 10.0 = 19.2dB$; $G(1,4) = G_1 + G_4 = 9.2 + 8.5 = 17.7dB$; $G(2,3) = G_2 + G_3 = 10.0 + 6.3 = 16.3dB$; $G(2,4) = G_2 + G_4 = 10.0 + 8.5 = 18.5dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.92dB = 1.236$, $F_2 = 1.15dB = 1.303$, $F_3 = 0.66dB = 1.164$, $F_4 = 0.74dB = 1.186$, $G_3 = 6.3dB = 4.266$, $G_4 = 8.5dB = 7.079$;

$F(4,1) = 1.186 + (1.236-1)/7.079 = 1.219 = 0.86dB$; $F(3,2) = 1.164 + (1.303-1)/4.266 = 1.235 = 0.92dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.9	$0.138 + j \cdot (-0.322)$	0.350	0.737	0.689
4.8	$-0.137 + j \cdot (-0.444)$	0.464	0.484	0.517

b) $\mu(1.9GHz) > \mu(4.8GHz)$ so the transistor has better stability at 1.9 GHz

c) we use S parameters for f = 1.9 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 94.46 = 19.75dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.100$, $U_{minus} = -0.826dB$, $U_{plus} = 0.913dB$ (L8/2021, S142)

Subject no. 37

1. $z = 0.920 - j \cdot 0.915$; $Y = 1 / 50\Omega / (0.920 - j \cdot 0.915) = 0.0109S + j \cdot (0.0109)S$; $\Gamma = (z-1)/(z+1) = (0.920 - j \cdot 0.915 - 1)/(0.920 - j \cdot 0.915 + 1) = 0.151 + j \cdot (-0.405) = 0.432 \angle -69.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

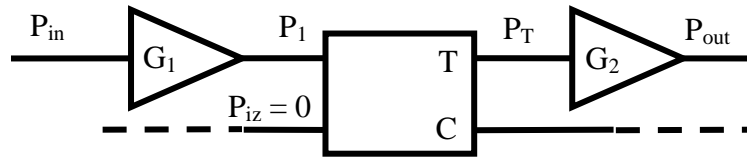2. $P_{in} = 1.15mW = 0.61dBm$; $P_1 = P_{in} + G_1 = 0.61dBm + 8.9dB = 9.51dBm = 8.93mW$; $P_c = P_1 - C = 9.51dBm - 4.50dB = 5.01dBm = 3.17mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.93mW - 3.17mW = 5.76mW = 7.60dBm$; $P_{out} = P_T + G_2 = 7.60dBm + 8.9dB = 16.50dBm = 44.71mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.088 + j \cdot 0.785 + 1)/[1 - (-0.088 + j \cdot 0.785)] = 10.45\Omega + j \cdot 43.61\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.22\Omega + j \cdot 21.81\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.567 + j \cdot 0.619 = 0.839 \angle 132.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.839$, $\arg(\Gamma) = 132.5^\circ$
 $\theta_{S1} = 7.3^\circ$; $\text{Im}(y_S) = -3.082$; $\theta_{P1} = 108.0^\circ$ **and** $\theta_{S2} = 40.2^\circ$; $\text{Im}(y_S) = 3.082$; $\theta_{P2} = 72.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.05dB$): $G(1,2) = G_1 + G_2 = 8.1 + 11.2 = 19.3dB$; $G(1,4) = G_1 + G_4 = 8.1 + 8.5 = 16.6dB$; $G(2,3) = G_2 + G_3 = 11.2 + 6.9 = 18.1dB$; $G(2,4) = G_2 + G_4 = 11.2 + 8.5 = 19.7dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.02dB = 1.265$, $F_2 = 1.20dB = 1.318$, $F_3 = 0.53dB = 1.130$, $F_4 = 0.77dB = 1.194$, $G_3 = 6.9dB = 4.898$, $G_4 = 8.5dB = 7.079$;

$F(4,1) = 1.194 + (1.265 - 1)/7.079 = 1.231 = 0.90dB$; $F(3,2) = 1.130 + (1.318 - 1)/4.898 = 1.195 = 0.77dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.7	$0.011 + j \cdot (-0.347)$	0.347	0.895	0.934
3.3	$0.119 + j \cdot (-0.488)$	0.502	0.325	0.791

b) $\mu'(2.7GHz) > \mu'(3.3GHz)$ so the transistor has better stability at 2.7 GHz

c) we use S parameters for f = 2.7 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 48.10 = 16.82dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.055$, $U_{minus} = -0.468dB$, $U_{plus} = 0.495dB$ (L8/2021, S142)

Subject no. 38

1. $z = 1.010 - j \cdot 0.865$; $Y = 1 / 50\Omega / (1.010 - j \cdot 0.865) = 0.0114S + j \cdot (0.0098)S$; $\Gamma = (z-1)/(z+1) = (1.010 - j \cdot 0.865 - 1)/(1.010 - j \cdot 0.865 + 1) = 0.160 + j \cdot (-0.361) = 0.395 \angle -66.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

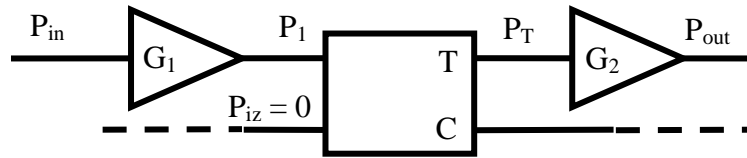2. $P_{in} = 2.15mW = 3.32dBm$; $P_1 = P_{in} + G_1 = 3.32dBm + 9.8dB = 13.12dBm = 20.53mW$; $P_c = P_1 - C = 13.12dBm - 4.35dB = 8.77dBm = 7.54mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 20.53mW - 7.54mW = 12.99mW = 11.14dBm$; $P_{out} = P_T + G_2 = 11.14dBm + 8.8dB = 19.94dBm = 98.55mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.318 + j \cdot 0.652 + 1)/[1 - (-0.318 + j \cdot 0.652)] = 10.96\Omega + j \cdot 30.15\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 5.48\Omega + j \cdot 15.08\Omega$;

$\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.679 + j \cdot 0.456 = 0.818 \angle 146.1^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.818$, $\arg(\Gamma) = 146.1^\circ$
 $\theta_{S1} = 179.4^\circ$; $\text{Im}(y_S) = -2.840$; $\theta_{P1} = 109.4^\circ$ **and** $\theta_{S2} = 34.5^\circ$; $\text{Im}(y_S) = 2.840$; $\theta_{P2} = 70.6^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.75dB$): $G(1,2) = G_1 + G_2 = 9.4 + 10.4 = 19.8dB$; $G(1,4) = G_1 + G_4 = 9.4 + 7.1 = 16.5dB$; $G(2,3) = G_2 + G_3 = 10.4 + 5.7 = 16.1dB$; $G(2,4) = G_2 + G_4 = 10.4 + 7.1 = 17.5dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.96dB=1.247$, $F_2 = 1.21dB=1.321$, $F_3 = 0.61dB=1.151$, $F_4 = 0.73dB=1.183$, $G_3 = 5.7dB=3.715$, $G_4 = 7.1dB=5.129$;

$F(4,1) = 1.183 + (1.247-1)/5.129 = 1.231 = 0.90dB$; $F(3,2) = 1.151 + (1.321-1)/3.715 = 1.237 = 0.92dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.5	$0.182 + j \cdot (-0.534)$	0.564	0.902	0.917
1.6	$0.414 + j \cdot (-0.328)$	0.529	0.192	0.859

b) $\mu'(2.5GHz) > \mu'(1.6GHz)$ so the transistor has better stability at 2.5 GHz

c) we use S parameters for f = 2.5 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 53.79 = 17.31dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.155$, $U_{minus} = -1.249dB$, $U_{plus} = 1.460dB$ (L8/2021, S142)

Subject no. 39

1. $z = 1.175 - j \cdot 0.910$; $Y = 1 / 50\Omega / (1.175 - j \cdot 0.910) = 0.0106S + j \cdot (0.0082)S$; $\Gamma = (z-1)/(z+1) = (1.175 - j \cdot 0.910 - 1)/(1.175 - j \cdot 0.910 + 1) = 0.217 + j \cdot (-0.327) = 0.393 \angle -56.4^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

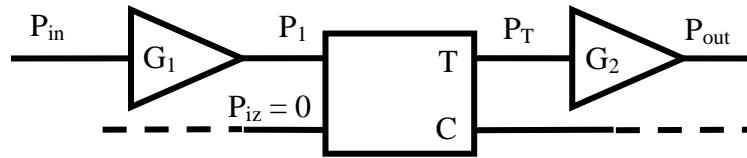2. $P_{in} = 1.65mW = 2.17dBm$; $P_1 = P_{in} + G_1 = 2.17dBm + 7.2dB = 9.37dBm = 8.66mW$; $P_c = P_1 - C = 9.37dBm - 4.25dB = 5.12dBm = 3.25mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.66mW - 3.25mW = 5.40mW = 7.33dBm$; $P_{out} = P_T + G_2 = 7.33dBm + 9.7dB = 17.03dBm = 50.44mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.444 + j \cdot 0.229 + 1) / [1 - (-0.444 + j \cdot 0.229)] = 17.55\Omega + j \cdot 10.71\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 8.78\Omega + j \cdot 5.36\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.687 + j \cdot 0.154 = 0.704 \angle 167.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.704$, $\arg(\Gamma) = 167.4^\circ$
 $\theta_{S1} = 163.7^\circ$; $\text{Im}(y_S) = -1.984$; $\theta_{P1} = 116.7^\circ$ **and** $\theta_{S2} = 28.9^\circ$; $\text{Im}(y_S) = 1.984$; $\theta_{P2} = 63.3^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 17.50dB$): $G(1,2) = G_1 + G_2 = 9.7 + 11.3 = 21.0dB$; $G(1,4) = G_1 + G_4 = 9.7 + 8.9 = 18.6dB$; $G(2,3) = G_2 + G_3 = 11.3 + 6.6 = 17.9dB$; $G(2,4) = G_2 + G_4 = 11.3 + 8.9 = 20.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.99dB = 1.256$, $F_2 = 1.15dB = 1.303$, $F_3 = 0.60dB = 1.148$, $F_4 = 0.85dB = 1.216$, $G_3 = 6.6dB = 4.571$, $G_4 = 8.9dB = 7.762$;

$F(4,1) = 1.216 + (1.256 - 1)/7.762 = 1.249 = 0.97dB$; $F(3,2) = 1.148 + (1.303 - 1)/4.571 = 1.214 = 0.84dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (**as requested!**) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.6	$0.026 + j \cdot (-0.349)$	0.350	0.875	0.921
4.3	$-0.062 + j \cdot (-0.478)$	0.482	0.418	0.783

b) $\mu'(2.6GHz) > \mu'(4.3GHz)$ so the transistor has better stability at 2.6 GHz

c) we use S parameters for f = 2.6 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 51.69 = 17.13dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.059$, $U_{minus} = -0.498dB$, $U_{plus} = 0.528dB$ (L8/2021, S142)

Subject no. 40

1. $z = 0.950 + j \cdot 1.240$; $Y = 1 / 50\Omega / (0.950 + j \cdot 1.240) = 0.0078S + j \cdot (-0.0102)S$; $\Gamma = (z-1)/(z+1) = (0.950 + j \cdot 1.240 - 1)/(0.950 + j \cdot 1.240 + 1) = 0.270 + j \cdot (0.464) = 0.537 \angle 59.9^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

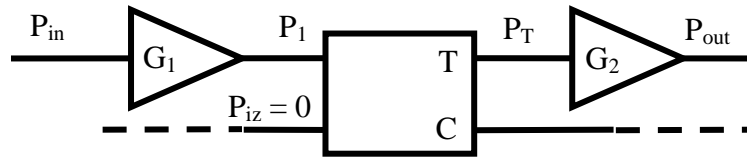2. $P_{in} = 2.10mW = 3.22dBm$; $P_1 = P_{in} + G_1 = 3.22dBm + 6.1dB = 9.32dBm = 8.55mW$; $P_c = P_1 - C = 9.32dBm - 5.70dB = 3.62dBm = 2.30mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 8.55mW - 2.30mW = 6.25mW = 7.96dBm$; $P_{out} = P_T + G_2 = 7.96dBm + 11.2dB = 19.16dBm = 82.42mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.020 + j \cdot 0.209 + 1)/[1 - (-0.020 + j \cdot 0.209)] = 44.09\Omega + j \cdot 19.28\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 22.04\Omega + j \cdot 9.64\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.364 + j \cdot 0.182 = 0.407 \angle 153.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.407$, $\arg(\Gamma) = 153.4^\circ$
 $\theta_{S1} = 160.3^\circ$; $\text{Im}(y_S) = -0.891$; $\theta_{P1} = 138.3^\circ$ **and** $\theta_{S2} = 46.3^\circ$; $\text{Im}(y_S) = 0.891$; $\theta_{P2} = 41.7^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 17.15dB$): $G(1,2) = G_1 + G_2 = 9.0 + 11.5 = 20.5dB$; $G(1,4) = G_1 + G_4 = 9.0 + 8.3 = 17.3dB$; $G(2,3) = G_2 + G_3 = 11.5 + 6.0 = 17.5dB$; $G(2,4) = G_2 + G_4 = 11.5 + 8.3 = 19.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.05dB = 1.274$, $F_2 = 1.22dB = 1.324$, $F_3 = 0.65dB = 1.161$, $F_4 = 0.77dB = 1.194$, $G_3 = 6.0dB = 3.981$, $G_4 = 8.3dB = 6.761$;

$F(4,1) = 1.194 + (1.274 - 1)/6.761 = 1.234 = 0.91dB$; $F(3,2) = 1.161 + (1.324 - 1)/3.981 = 1.243 = 0.94dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.3	$0.479 + j \cdot (-0.246)$	0.539	0.671	0.545
1.9	$0.372 + j \cdot (-0.372)$	0.526	0.217	0.240

b) $\mu(1.3GHz) > \mu(1.9GHz)$ so the transistor has better stability at 1.3 GHz

c) we use S parameters for f = 1.3 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 183.89 = 22.65dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.229$, $U_{minus} = -1.794dB$, $U_{plus} = 2.263dB$ (L8/2021, S142)

Subject no. 41

1. $z = 0.720 + j \cdot 1.115$; $Y = 1 / 50\Omega / (0.720 + j \cdot 1.115) = 0.0082S + j \cdot (-0.0127)S$; $\Gamma = (z-1)/(z+1) = (0.720 + j \cdot 1.115 - 1)/(0.720 + j \cdot 1.115 + 1) = 0.181 + j \cdot (0.531) = 0.561 \angle 71.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

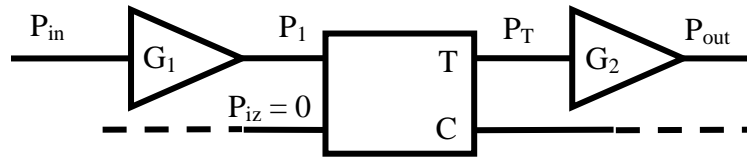2. $P_{in} = 1.65mW = 2.17dBm$; $P_1 = P_{in} + G_1 = 2.17dBm + 8.6dB = 10.77dBm = 11.95mW$; $P_c = P_1 - C = 10.77dBm - 5.00dB = 5.77dBm = 3.78mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 11.95mW - 3.78mW = 8.17mW = 9.12dBm$; $P_{out} = P_T + G_2 = 9.12dBm + 9.4dB = 18.52dBm = 71.19mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.338 + j \cdot 0.327 + 1)/[1 - (-0.338 + j \cdot 0.327)] = 20.53\Omega + j \cdot 17.24\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 10.26\Omega + j \cdot 8.62\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.626 + j \cdot 0.233 = 0.668 \angle 159.6^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.668$, $\arg(\Gamma) = 159.6^\circ$
 $\theta_{S1} = 166.1^\circ$; $\text{Im}(y_S) = -1.795$; $\theta_{P1} = 119.1^\circ$ **and** $\theta_{S2} = 34.2^\circ$; $\text{Im}(y_S) = 1.795$; $\theta_{P2} = 60.9^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.55dB$): $G(1,2) = G_1 + G_2 = 8.4 + 10.0 = 18.4dB$; $G(1,4) = G_1 + G_4 = 8.4 + 8.8 = 17.2dB$; $G(2,3) = G_2 + G_3 = 10.0 + 6.9 = 16.9dB$; $G(2,4) = G_2 + G_4 = 10.0 + 8.8 = 18.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.98dB = 1.253$, $F_2 = 1.17dB = 1.309$, $F_3 = 0.65dB = 1.161$, $F_4 = 0.86dB = 1.219$, $G_3 = 6.9dB = 4.898$, $G_4 = 8.8dB = 7.586$;

$F(4,1) = 1.219 + (1.253 - 1)/7.586 = 1.252 = 0.98dB$; $F(3,2) = 1.161 + (1.309 - 1)/4.898 = 1.225 = 0.88dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
0.9	$0.506 + j \cdot (-0.105)$	0.517	0.530	0.645
3.7	$0.047 + j \cdot (-0.490)$	0.492	0.385	0.791

b) $\mu'(0.9GHz) < \mu'(3.7GHz)$ so the transistor has better stability at 3.7 GHz

c) we use S parameters for f = 3.7 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 206.58 = 23.15dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.724$, $U_{minus} = -4.731dB$, $U_{plus} = 11.184dB$ (L8/2021, S142)

Subject no. 42

1. $z = 0.985 - j \cdot 1.175$; $Y = 1 / 50\Omega / (0.985 - j \cdot 1.175) = 0.0084S + j \cdot (0.0100)S$; $\Gamma = (z-1)/(z+1) = (0.985 - j \cdot 1.175 - 1)/(0.985 - j \cdot 1.175 + 1) = 0.254 + j \cdot (-0.442) = 0.509 \angle -60.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

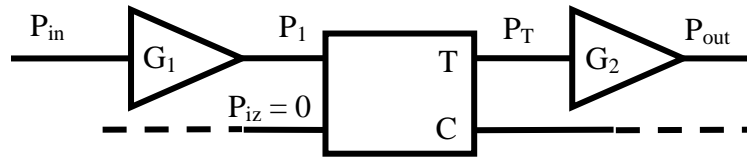2. $P_{in} = 1.25mW = 0.97dBm$; $P_1 = P_{in} + G_1 = 0.97dBm + 8.8dB = 9.77dBm = 9.48mW$; $P_c = P_1 - C = 9.77dBm - 6.35dB = 3.42dBm = 2.20mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 9.48mW - 2.20mW = 7.28mW = 8.62dBm$; $P_{out} = P_T + G_2 = 8.62dBm + 10.7dB = 19.32dBm = 85.59mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.097 + j \cdot 0.071 + 1) / [1 - (-0.097 + j \cdot 0.071)] = 40.78\Omega + j \cdot 5.88\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 20.39\Omega + j \cdot 2.94\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.418 + j \cdot 0.059 = 0.422 \angle 171.9^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.422$, $\arg(\Gamma) = 171.9^\circ$
 $\theta_{S1} = 151.5^\circ$; $\text{Im}(y_S) = -0.932$; $\theta_{P1} = 137.0^\circ$ **and** $\theta_{S2} = 36.5^\circ$; $\text{Im}(y_S) = 0.932$; $\theta_{P2} = 43.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.90dB$): $G(1,2) = G_1 + G_2 = 9.7 + 11.1 = 20.8dB$; $G(1,4) = G_1 + G_4 = 9.7 + 7.3 = 17.0dB$; $G(2,3) = G_2 + G_3 = 11.1 + 6.9 = 18.0dB$; $G(2,4) = G_2 + G_4 = 11.1 + 7.3 = 18.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.97dB = 1.250$, $F_2 = 1.17dB = 1.309$, $F_3 = 0.62dB = 1.153$, $F_4 = 0.87dB = 1.222$, $G_3 = 6.9dB = 4.898$, $G_4 = 7.3dB = 5.370$;

$F(4,1) = 1.222 + (1.250 - 1)/5.370 = 1.268 = 1.03dB$; $F(3,2) = 1.153 + (1.309 - 1)/4.898 = 1.217 = 0.85dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
1.7	$0.169 + j \cdot (-0.312)$	0.355	0.689	0.640
4.7	$-0.125 + j \cdot (-0.451)$	0.468	0.472	0.505

b) $\mu(1.7GHz) > \mu(4.7GHz)$ so the transistor has better stability at 1.7 GHz

c) we use S parameters for f = 1.7 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)

$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 116.95 = 20.68dB$


d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.119$, $U_{minus} = -0.974dB$, $U_{plus} = 1.097dB$

(L8/2021, S142)

Subject no. 43

1. $z = 0.745 - j \cdot 0.835$; $Y = 1 / 50\Omega / (0.745 - j \cdot 0.835) = 0.0119S + j \cdot (0.0133)S$; $\Gamma = (z-1)/(z+1) = (0.745 - j \cdot 0.835 - 1)/(0.745 - j \cdot 0.835 + 1) = 0.067 + j \cdot (-0.446) = 0.451 \angle -81.4^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

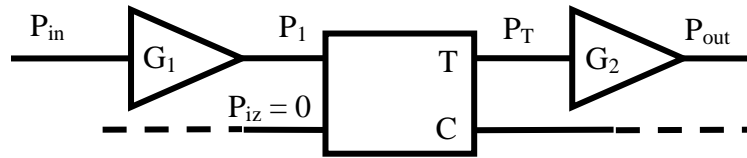2. $P_{in} = 1.10mW = 0.41dBm$; $P_1 = P_{in} + G_1 = 0.41dBm + 7.6dB = 8.01dBm = 6.33mW$; $P_c = P_1 - C = 8.01dBm - 6.45dB = 1.56dBm = 1.43mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 6.33mW - 1.43mW = 4.90mW = 6.90dBm$; $P_{out} = P_T + G_2 = 6.90dBm + 9.5dB = 16.40dBm = 43.64mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.308 + j \cdot 0.105 + 1)/[1 - (-0.308 + j \cdot 0.105)] = 25.96\Omega + j \cdot 6.10\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 12.98\Omega + j \cdot 3.05\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.584 + j \cdot 0.077 = 0.589 \angle 172.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.589$, $\arg(\Gamma) = 172.5^\circ$
 $\theta_{S1} = 156.8^\circ$; $\text{Im}(y_S) = -1.458$; $\theta_{P1} = 124.4^\circ$ **and** $\theta_{S2} = 30.7^\circ$; $\text{Im}(y_S) = 1.458$; $\theta_{P2} = 55.6^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.90dB$): $G(1,2) = G_1 + G_2 = 8.9 + 10.9 = 19.8dB$; $G(1,4) = G_1 + G_4 = 8.9 + 8.5 = 17.4dB$; $G(2,3) = G_2 + G_3 = 10.9 + 6.6 = 17.5dB$; $G(2,4) = G_2 + G_4 = 10.9 + 8.5 = 19.4dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.02dB = 1.265$, $F_2 = 1.26dB = 1.337$, $F_3 = 0.50dB = 1.122$, $F_4 = 0.75dB = 1.189$, $G_3 = 6.6dB = 4.571$, $G_4 = 8.5dB = 7.079$;

$F(4,1) = 1.189 + (1.265 - 1)/7.079 = 1.226 = 0.88dB$; $F(3,2) = 1.122 + (1.337 - 1)/4.571 = 1.196 = 0.78dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.7	$0.111 + j \cdot (-0.558)$	0.569	0.922	0.933
4.4	$-0.079 + j \cdot (-0.473)$	0.479	0.431	0.784

b) $\mu'(2.7GHz) > \mu'(4.4GHz)$ so the transistor has better stability at 2.7 GHz

c) we use S parameters for f = 2.7 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 46.65 = 16.69dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.151$, $U_{minus} = -1.224dB$, $U_{plus} = 1.425dB$ (L8/2021, S142)

Subject no. 44

1. $z = 1.280 + j \cdot 1.205$; $Y = 1 / 50\Omega / (1.280 + j \cdot 1.205) = 0.0083S + j \cdot (-0.0078)S$; $\Gamma = (z-1)/(z+1) = (1.280 + j \cdot 1.205 - 1)/(1.280 + j \cdot 1.205 + 1) = 0.314 + j \cdot (0.362) = 0.480 \angle 49.1^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

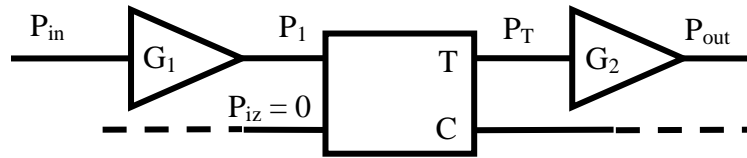2. $P_{in} = 3.45mW = 5.38dBm$; $P_1 = P_{in} + G_1 = 5.38dBm + 6.9dB = 12.28dBm = 16.90mW$; $P_c = P_1 - C = 12.28dBm - 4.30dB = 7.98dBm = 6.28mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 16.90mW - 6.28mW = 10.62mW = 10.26dBm$; $P_{out} = P_T + G_2 = 10.26dBm + 8.3dB = 18.56dBm = 71.80mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.262 + j \cdot 0.099 + 1)/[1 - (0.262 + j \cdot 0.099)] = 83.11\Omega + j \cdot 17.86\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 41.55\Omega + j \cdot 8.93\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.082 + j \cdot 0.106 = 0.134 \angle 127.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.134$, $\arg(\Gamma) = 127.8^\circ$
 $\theta_{S1} = 164.9^\circ$; $\text{Im}(y_S) = -0.270$; $\theta_{P1} = 164.9^\circ$ **and** $\theta_{S2} = 67.2^\circ$; $\text{Im}(y_S) = 0.270$; $\theta_{P2} = 15.1^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.45dB$): $G(1,2) = G_1 + G_2 = 8.8 + 10.6 = 19.4dB$; $G(1,4) = G_1 + G_4 = 8.8 + 8.2 = 17.0dB$; $G(2,3) = G_2 + G_3 = 10.6 + 6.6 = 17.2dB$; $G(2,4) = G_2 + G_4 = 10.6 + 8.2 = 18.8dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.90dB = 1.230$, $F_2 = 1.23dB = 1.327$, $F_3 = 0.58dB = 1.143$, $F_4 = 0.89dB = 1.227$, $G_3 = 6.6dB = 4.571$, $G_4 = 8.2dB = 6.607$;

$F(4,1) = 1.227 + (1.230 - 1)/6.607 = 1.262 = 1.01dB$; $F(3,2) = 1.143 + (1.327 - 1)/4.571 = 1.215 = 0.84dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.6	$0.146 + j \cdot (-0.550)$	0.569	0.910	0.922
2.9	$0.195 + j \cdot (-0.470)$	0.509	0.293	0.800

b) $\mu'(2.6GHz) > \mu'(2.9GHz)$ so the transistor has better stability at 2.6 GHz

c) we use S parameters for f = 2.6 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 50.09 = 17.00dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.153$, $U_{minus} = -1.236dB$, $U_{plus} = 1.442dB$ (L8/2021, S142)

Subject no. 45

1. $z = 0.910 - j \cdot 1.295$; $Y = 1 / 50\Omega / (0.910 - j \cdot 1.295) = 0.0073S + j \cdot (0.0103)S$; $\Gamma = (z-1)/(z+1) = (0.910 - j \cdot 1.295 - 1)/(0.910 - j \cdot 1.295 + 1) = 0.283 + j \cdot (-0.486) = 0.563 \angle -59.8^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

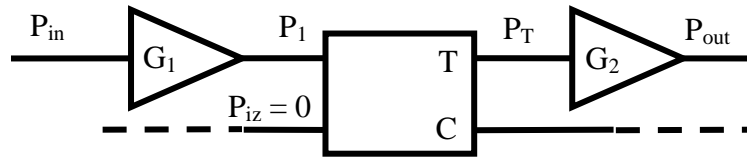2. $P_{in} = 1.20mW = 0.79dBm$; $P_1 = P_{in} + G_1 = 0.79dBm + 7.9dB = 8.69dBm = 7.40mW$; $P_c = P_1 - C = 8.69dBm - 5.85dB = 2.84dBm = 1.92mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 7.40mW - 1.92mW = 5.48mW = 7.38dBm$; $P_{out} = P_T + G_2 = 7.38dBm + 8.3dB = 15.68dBm = 37.02mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (-0.345 + j \cdot 0.191 + 1)/[1 - (-0.345 + j \cdot 0.191)] = 22.88\Omega + j \cdot 10.35\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 11.44\Omega + j \cdot 5.17\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.616 + j \cdot 0.136 = 0.631 \angle 167.5^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.631$, $\arg(\Gamma) = 167.5^\circ$
 $\theta_{S1} = 160.8^\circ$; $\text{Im}(y_S) = -1.627$; $\theta_{P1} = 121.6^\circ$ **and** $\theta_{S2} = 31.7^\circ$; $\text{Im}(y_S) = 1.627$; $\theta_{P2} = 58.4^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.35dB$): $G(1,2) = G_1 + G_2 = 8.9 + 11.6 = 20.5dB$; $G(1,4) = G_1 + G_4 = 8.9 + 8.1 = 17.0dB$; $G(2,3) = G_2 + G_3 = 11.6 + 6.2 = 17.8dB$; $G(2,4) = G_2 + G_4 = 11.6 + 8.1 = 19.7dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.01dB = 1.262$, $F_2 = 1.25dB = 1.334$, $F_3 = 0.64dB = 1.159$, $F_4 = 0.70dB = 1.175$, $G_3 = 6.2dB = 4.169$, $G_4 = 8.1dB = 6.457$;

$F(4,1) = 1.175 + (1.262 - 1)/6.457 = 1.215 = 0.85dB$; $F(3,2) = 1.159 + (1.334 - 1)/4.169 = 1.239 = 0.93dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
0.6	$0.467 + j \cdot (0.010)$	0.467	0.394	0.305
3.4	$0.100 + j \cdot (-0.492)$	0.502	0.330	0.360

b) $\mu(0.6GHz) < \mu(3.4GHz)$ so the transistor has better stability at 3.4 GHz

c) we use S parameters for f = 3.4 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 266.21 = 24.25dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.884$, $U_{minus} = -5.499dB$, $U_{plus} = 18.674dB$ (L8/2021, S142)

Subject no. 46

1. $z = 1.125 - j \cdot 1.015$; $Y = 1 / 50\Omega / (1.125 - j \cdot 1.015) = 0.0098S + j \cdot (0.0088)S$; $\Gamma = (z-1)/(z+1) = (1.125 - j \cdot 1.015 - 1)/(1.125 - j \cdot 1.015 + 1) = 0.234 + j \cdot (-0.366) = 0.434 \angle -57.4^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

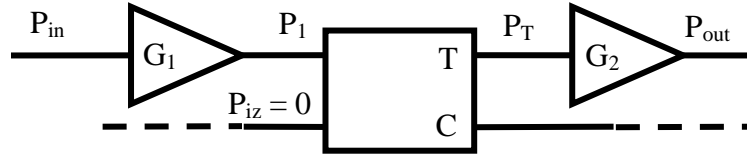2. $P_{in} = 2.30mW = 3.62dBm$; $P_1 = P_{in} + G_1 = 3.62dBm + 9.7dB = 13.32dBm = 21.46mW$; $P_c = P_1 - C = 13.32dBm - 6.20dB = 7.12dBm = 5.15mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 21.46mW - 5.15mW = 16.32mW = 12.13dBm$; $P_{out} = P_T + G_2 = 12.13dBm + 9.7dB = 21.83dBm = 152.27mW$



3. a) $\Gamma = (Z-50\Omega)/(Z+50\Omega)$; $Z = 50\Omega \cdot (1+\Gamma)/(1-\Gamma) = 50\Omega \cdot (0.043 + j \cdot 0.433 + 1)/[1 - (0.043 + j \cdot 0.433)] = 36.74\Omega + j \cdot 39.24\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 18.37\Omega + j \cdot 19.62\Omega$; $\Gamma = (Z/2-50\Omega)/(Z/2+50\Omega) = -0.351 + j \cdot 0.388 = 0.523 \angle 132.2^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.523$, $\arg(\Gamma) = 132.2^\circ$ $\theta_{S1} = 174.7^\circ$; $\text{Im}(y_S) = -1.228$; $\theta_{P1} = 129.2^\circ$ **and** $\theta_{S2} = 53.1^\circ$; $\text{Im}(y_S) = 1.228$; $\theta_{P2} = 50.8^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.40dB$): $G(1,2) = G_1 + G_2 = 8.1 + 10.5 = 18.6dB$; $G(1,4) = G_1 + G_4 = 8.1 + 8.4 = 16.5dB$; $G(2,3) = G_2 + G_3 = 10.5 + 5.6 = 16.1dB$; $G(2,4) = G_2 + G_4 = 10.5 + 8.4 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b-1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1-1)/G_4 < F_4 + (F_2-1)/G_4 < F_1 + (F_2-1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.95dB=1.245$, $F_2 = 1.11dB=1.291$, $F_3 = 0.64dB=1.159$, $F_4 = 0.70dB=1.175$, $G_3 = 5.6dB=3.631$, $G_4 = 8.4dB=6.918$;

$F(4,1) = 1.175 + (1.245-1)/6.918 = 1.210 = 0.83dB$; $F(3,2) = 1.159 + (1.291-1)/3.631 = 1.239 = 0.93dB$;

$F(4,1) < F(3,2) \rightarrow$ minimum noise is when we use devices **4,1**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
0.3	$0.357 + j \cdot (0.082)$	0.366	0.206	0.585
5.1	$-0.177 + j \cdot (-0.418)$	0.454	0.528	0.804

b) $\mu' (0.3GHz) < \mu' (5.1 GHz)$ so the transistor has better stability at 5.1 GHz

c) we use S parameters for f = 5.1 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 109.67 = 20.40dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.446$, $U_{minus} = -3.206dB$, $U_{plus} = 5.137dB$ (L8/2021, S142)

Subject no. 47

1. $z = 1.090 + j \cdot 1.290$; $Y = 1 / 50\Omega / (1.090 + j \cdot 1.290) = 0.0076S + j \cdot (-0.0090)S$; $\Gamma = (z-1)/(z+1) = (1.090 + j \cdot 1.290 - 1)/(1.090 + j \cdot 1.290 + 1) = 0.307 + j \cdot (0.428) = 0.527 \angle 54.3^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

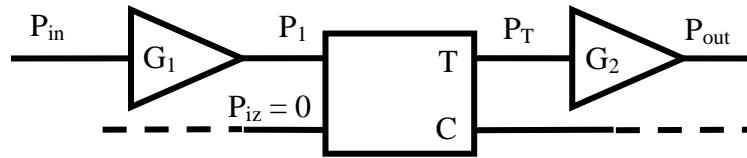2. $P_{in} = 2.15mW = 3.32dBm$; $P_1 = P_{in} + G_1 = 3.32dBm + 9.1dB = 12.42dBm = 17.48mW$; $P_c = P_1 - C = 12.42dBm - 5.70dB = 6.72dBm = 4.70mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 17.48mW - 4.70mW = 12.77mW = 11.06dBm$; $P_{out} = P_T + G_2 = 11.06dBm + 8.7dB = 19.76dBm = 94.68mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.470 + j \cdot 0.539 + 1)/[1 - (0.470 + j \cdot 0.539)] = 42.75\Omega + j \cdot 94.33\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 21.38\Omega + j \cdot 47.16\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.025 + j \cdot 0.644 = 0.645 \angle 87.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.645$, $\arg(\Gamma) = 87.8^\circ$; $\theta_{S1} = 21.2^\circ$; $\text{Im}(y_S) = -1.688$; $\theta_{P1} = 120.6^\circ$ **and** $\theta_{S2} = 71.0^\circ$; $\text{Im}(y_S) = 1.688$; $\theta_{P2} = 59.4^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.40dB$): $G(1,2) = G_1 + G_2 = 8.8 + 11.0 = 19.8dB$; $G(1,4) = G_1 + G_4 = 8.8 + 7.9 = 16.7dB$; $G(2,3) = G_2 + G_3 = 11.0 + 6.5 = 17.5dB$; $G(2,4) = G_2 + G_4 = 11.0 + 7.9 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.07dB = 1.279$, $F_2 = 1.14dB = 1.300$, $F_3 = 0.58dB = 1.143$, $F_4 = 0.79dB = 1.199$, $G_3 = 6.5dB = 4.467$, $G_4 = 7.9dB = 6.166$;

$F(4,1) = 1.199 + (1.279 - 1)/6.166 = 1.245 = 0.95dB$; $F(3,2) = 1.143 + (1.300 - 1)/4.467 = 1.210 = 0.83dB$; $F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.9	$0.042 + j \cdot (-0.569)$	0.571	0.941	0.879
4.2	$-0.043 + j \cdot (-0.484)$	0.486	0.409	0.439

b) $\mu(2.9GHz) > \mu(4.2GHz)$ so the transistor has better stability at 2.9 GHz

c) we use S parameters for f = 2.9 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 41.09 = 16.14dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.151$, $U_{minus} = -1.223dB$, $U_{plus} = 1.424dB$ (L8/2021, S142)

Subject no. 48

1. $z = 0.820 + j \cdot 0.720$; $Y = 1 / 50\Omega / (0.820 + j \cdot 0.720) = 0.0138S + j \cdot (-0.0121)S$; $\Gamma = (z-1)/(z+1) = (0.820 + j \cdot 0.720 - 1)/(0.820 + j \cdot 0.720 + 1) = 0.050 + j \cdot (0.376) = 0.379 \angle 82.5^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

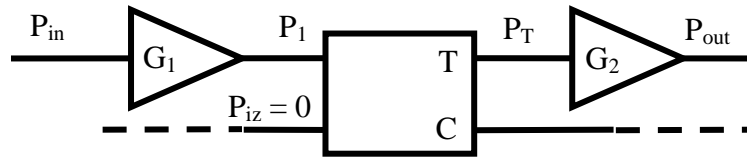2. $P_{in} = 2.10mW = 3.22dBm$; $P_1 = P_{in} + G_1 = 3.22dBm + 9.6dB = 12.82dBm = 19.15mW$; $P_c = P_1 - C = 12.82dBm - 5.80dB = 7.02dBm = 5.04mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 19.15mW - 5.04mW = 14.11mW = 11.50dBm$; $P_{out} = P_T + G_2 = 11.50dBm + 9.3dB = 20.80dBm = 120.14mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.116 + j \cdot 0.117 + 1)/[1 - (0.116 + j \cdot 0.117)] = 61.17\Omega + j \cdot 14.71\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 30.59\Omega + j \cdot 7.36\Omega$;

$\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.231 + j \cdot 0.112 = 0.257 \angle 154.0^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.257$, $\arg(\Gamma) = 154.0^\circ$
 $\theta_{S1} = 155.4^\circ$; $\text{Im}(y_S) = -0.531$; $\theta_{P1} = 152.0^\circ$ **and** $\theta_{S2} = 50.6^\circ$; $\text{Im}(y_S) = 0.531$; $\theta_{P2} = 28.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.80dB$): $G(1,2) = G_1 + G_2 = 9.2 + 11.8 = 21.0dB$; $G(1,4) = G_1 + G_4 = 9.2 + 7.1 = 16.3dB$; $G(2,3) = G_2 + G_3 = 11.8 + 6.5 = 18.3dB$; $G(2,4) = G_2 + G_4 = 11.8 + 7.1 = 18.9dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 0.95dB = 1.245$, $F_2 = 1.12dB = 1.294$, $F_3 = 0.69dB = 1.172$, $F_4 = 0.79dB = 1.199$, $G_3 = 6.5dB = 4.467$, $G_4 = 7.1dB = 5.129$;

$F(4,1) = 1.199 + (1.245 - 1)/5.129 = 1.247 = 0.96dB$; $F(3,2) = 1.172 + (1.294 - 1)/4.467 = 1.238 = 0.93dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.4	$0.061 + j \cdot (-0.344)$	0.349	0.844	0.900
3.9	$0.013 + j \cdot (-0.489)$	0.490	0.390	0.785

b) $\mu'(2.4GHz) > \mu'(3.9GHz)$ so the transistor has better stability at 2.4 GHz

c) we use S parameters for f = 2.4 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 59.76 = 17.76dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.067$, $U_{minus} = -0.566dB$, $U_{plus} = 0.606dB$ (L8/2021, S142)

Subject no. 49

1. $z = 1.005 + j \cdot 0.725$; $Y = 1 / 50\Omega / (1.005 + j \cdot 0.725) = 0.0131S + j \cdot (-0.0094)S$; $\Gamma = (z-1)/(z+1) = (1.005 + j \cdot 0.725 - 1)/(1.005 + j \cdot 0.725 + 1) = 0.118 + j \cdot (0.319) = 0.340 \angle 69.7^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

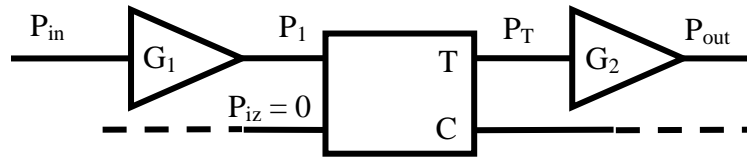2. $P_{in} = 3.30mW = 5.19dBm$; $P_1 = P_{in} + G_1 = 5.19dBm + 9.3dB = 14.49dBm = 28.09mW$; $P_c = P_1 - C = 14.49dBm - 6.95dB = 7.54dBm = 5.67mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 28.09mW - 5.67mW = 22.42mW = 13.51dBm$; $P_{out} = P_T + G_2 = 13.51dBm + 11.6dB = 25.11dBm = 324.05mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.448 + j \cdot 0.484 + 1)/[1 - (0.448 + j \cdot 0.484)] = 52.42\Omega + j \cdot 89.80\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 26.21\Omega + j \cdot 44.90\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = 0.026 + j \cdot 0.574 = 0.574 \angle 87.4^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.574$, $\arg(\Gamma) = 87.4^\circ$; $\theta_{S1} = 18.8^\circ$; $\text{Im}(y_S) = -1.404$; $\theta_{P1} = 125.5^\circ$ **and** $\theta_{S2} = 73.8^\circ$; $\text{Im}(y_S) = 1.404$; $\theta_{P2} = 54.5^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 15.55dB$): $G(1,2) = G_1 + G_2 = 9.2 + 11.4 = 20.6dB$; $G(1,4) = G_1 + G_4 = 9.2 + 7.1 = 16.3dB$; $G(2,3) = G_2 + G_3 = 11.4 + 5.8 = 17.2dB$; $G(2,4) = G_2 + G_4 = 11.4 + 7.1 = 18.5dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.02dB = 1.265$, $F_2 = 1.10dB = 1.288$, $F_3 = 0.52dB = 1.127$, $F_4 = 0.85dB = 1.216$, $G_3 = 5.8dB = 3.802$, $G_4 = 7.1dB = 5.129$;

$F(4,1) = 1.216 + (1.265 - 1)/5.129 = 1.268 = 1.03dB$; $F(3,2) = 1.127 + (1.288 - 1)/3.802 = 1.203 = 0.80dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ
2.1	$0.109 + j \cdot (-0.331)$	0.349	0.787	0.742
1.4	$0.444 + j \cdot (-0.292)$	0.531	0.170	0.190

b) $\mu(2.1GHz) > \mu(1.4GHz)$ so the transistor has better stability at 2.1 GHz

c) we use S parameters for $f = 2.1GHz$ and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)


$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 77.40 = 18.89dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.084$, $U_{minus} = -0.699dB$, $U_{plus} = 0.760dB$ (L8/2021, S142)

Subject no. 50

1. $z = 1.060 - j \cdot 1.105$; $Y = 1 / 50\Omega / (1.060 - j \cdot 1.105) = 0.0090S + j \cdot (0.0094)S$; $\Gamma = (z-1)/(z+1) = (1.060 - j \cdot 1.105 - 1)/(1.060 - j \cdot 1.105 + 1) = 0.246 + j \cdot (-0.404) = 0.473 \angle -58.7^\circ$, plot point in complex plane either with rectangular coordinates or polar coordinates

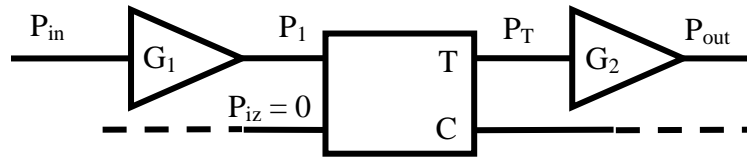2. $P_{in} = 3.40mW = 5.31dBm$; $P_1 = P_{in} + G_1 = 5.31dBm + 9.9dB = 15.21dBm = 33.23mW$; $P_c = P_1 - C = 15.21dBm - 4.45dB = 10.76dBm = 11.93mW$; Lossless coupler: $P_T = P_1 - P_c - P_{iz} = 33.23mW - 11.93mW = 21.30mW = 13.28dBm$; $P_{out} = P_T + G_2 = 13.28dBm + 11.0dB = 24.28dBm = 268.16mW$



3. a) $\Gamma = (Z - 50\Omega)/(Z + 50\Omega)$; $Z = 50\Omega \cdot (1 + \Gamma)/(1 - \Gamma) = 50\Omega \cdot (0.036 + j \cdot 0.484 + 1) / [1 - (0.036 + j \cdot 0.484)] = 32.85\Omega + j \cdot 41.60\Omega$

b) 2 identical loads from a) in parallel connection will have an impedance $Z/2 = 16.42\Omega + j \cdot 20.80\Omega$; $\Gamma = (Z/2 - 50\Omega)/(Z/2 + 50\Omega) = -0.371 + j \cdot 0.429 = 0.567 \angle 130.8^\circ$;

c) Complex calculus from L7/2021, S165÷169, 2 solutions for the match, $|\Gamma| = 0.567$, $\arg(\Gamma) = 130.8^\circ$ $\theta_{S1} = 176.9^\circ$; $\text{Im}(y_S) = -1.378$; $\theta_{P1} = 126.0^\circ$ **and** $\theta_{S2} = 52.3^\circ$; $\text{Im}(y_S) = 1.378$; $\theta_{P2} = 54.0^\circ$, all lines with $Z_0 = 50\Omega$

d) The shunt stub θ_{P1}/θ_{P2} must be in parallel with the 50Ω source

4. a) From the 6 possible combinations, 2 don't offer the required gain (1,3 ; 3,4).

The 4 possible combinations ($G > 16.90dB$): $G(1,2) = G_1 + G_2 = 9.9 + 11.0 = 20.9dB$; $G(1,4) = G_1 + G_4 = 9.9 + 7.2 = 17.1dB$; $G(2,3) = G_2 + G_3 = 11.0 + 6.0 = 17.0dB$; $G(2,4) = G_2 + G_4 = 11.0 + 7.2 = 18.2dB$

b) Friis formula (L8/2021, S177), $F = F_a + (F_b - 1)/G_a$; We note that $F_3 < F_4 < F_1 < F_2$;

For every one of the 4 combinations of 2 devices, minimum noise factor is obtained if the first device in cascade is the one with lower noise. From the 4 possible combinations with required gain, we only have to compare (4,1) and (2,3) because always $F_4 + (F_1 - 1)/G_4 < F_4 + (F_2 - 1)/G_4 < F_1 + (F_2 - 1)/G_1$ so (4,2) and (1,2) will always have higher noise

$F_1 = 1.03dB = 1.268$, $F_2 = 1.11dB = 1.291$, $F_3 = 0.53dB = 1.130$, $F_4 = 0.75dB = 1.189$, $G_3 = 6.0dB = 3.981$, $G_4 = 7.2dB = 5.248$;

$F(4,1) = 1.189 + (1.268 - 1)/5.248 = 1.240 = 0.93dB$; $F(3,2) = 1.130 + (1.291 - 1)/3.981 = 1.203 = 0.80dB$;

$F(4,1) > F(3,2) \rightarrow$ minimum noise is when we use devices **3,2**, in that order

5. a) Must compute either μ or μ' (as requested!) (L8/2021, S82 or 83);

f [GHz]	Δ	$ \Delta $	K	μ'
2.4	$0.213 + j \cdot (-0.521)$	0.562	0.890	0.907
5.2	$-0.191 + j \cdot (-0.406)$	0.449	0.541	0.809

b) $\mu'(2.4GHz) > \mu'(5.2GHz)$ so the transistor has better stability at 2.4 GHz

c) we use S parameters for f = 2.4 GHz and assume $S_{12} = 0 \angle 0^\circ$ (unilateral - L8/2021, S141)

$G_{TUmax} = 1 / (1 - |S_{11}|^2) \cdot |S_{21}|^2 / (1 - |S_{22}|^2) = 57.78 = 17.62dB$

d) $U = |S_{11}| \cdot |S_{12}| \cdot |S_{21}| \cdot |S_{22}| / (1 - |S_{11}|^2) / (1 - |S_{22}|^2) = 0.154$, $U_{minus} = -1.247dB$, $U_{plus} = 1.457dB$ (L8/2021, S142)

